

Fernando Hernandez

TCET-2220

Chapter 5

12/10/2013

- 1) A 50Ω lossless line is terminated in $Z_2 = 15 - j20 \Omega$.
 - a) Plot the normalized impedance on a Smith chart.
 - b) Using the Smith chart, determine the corresponding normalized admittance y_2 .
 - c) Using the result of (b), determine the actual admittance Y_2 .

a) $z_2 = \frac{Z_2}{R_o} = \frac{15-j20}{50} = .3 - j.4$

b) $y_2 = 1.2 + j1.6$

c) $G_o = \frac{1}{R_o} = \frac{1}{50} = 0.02 S$

$$Y_2 = G_o y_2 = 0.02 S (1.2 + j1.6) = .024 + j.032$$

- 2) A 50Ω lossless line is terminated in $Y_2 = 0.01 + j0.02 S$.
 - a) Plot the normalized admittance on a Smith chart.
 - b) Using the Smith chart, determine the corresponding normalized impedance z_2 .
 - c) Using the result of (b), determine the actual impedance Z_2 .

a) $y_2 = \frac{Y_2}{G_o} = \frac{0.01+j0.02}{0.02} = .5 + j1$

b) $z_2 = 0.4 - j0.8$

c) $Z_2 = Z_o z_2 = 50(0.4 - j0.8) = 20 - j40$

- 3) For the system of Problem 5.1, determine the VSWR and the reflection coefficient.

$$VSWR = 3.9$$

$$\Gamma_2 = \frac{S - 1}{S + 1} = \frac{3.9 - 1}{3.9 + 1} = 0.592 \angle -133^\circ$$

- 4) For the system of Problem 5.1, determine the VSWR and the reflection coefficient.

$$VSWR = 4.3$$

$$\Gamma_2 = \frac{S - 1}{S + 1} = \frac{4.3 - 1}{4.3 + 1} = 0.623 \angle -97^\circ$$

5) A 50-Ω lossless line is terminated in a real load impedance $Z_2=R_2=150\Omega$. Using a Smith chart, determine the input impedance for each of the following line lengths:

$$z_2 = \frac{Z_2}{R_o} = \frac{150}{50} = 3$$

a)

$$0.15\lambda = 0.25 + 0.15 = 0.4$$

$$z_{in} = 0.46 - j0.62$$

$$Z_{in} = R_o z_{in} = 50 \times (0.46 - j0.62) = 23 + j31$$

b)

$$0.25\lambda = 0.25 + 0.25 = 0.5 \text{ or } 0$$

$$z_{in} = 0.32$$

$$Z_{in} = R_o z_{in} = 50 \times 0.32 = 16$$

c)

$$0.35\lambda = 0.25 + 0.35 = 0.6 - 0.5 = 0.1$$

$$z_{in} = 0.475 + j0.625$$

$$Z_{in} = R_o z_{in} = 50 \times (0.475 + j0.625) = 23.75 + j31.25$$

d)

$$0.45\lambda = 0.25 + 0.45 = 0.7 - 0.5 = 0.2$$

$$z_{in} = 1.7 + j1.4$$

$$Z_{in} = R_o z_{in} = 50 \times (1.7 + j1.4) = 85 + j70$$

6) A 50-Ω lossless line is terminated in a real load admittance $Y_2=0.01 \text{ S}$. Using a Smith chart, determine the input admittance for the following line lengths:

$$G_o = \frac{1}{R_o} = \frac{1}{50} = 0.02$$

$$y_2 = \frac{Y_2}{G_o} = \frac{0.01}{0.02} = 0.5$$

a)

$$0.125\lambda$$

$$y_{in} = 0.8 + j0.6$$

$$Y_{in} = G_o y_{in} = 0.02 \times (0.8 + j0.6) = 0.16 + j0.12$$

b)
 0.25λ
 $Y_{in} = 2$

$$Y_{in} = G_o y_{in} = 0.02 \times 2 = 0.04$$

c)
 0.375λ
 $y_{in} = 0.8 - j0.6$

$$Y_{in} = G_o y_{in} = 0.02 \times (0.8 - j0.6) = 0.16 - j0.12$$

d)
 0.50λ
 $y_{in} = 0.5$

$$Y_{in} = G_o y_{in} = 0.02 \times 0.5 = 0.01$$

7) A 50-Ω lossless line is terminated in a load impedance $Z_2 = 75 + j100\Omega$.

- a) Using a Smith chart, determine the input impedance for a line of length 0.2λ .
- b) Determine the VSWR and the reflection coefficient at the load.

a)

$$z_2 = \frac{Z_2}{R_o} = \frac{75 + j100}{50} = 1.5 - j2$$

$$z_{in} = 0.34 - j0.68$$

$$Z_{in} = R_o z_{in} = 50(0.34 - j0.68) = 17 - j34$$

b)

$$VSWR = 4.6$$

$$\Gamma_2 = \frac{S - 1}{S + 1} = \frac{4.6 - 1}{4.6 + 1} = 0.643 \angle 37^\circ$$

8) A 300-Ω lossless line is terminated in a load impedance $Z_2 = 150 - j240\Omega$.

- a) Using a Smith chart, determine the input impedance for a line of length 0.3λ .
- b) Determine the VSWR and the reflection coefficient at the load.

a)

$$z_2 = \frac{Z_2}{R_o} = \frac{150 - j240}{300} = 0.5 - j0.8$$

$$z_{in} = 1.18 + j1.41$$

$$Z_{in} = R_o z_{in} = 300(1.18 + j1.41) = 354 + j423$$

b)

$$VSWR = 3.5$$

$$\Gamma_2 = \frac{S - 1}{S + 1} = \frac{3.5 - 1}{3.5 + 1} = 0.556 \angle -94^\circ$$