







- a) Plot voltage at both ends of the line
- b) Repeat (a) for the currents

$$\Gamma_L = \frac{R_L - R_0}{R_L + R_0} = \frac{50 - 50}{50 + 50} = 0$$


$$\Gamma_g = \frac{R_g - R_0}{R_g + R_0} = \frac{50 - 50}{50 + 50} = 0$$

$$V_1^+ = E \frac{R_0}{R_0 + R_g} = 80 \left(\frac{50}{50 + 50} \right) = 40V \Rightarrow I_1^+ = \frac{40}{50} = 0.8$$
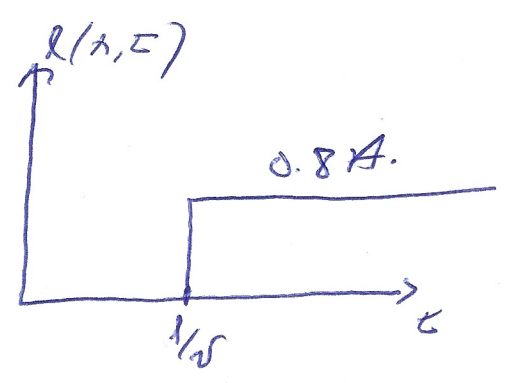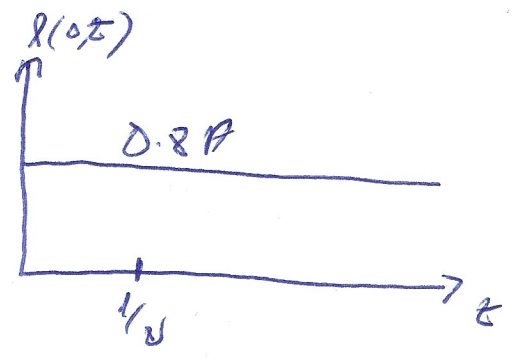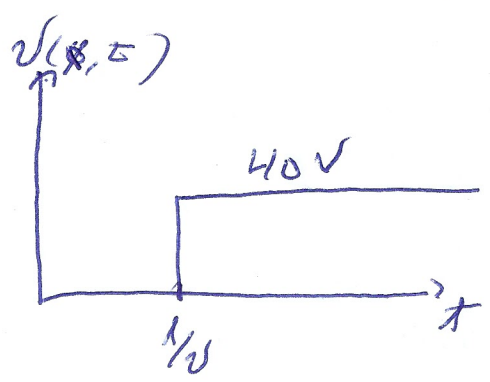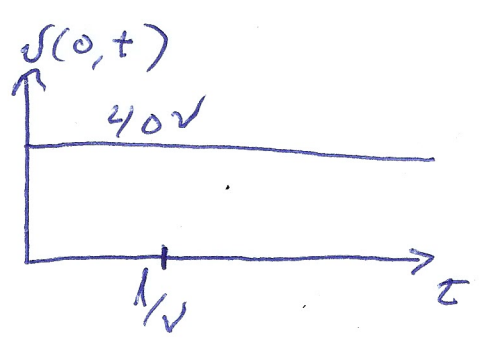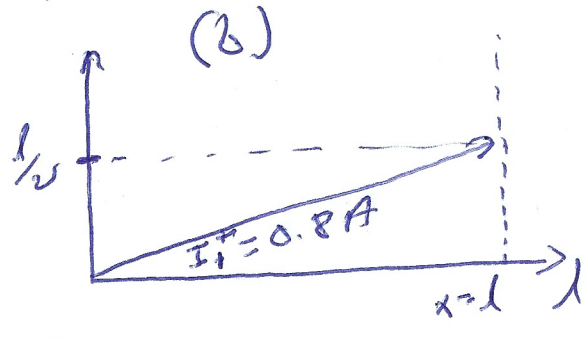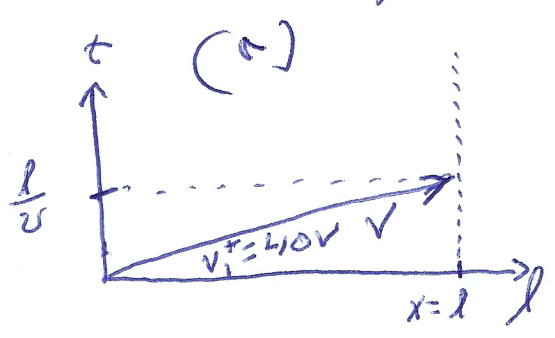
$$V_1^- = \Gamma_L (E V_1^+) = (0)(40) = 0V \Rightarrow I_1^- = \frac{0}{50} = 0A$$



2-2)



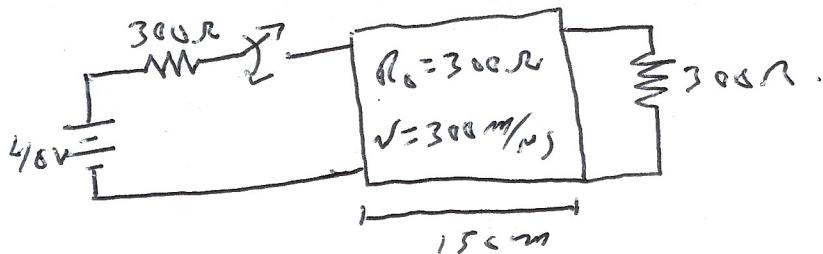


(2)

$$\Gamma_L = 0 \quad ; \quad \Gamma_g = 0$$

$$V_1^+ = E \left[\frac{R_0}{R_0 + R_g} \right] = 40 \left[\frac{300}{300 + 300} \right] = 20 \text{ V} \Rightarrow I_1^+ = \frac{V_1^+}{R_0} = \frac{20}{300} = 0.067$$
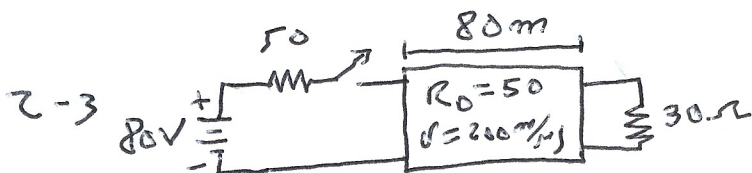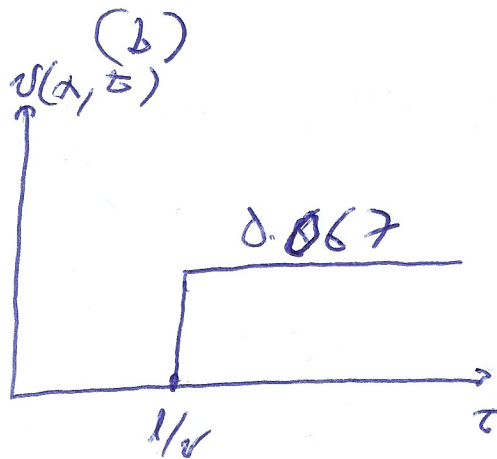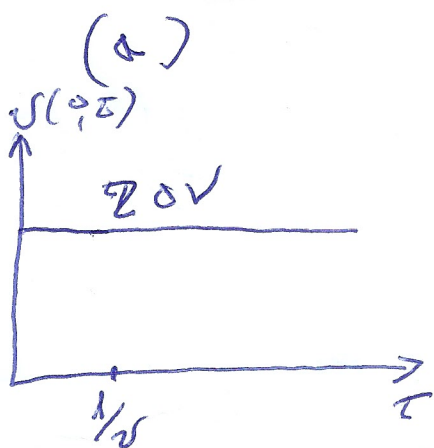
$$V_1^- = \Gamma_L (V_1^+) = 0 \Rightarrow I_1^- = \frac{V_1^-}{R_0} = \frac{0}{300} = 0 \text{ A}$$










$$\Gamma_L = \frac{R_L - R_0}{R_L + R_0} = \frac{30 - 50}{30 + 50} = -0.25$$

$$\Gamma_g = 0$$

$$V_1^+ = 80 \left(\frac{50}{50 + 50} \right) = 40 \text{ V} \Rightarrow I_1^+ = \frac{V_1^+}{R_0} = \frac{40}{50} = 0.8 \text{ A}$$

$$V_1^- = \Gamma_L (V_1^+) = -0.25(40) = -10 \text{ V} \Rightarrow I_1^- = \frac{-10}{50} = -0.2 \text{ A}$$
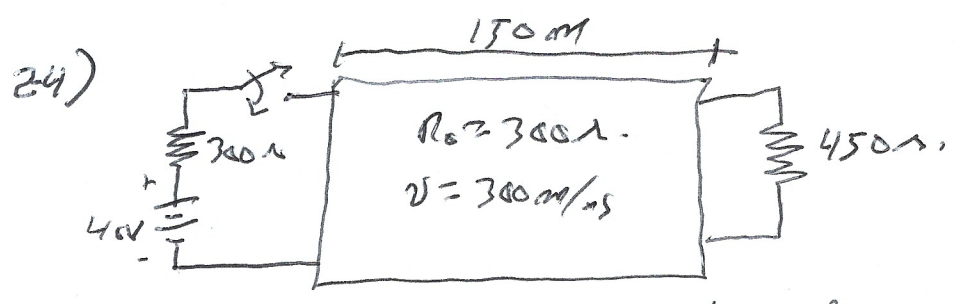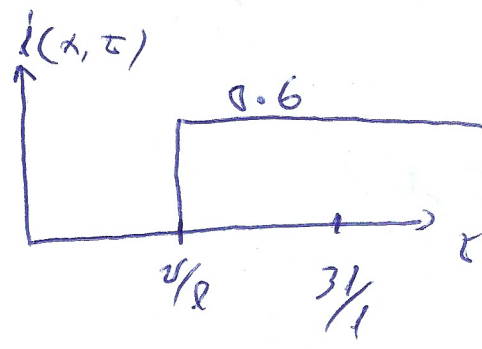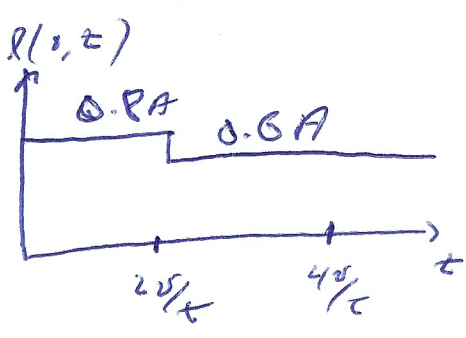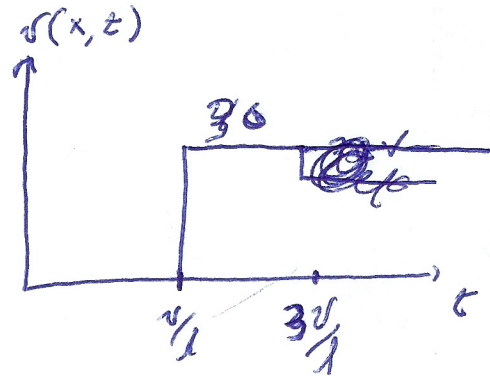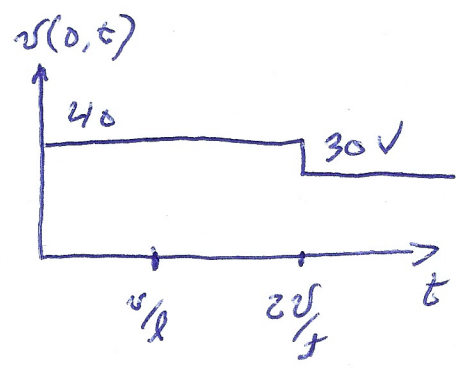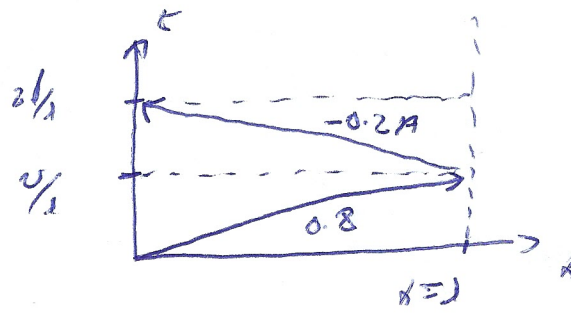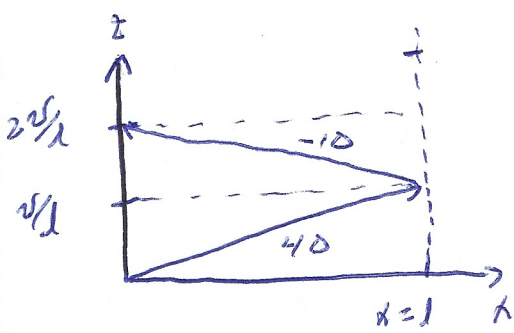
$$V_2^+ = \Gamma_g (V_1^-) = 0(-10) = 0 \Rightarrow I_2^+ = \frac{0}{R_0} = 0 \text{ A}$$




- a) Plot voltage at both end of the line
- b) repeat (a) for the currents.

$$t_1 = \frac{150}{\frac{300 \times 10^3}{10^8}} = 0.5 \mu s$$

$$\Gamma_g = \frac{300 - 300}{300 + 300} = 0$$

$$\Gamma_b = \frac{450 - 300}{300 + 300} = \frac{150}{600} = 0.25$$

2-5)

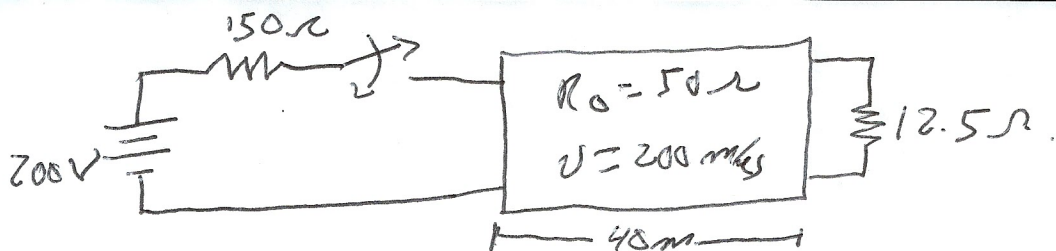

(4)

a) Plot the $V(z, t)$ and $I(z, t)$ b) repeat (a) for the currents $I(0, t)$ and $I(z, t)$

$$a) \tau_1 = \frac{40}{\frac{200 \text{ m}}{10^{-6} \text{ s}}} = 0.2 \text{ ms}$$

$$\Gamma_L = \frac{R_L - R_0}{R_L + R_0} = \frac{12.5 - 50}{12.5 + 50} = -0.6$$

$$\Gamma_g = \frac{R_g - R_0}{R_g + R_0} = \frac{150 - 50}{150 + 50} = 0.5$$

$$V_1^+ = E \left(\frac{R_0}{R_0 + R_g} \right) = \frac{50}{50 + 150} (200) = 50 \text{ V} \Rightarrow I_1^+ = \frac{V_1^+}{R_0} = \frac{50}{50} = 1 \text{ A}$$

$$V_1^- = \Gamma_L (V_1^+) = -0.6 (50) = -30 \text{ V} \Rightarrow I_1^- = \frac{-30}{50} = -0.6 \text{ A}$$

$$V_2^+ = \Gamma_g (V_1^-) = 0.5 (-30) = -15 \text{ V} \Rightarrow I_2^+ = \frac{-15}{50} = -0.3 \text{ A}$$






$$V_2^- = \Gamma_L (V_2^+) = -0.6 (-15) = 9 \text{ V} \Rightarrow I_2^- = \frac{9}{50} = 0.18 \text{ A}$$

$$V_3^+ = \Gamma_g (V_2^-) = 0.5 (9) = 4.5 \text{ V} \Rightarrow I_3^+ = \frac{4.5}{50} = 0.09 \text{ A}$$

$$V_3^- = \Gamma_L (V_3^+) = -0.6 (4.5) = -2.7 \text{ V} \Rightarrow I_3^- = \frac{-2.7}{50} = -0.054 \text{ A}$$

$$V_4^+ = \Gamma_g (V_3^-) = +0.5 (-2.7) = -1.35 \text{ V} \Rightarrow I_4^+ = \frac{-1.35}{50} = -0.027 \text{ A}$$
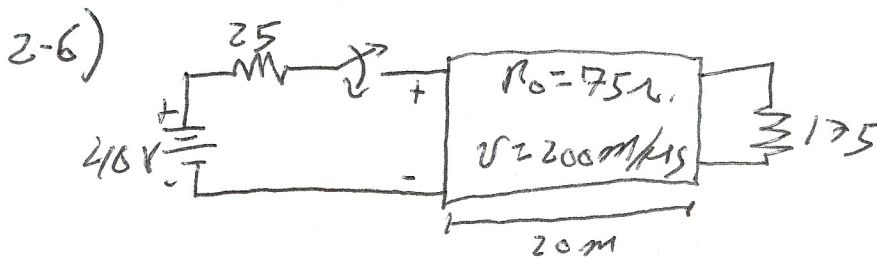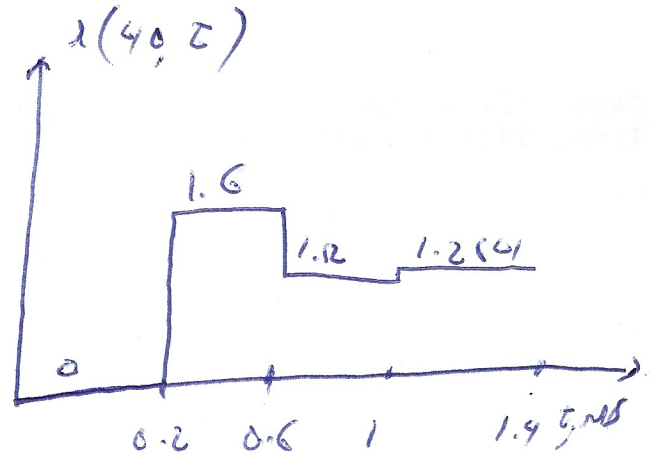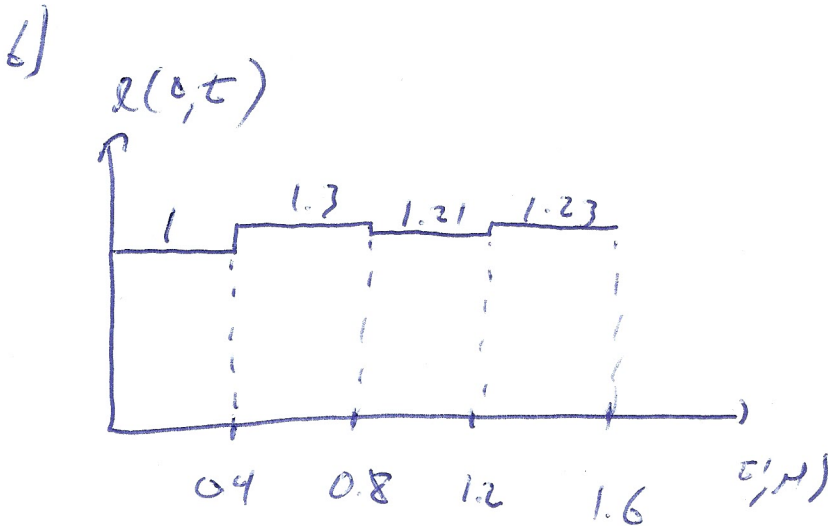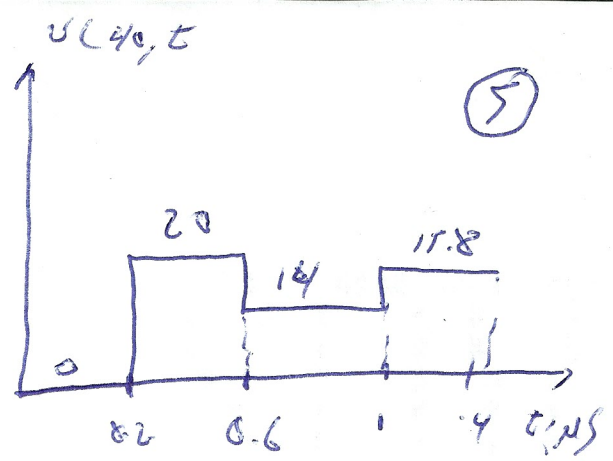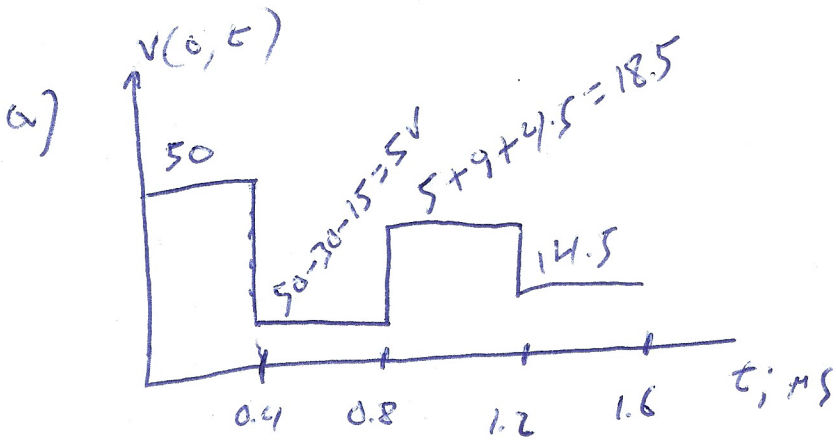
$$V_4^- = \Gamma_L (V_4^+) = -0.6 (-1.35) = 0.81 \text{ V} \Rightarrow I_4^- = \frac{0.81}{50} = 0.0162 \text{ A}$$



a) plot the $v(0, t)$ and $v(40, t)$

b) repeat (a) for the currents $i(0, t)$ and $i(40, t)$

$$t_c = \frac{20}{\frac{2000}{1615}} = 0.125$$

$$\Gamma_L = \frac{R_L - R_0}{R_L + R_0} = \frac{175 - 75}{175 + 75} = 0.4$$

$$\Gamma_g = \frac{R_g - R_0}{R_g + R_0} = \frac{25 - 75}{75 + 25} = -0.5$$

$$V_1^+ = E \left(\frac{R_0}{R_0 + R_1} \right) = 40 \left(\frac{75}{75 + 25} \right) = 30V \Rightarrow I_1^+ = \frac{30}{75} = 0.4A$$

$$V_1^- = \Gamma_L(V_1^+) = 0.4(30) = 12V \Rightarrow I_1^- = \frac{12}{75} = 0.16A$$

$$V_2^+ = \Gamma_g(V_1^-) = -0.5(12) = -6V \Rightarrow I_2^+ = \frac{-6}{75} = -0.08A$$





$$V_2^- = \Gamma_L(V_2^+) = 0.4(-6) = -2.4V \Rightarrow I_2^- = \frac{-2.4}{75} = -0.032A$$

$$V_3^+ = \Gamma_g(V_2^-) = -0.5(-2.4) = 1.2V \Rightarrow I_3^+ = \frac{1.2}{75} = 0.016A$$

$$V_3^- = \Gamma_L(V_3^+) = 0.4(1.2) = 0.48V \Rightarrow I_3^- = \frac{0.48}{75} = 0.0064A$$


$$V_4^+ = \Gamma_g(V_3^-) = -0.5(0.48) = -0.24V \Rightarrow I_4^+ = \frac{-0.24}{75} = -0.0032A$$
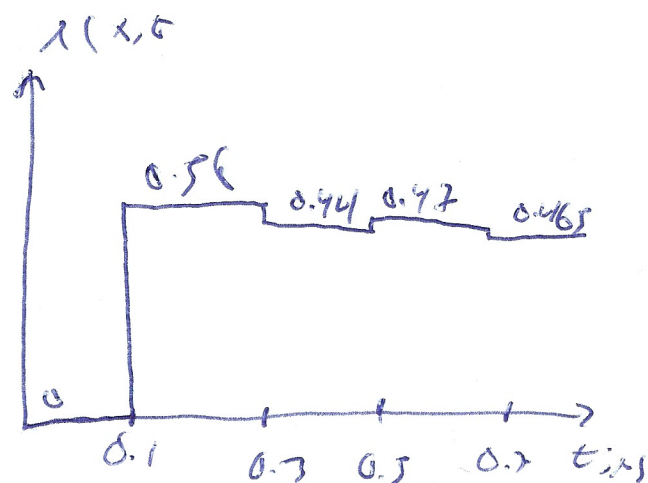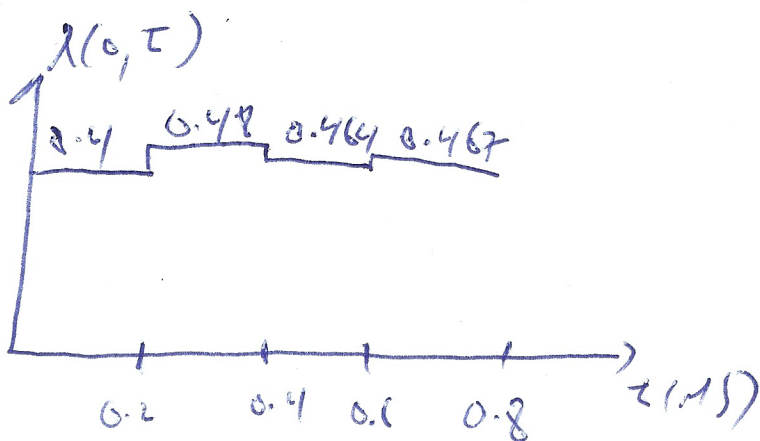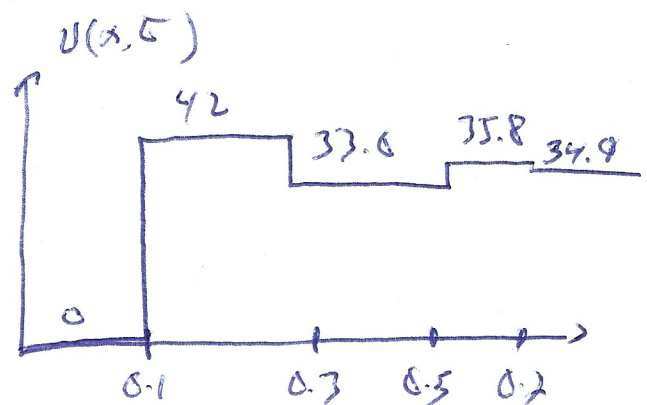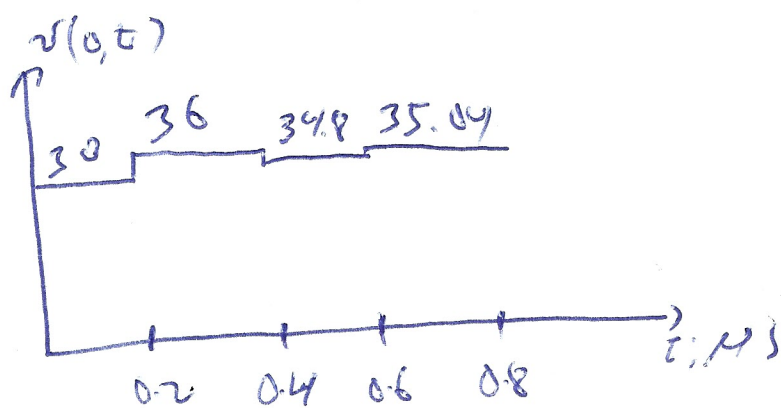
$$V_4^- = \Gamma_L(V_4^+) = 0.4(-0.24) = -0.096V \Rightarrow I_4^- = \frac{-0.096}{75} = -0.00128A$$



2-7)

(7)

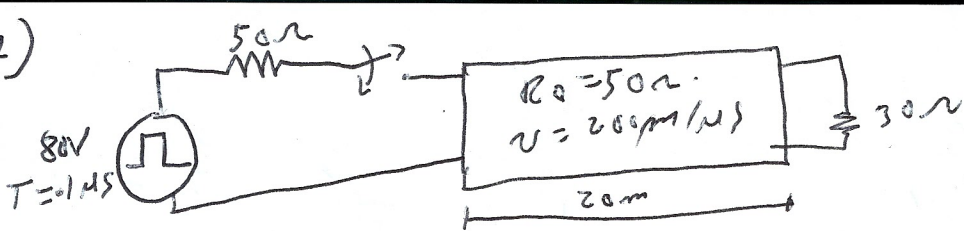

$$\Gamma_1 = \frac{50 - 50}{100} = 0$$

$$\Gamma_2 = \frac{30 - 50}{80} = -0.25$$





$$Z_1 = \frac{d}{v} = \frac{80}{\frac{200}{1 \times 10^{-6}}} = 0.4 \text{ ns}$$

$$V_1^+ = 80 \left[\frac{50}{100} \right] = 40 \text{ V} \Rightarrow I_1^+ = \frac{40}{50} = 0.8 \text{ A}$$


$$V_1^- = (40)(-0.25) = -10 \text{ V} \Rightarrow I_1^- = \frac{-10}{50} = -0.2 \text{ A}$$

$$V_2^+ = 0$$

$$\Rightarrow I_2^+ = 0$$

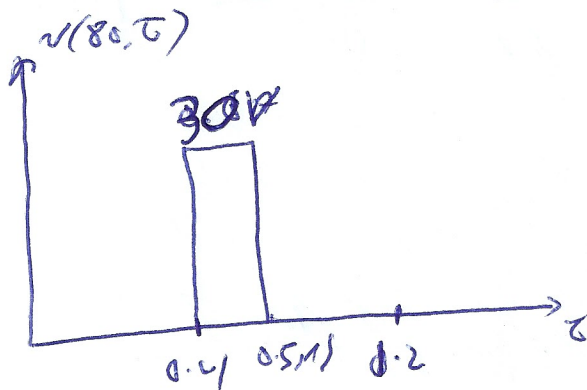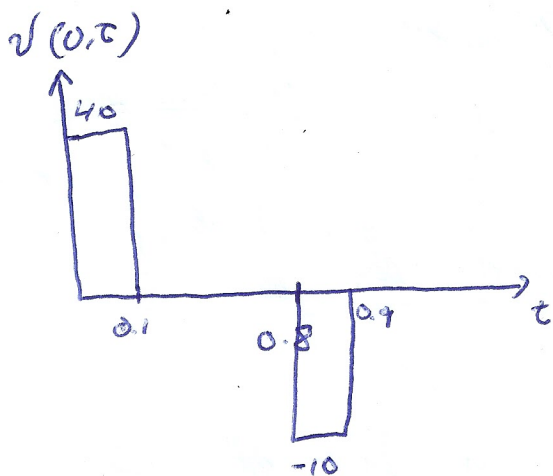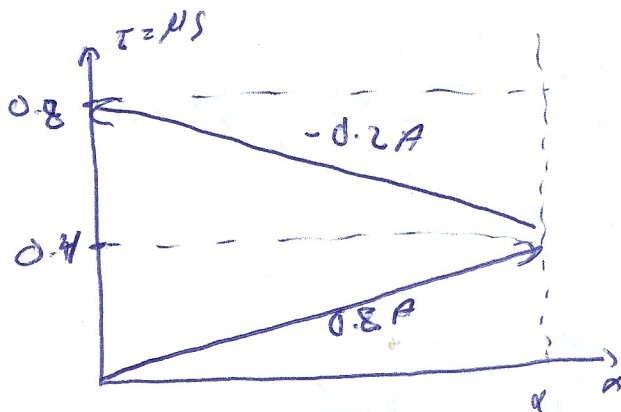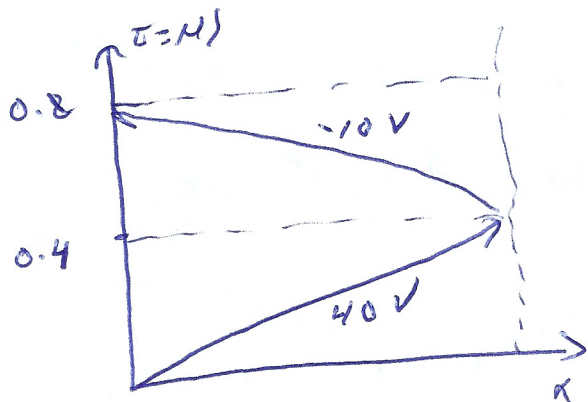

2-8

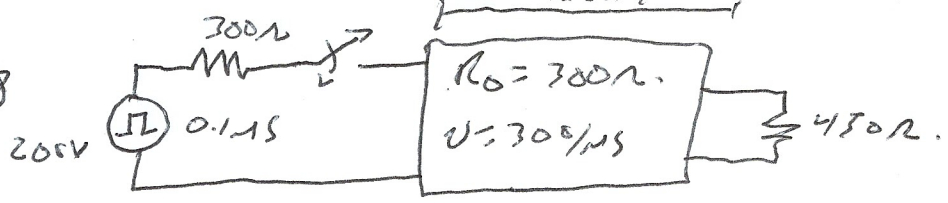

(8)

$$\Gamma_g = \frac{R_g - R_o}{R_g + R_o} = \frac{300 - 300}{600} = 0$$

$$\Gamma_L = \frac{R_L - R_o}{R_L + R_o} = \frac{450 - 300}{450 + 300} = \frac{150}{750} = 0.2$$

$$\tau = \frac{l}{v} = \frac{150}{\frac{300 \times 10^3}{10^6}} = 0.5 \mu s$$

$$V_1^+ = E \frac{R_o}{R_o + R_g} = 200 \left[\frac{300}{600} \right] = 100V \Rightarrow I_1^+ = \frac{100}{300} = 0.33A$$

$$V_1^- = \Gamma_L(V_1^+) = (0.2)(100) = 20V \Rightarrow I_1^- = \frac{20}{300} = 0.067A$$

