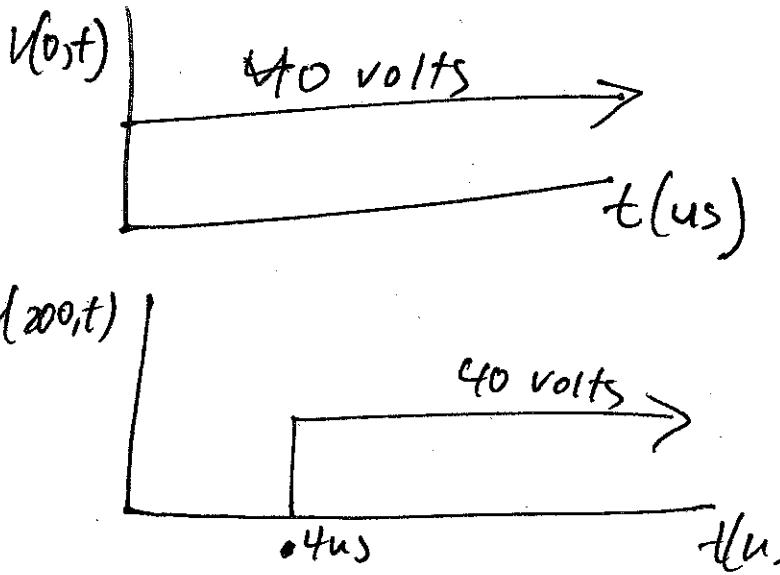


- 1a. For the circuit of Fig P 2-1, plot the voltages at both ends of the line.


$$\left( \frac{R_0}{R_0 + R_1} \right) * E = \left( \frac{50}{50 + 100} \right) * 80 = 40 \text{ Volts}$$

$$t = \frac{d}{v} = \frac{80}{200 \text{ m}/\mu\text{s}} = .4 \mu\text{s}$$



- 1b. Repeat (a) for the currents at both ends of the line.
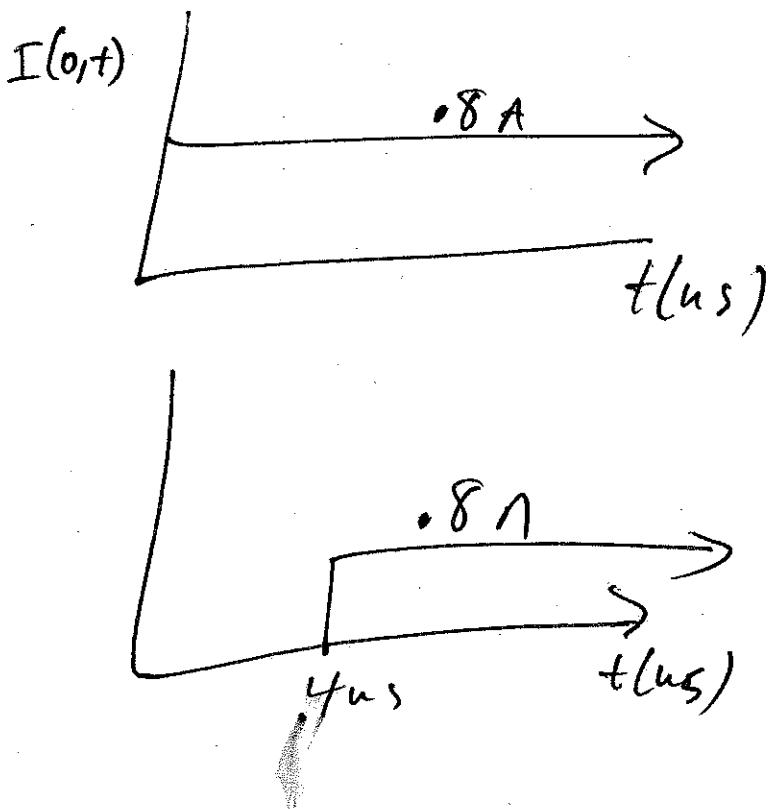
$$I = \frac{40 \text{ Volts}}{50 - \Omega} = .8 \text{ Amps}$$





2a. For the circuit of Fig. P2-2, plot the voltages at both ends of the line.

$$\Gamma_1 = \frac{R_1 - R_0}{R_0 + R_0} = \frac{300 - 300}{300 + 300} = 0$$

$$\Gamma_2 = \frac{R_2 - R_0}{R_2 + R_0} = \frac{300 - 300}{300 + 300} = 0$$

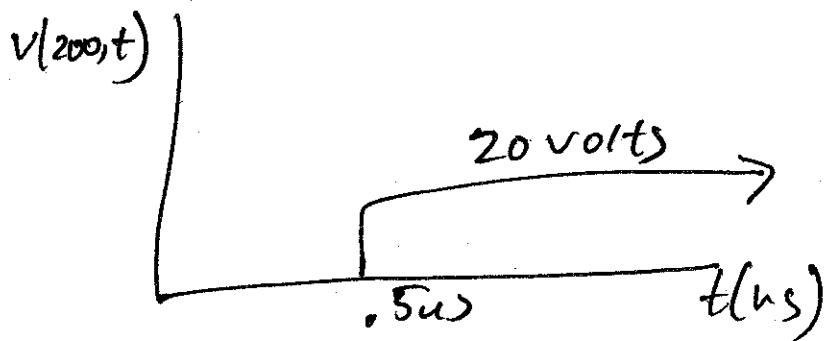
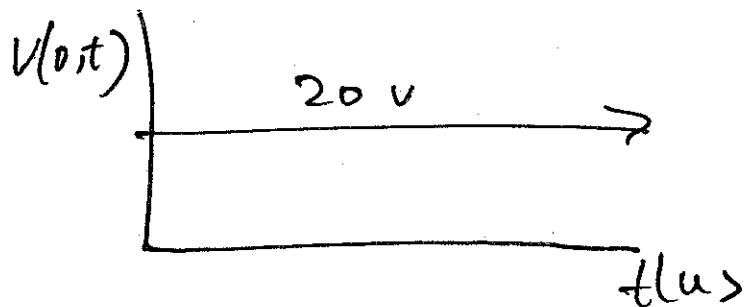
$$\left( \frac{R_0}{R_0 + R_1} \right) * E = \left( \frac{300}{300 + 300} \right) * 40 = 20 \text{ Volts}$$



2b) Repeat (a) for the currents at both ends of the line.

$$t = \frac{d}{v} = \frac{150}{300 \text{ m}/\mu\text{s}} = .5 \mu\text{s}$$
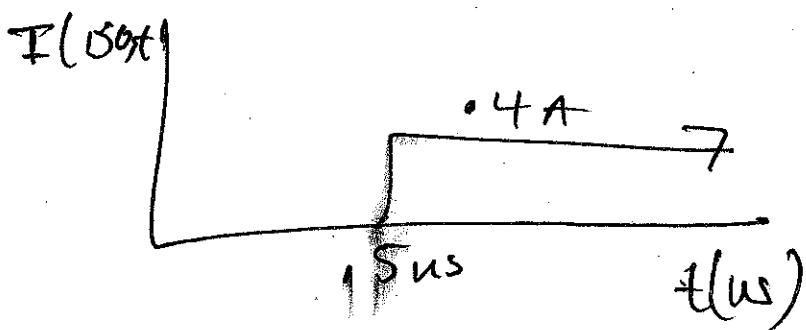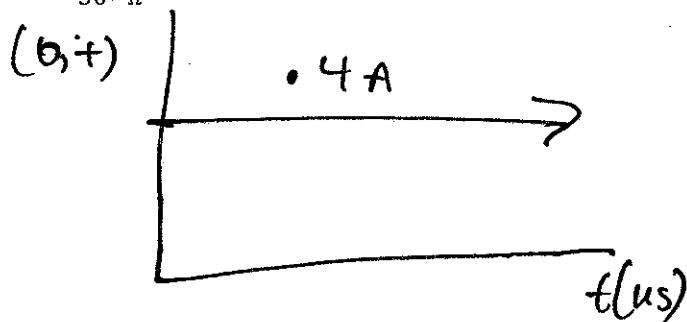
$$I = \frac{20 \text{ Volts}}{50 - \Omega} = .4 \text{ Amps}$$





Mohammed Islam Homework Chapter 2

3a) For the circuit of Fig. P2-3, plot the voltages at both ends of the line.

$$\Gamma_1 = \frac{R_1 - R_0}{R_0 + R_1} = \frac{50 - 50}{50 + 50} = \frac{0}{100} = 0$$

$$\Gamma_2 = \frac{R_2 - R_0}{R_2 + R_0} = \frac{30 - 50}{30 + 50} = \frac{-20}{80} = \frac{-1}{4}$$

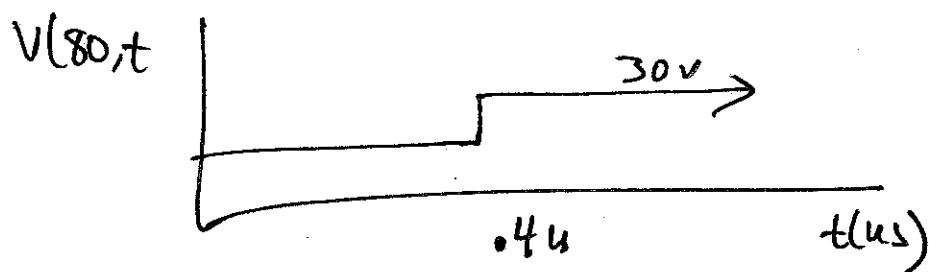
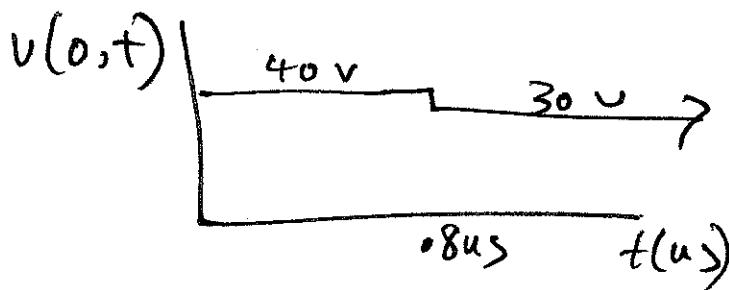
$$\left( \frac{R_0}{R_0 + R_1} \right) * E = \left( \frac{50}{50 + 50} \right) * 80 = 40 \text{ Volts}$$



3b) Repeat (a) for the currents at both ends of the line.

$$t = \frac{d}{v} = \frac{80}{200 \text{ m/μs}} = .4 \text{ μs}$$
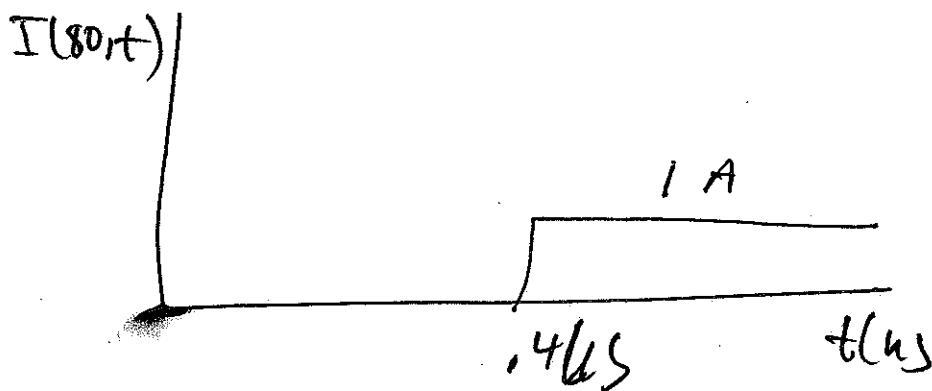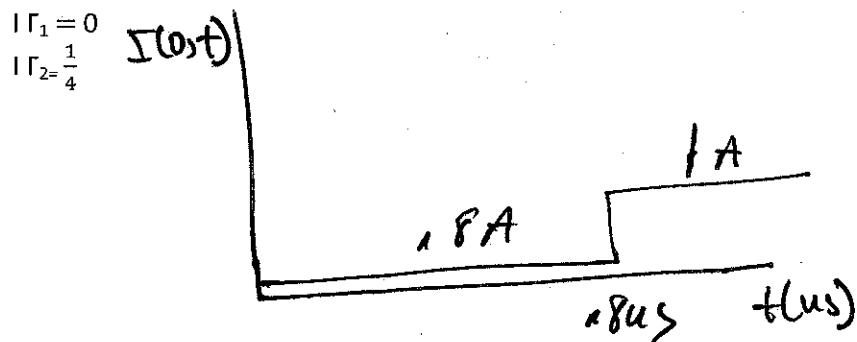
$$I = \frac{40 \text{ Volts}}{50 \Omega} = .8 \text{ Amps}$$





4a) For the circuit of Fig P2-4, plot the voltages at both ends of the line.

$$\Gamma_1 = \frac{R_1 - R_0}{R_0 + R_0} = \frac{300 - 300}{300 + 300} = \frac{0}{600} = 0$$

$$\Gamma_2 = \frac{R_2 - R_0}{R_2 + R_0} = \frac{450 - 300}{450 + 300} = \frac{150}{750} = .2$$
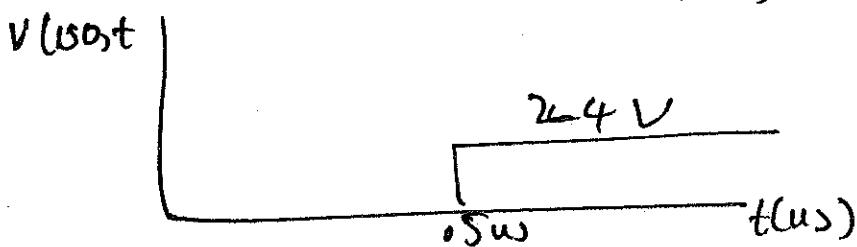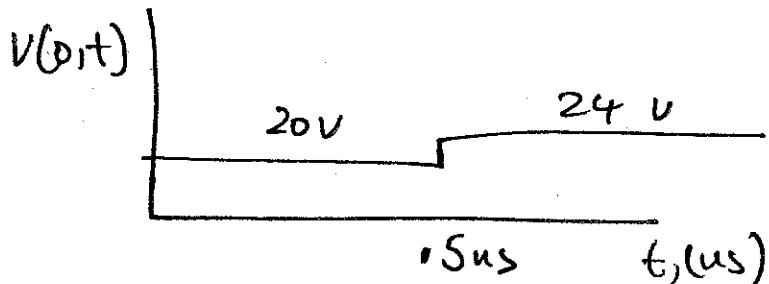
$$\left( \frac{R_0}{R_0 + R_1} \right) * E = \left( \frac{300}{300 + 300} \right) * 80 = 40 \text{ Volts}$$





b) Repeat (a) for the currents at both ends of the line.

$$t = \frac{d}{v} = \frac{150}{300 \text{ m}/\mu\text{s}} = .5 \mu\text{s}$$

$$I = \frac{20 \text{ Volts}}{300 - \Omega} = .067 \text{ Amps}$$

$$|\Gamma_1 = 0$$

$$|\Gamma_2 = -.2$$

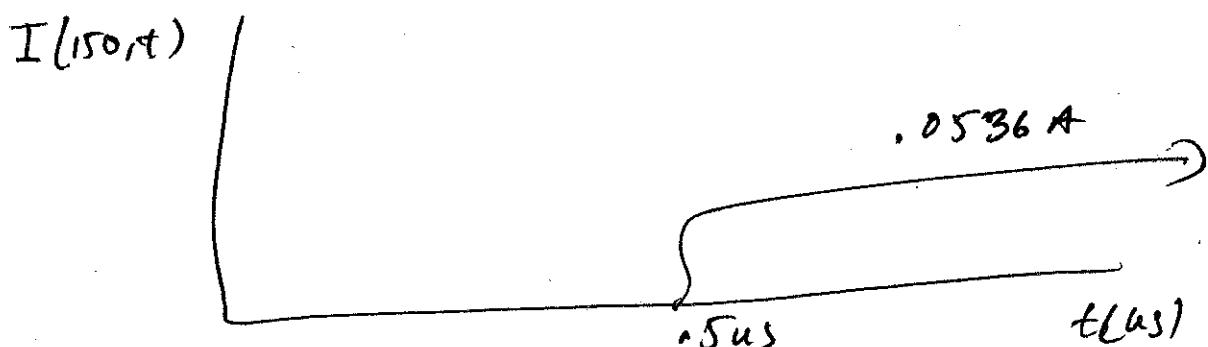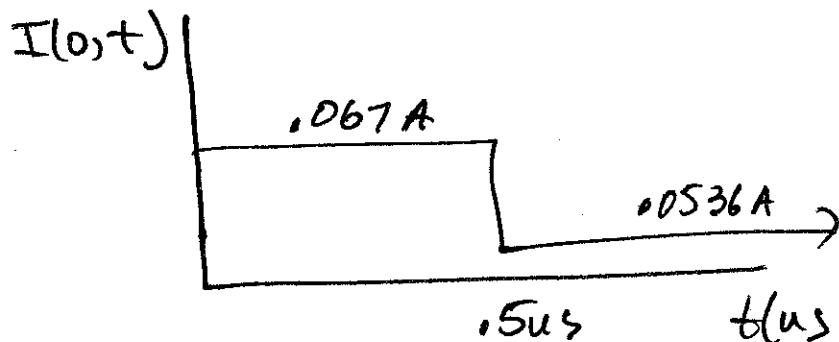



Mohammed Islam Homework Chapter 2

5a) For the circuit of Fig. P2-5, plot the voltages at both ends of the line.

$$\Gamma_1 = \frac{R_1 - R_0}{R_0 + R_0} = \frac{150 - 50}{150 + 50} = \frac{100}{200} = .5$$

$$\Gamma_2 = \frac{R_2 - R_0}{R_2 + R_0} = \frac{12.5 - 50}{12.5 + 50} = \frac{-37.5}{62.5} = -.6$$

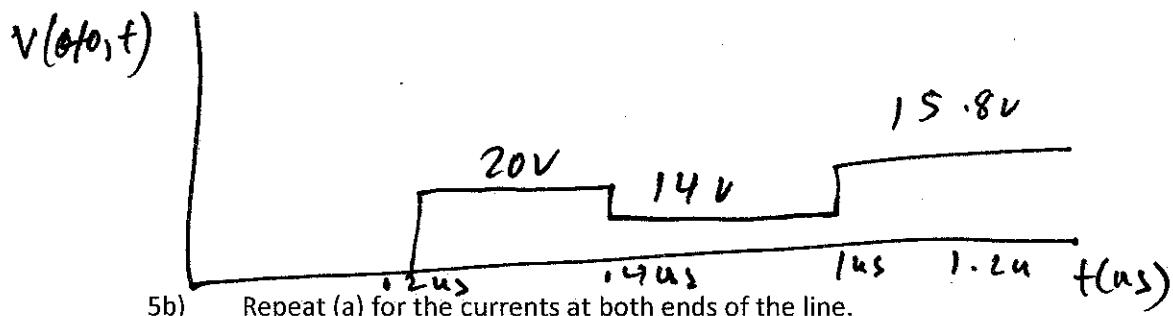
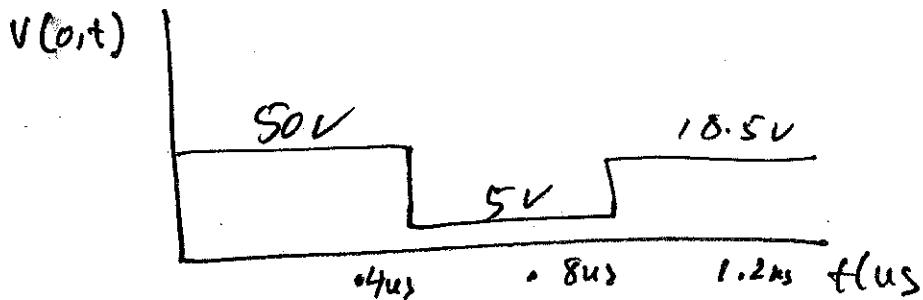
$$\left( \frac{R_0}{R_0 + R_1} \right) * E = \left( \frac{50}{50 + 150} \right) * 200 = 50 \text{ Volts}$$



5b) Repeat (a) for the currents at both ends of the line.

$$t = \frac{d}{v} = \frac{40}{200 \text{ m}/\mu\text{s}} = .2 \mu\text{s}$$
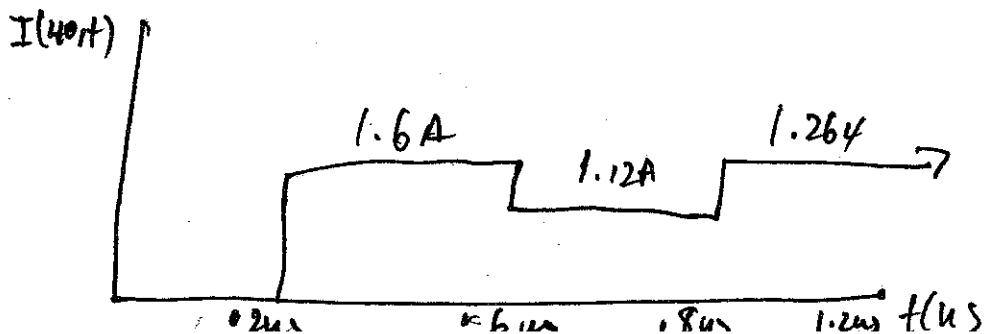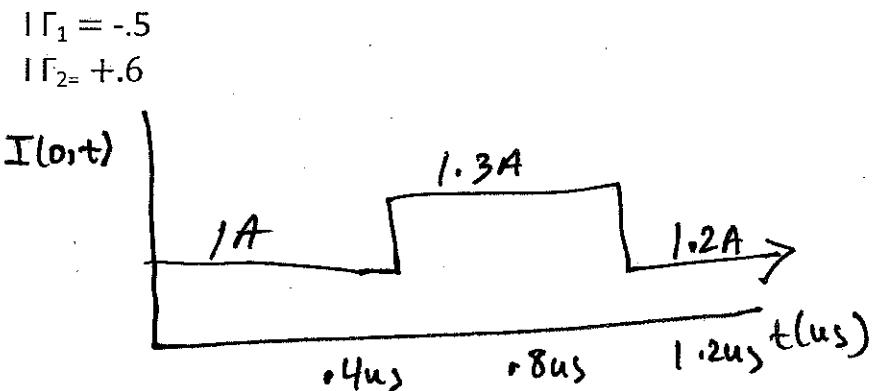
$$I = \frac{20 \text{ Volts}}{300 \Omega} = .067 \text{ Amps}$$





- 6a) For the circuit of Fig. P2-6, plot the voltages at both ends of the line.

$$\Gamma_1 = \frac{R_1 - R_0}{R_0 + R_0} = \frac{25 - 75}{25 + 75} = \frac{-50}{100} = -.5$$

$$\Gamma_2 = \frac{R_2 - R_0}{R_2 + R_0} = \frac{175 - 75}{175 + 75} = \frac{100}{250} = .4$$

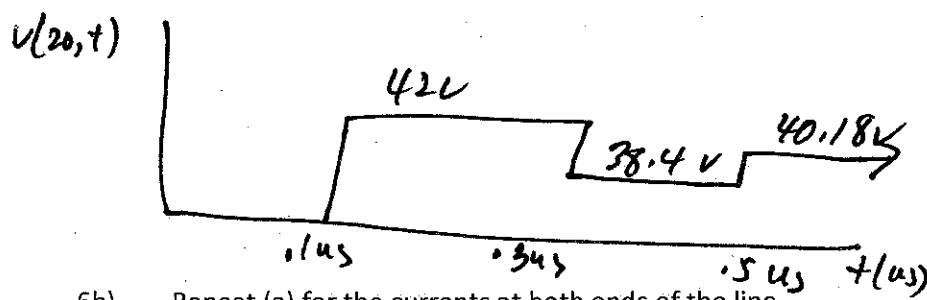
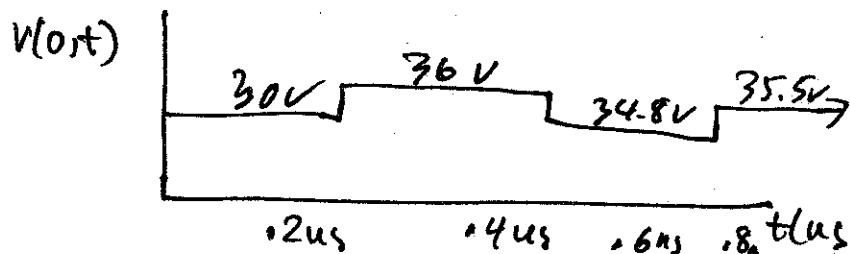
$$\left( \frac{R_0}{R_0 + R_1} \right) * E = \left( \frac{75}{75 + 25} \right) * 40 = 30 \text{ Volts}$$



- 6b) Repeat (a) for the currents at both ends of the line.



$$t = \frac{d}{v} = \frac{20}{200 \text{ m/μs}} = .1 \text{ μs}$$
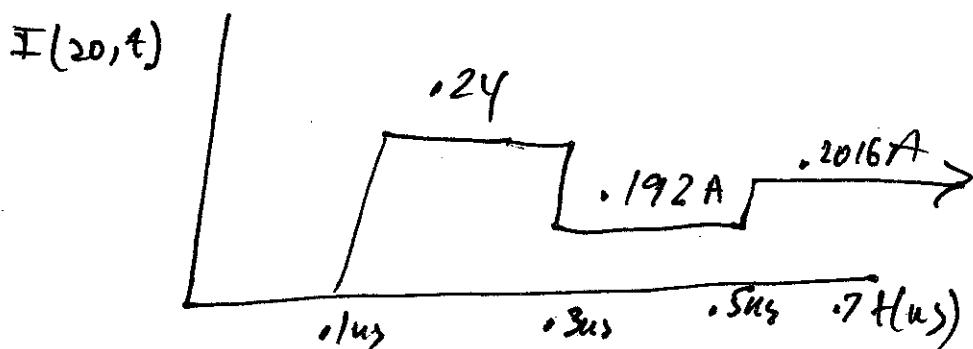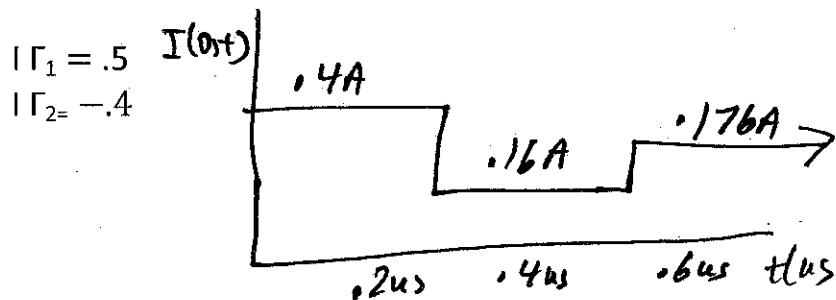
$$I = \frac{30 \text{ Volts}}{75 \Omega} = .4 \text{ Amps}$$





7) Assume in the circuit of Problem 2-3 (Fig. P2-3) that the 80-V dc source is replaced by an 80-V pulse of width 0.1  $\mu$ s starting at  $t=0$ .

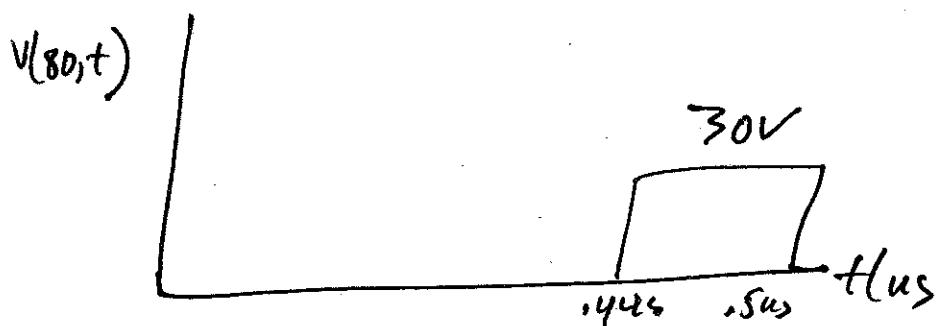
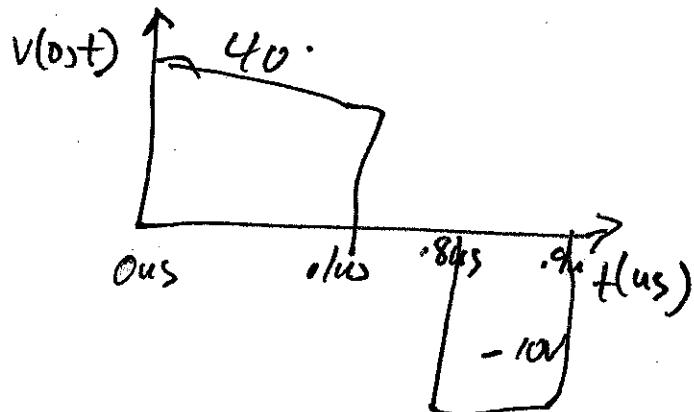
a) Plot the voltages at the two ends of the line.



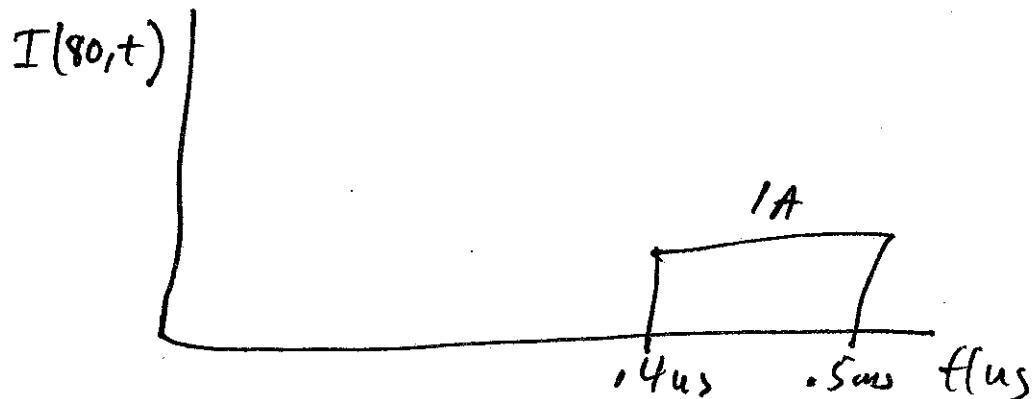
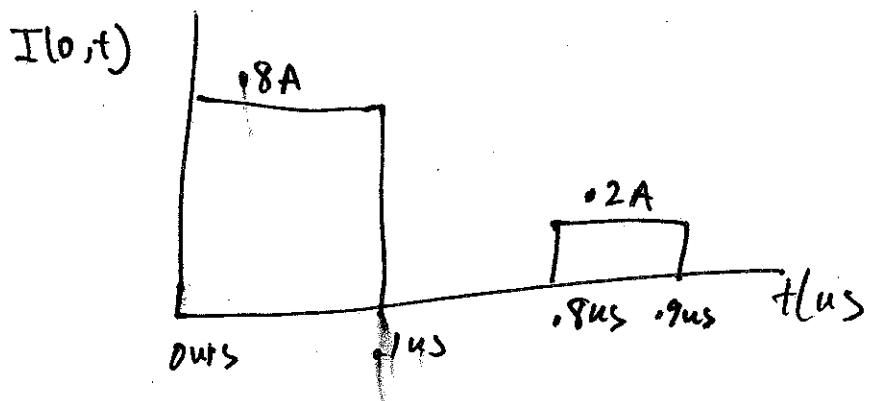
b) Plot the currents at the two ends of the line.



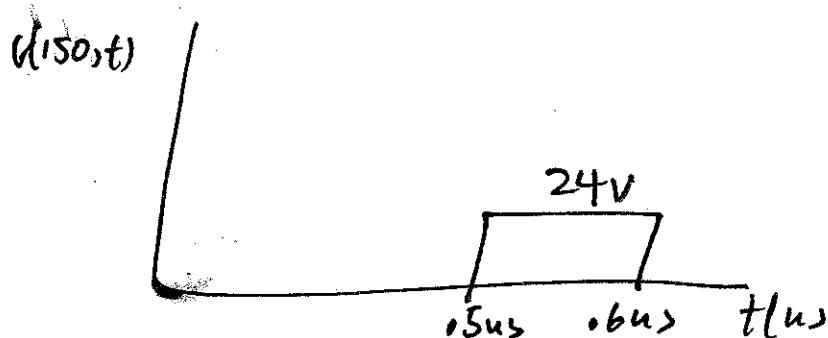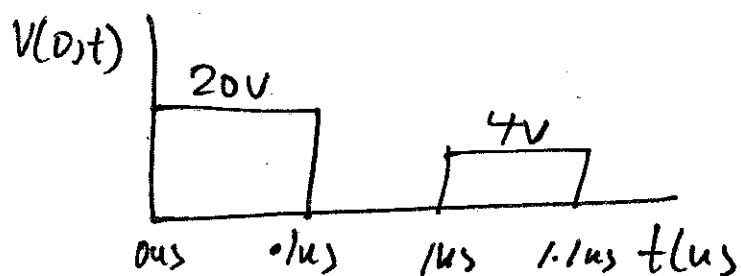- 8) Assume in the circuit of Problem 2-4 (Fig. P2-4) that the 40-V dc source is replaced by an 40-V pulse of width 0.1  $\mu$ s starting at  $t=0$ .
- a) Plot the voltages at the two ends of the line.



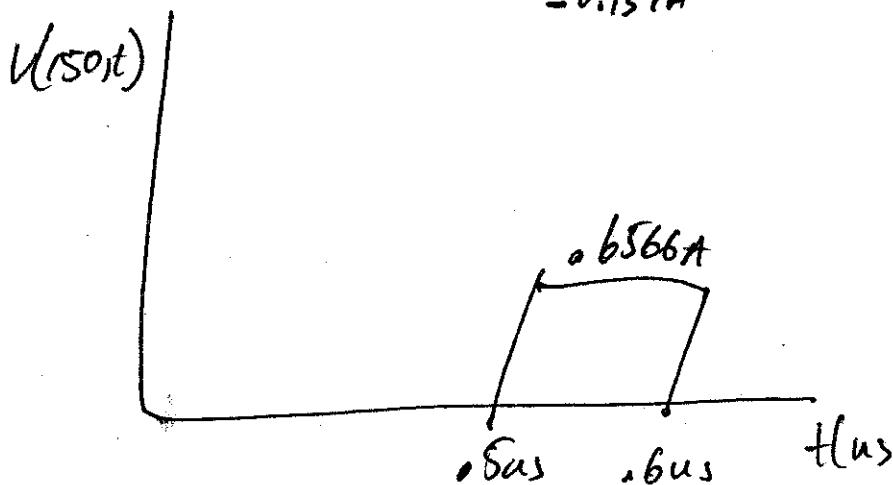
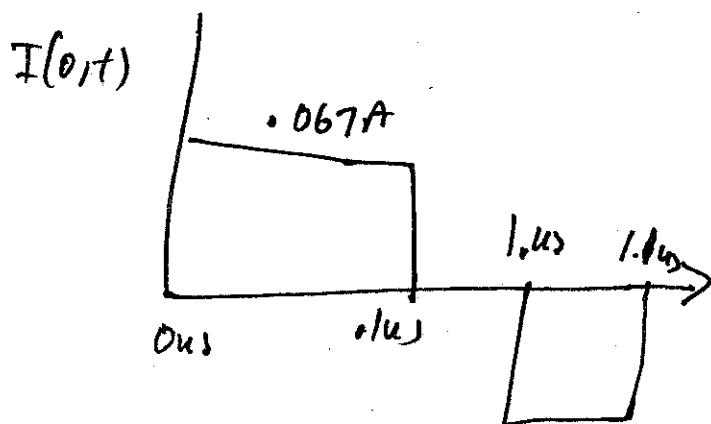
- b) Plot the currents at the two ends of the line.





Mohammed Islam Homework Chapter 2

9) Assume in the circuit of Problem 2-5 (Fig. P2-5) that the 200-V dc source is replaced by an 200-V pulse of width 0.1  $\mu$ s starting at  $t=0$ .

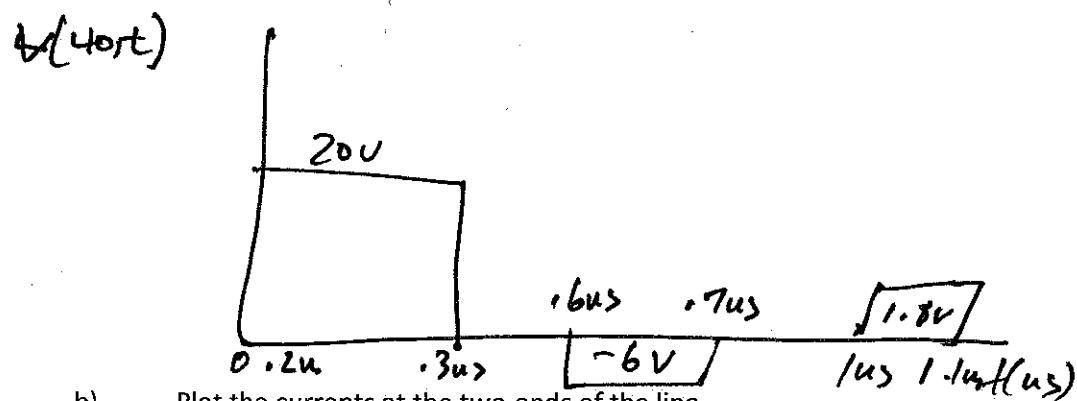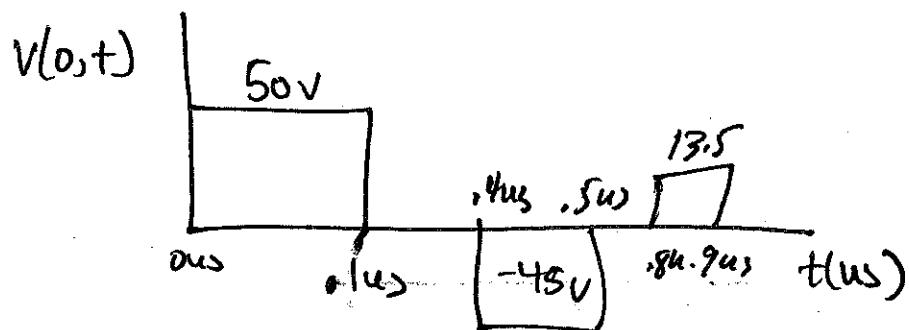a) Plot the voltages at the two ends of the line.





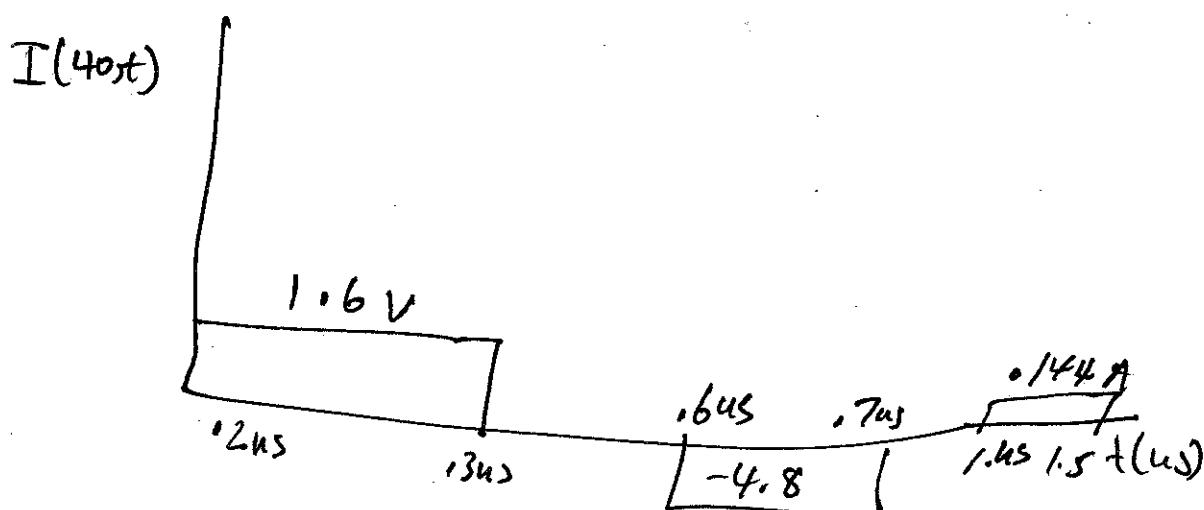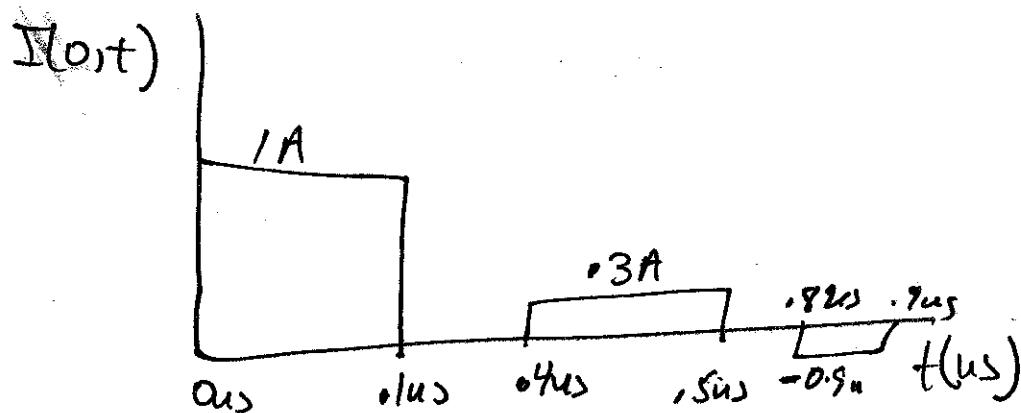b) Plot the currents at the two ends of the line.





- 10) Assume in the circuit of Problem 2-6 (Fig. P2-6) that the 40-V dc source is replaced by an 40-V pulse of width 0.1  $\mu$ s starting at t=0.

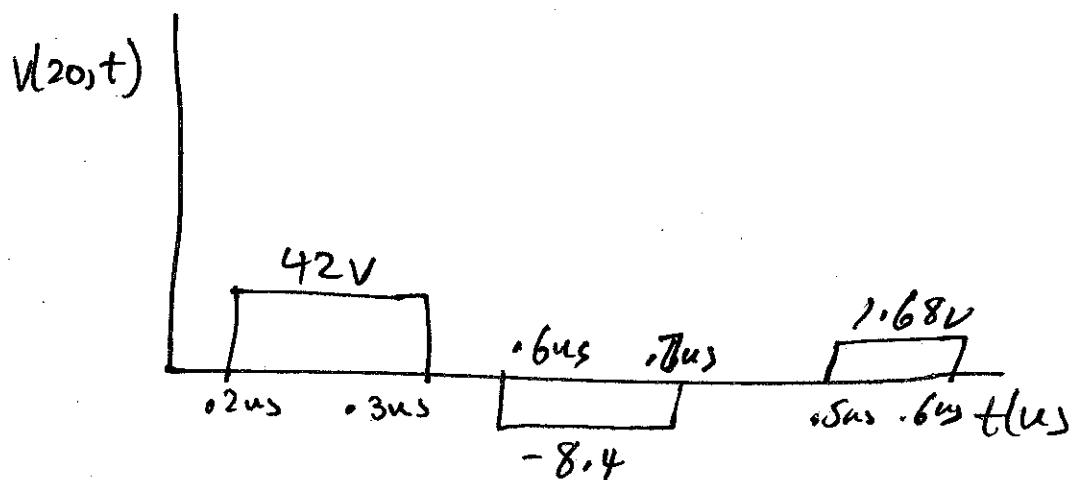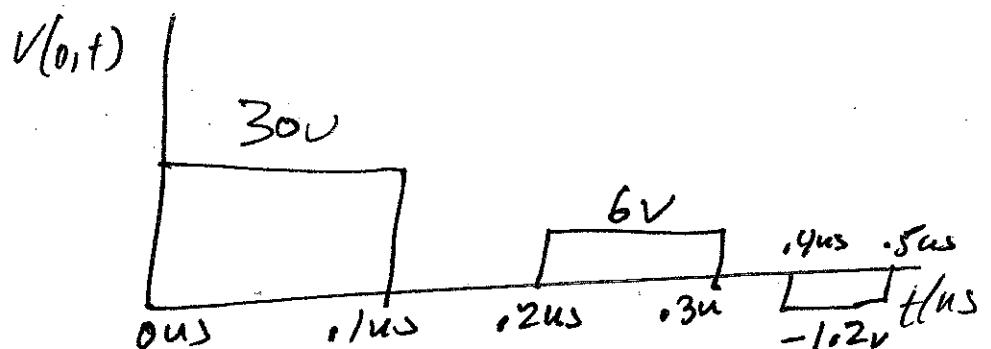a) Plot the voltages at the two ends of the line.



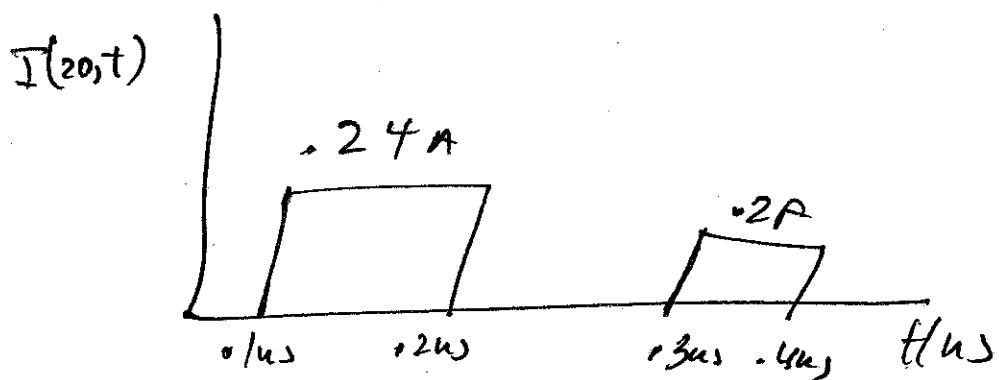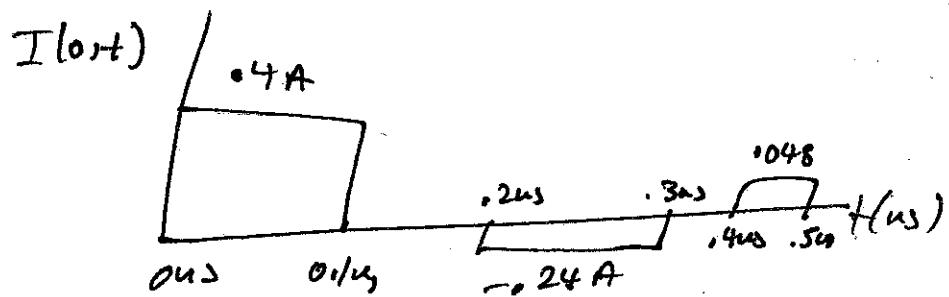b) Plot the currents at the two ends of the line.




Mohammed Islam Homework Chapter 2

- 11) For the circuit of Fig. P 2-11, plot the voltage  $v(0,t)$ .

$$\Gamma_1 = \frac{R_1 - R_0}{R_0 + R_0} = \frac{50 - 50}{50 + 50} = 0$$

$$\Gamma_2 = \frac{R_2 - R_0}{R_2 + R_0} = \frac{0 - 50}{0 + 50} = -1$$
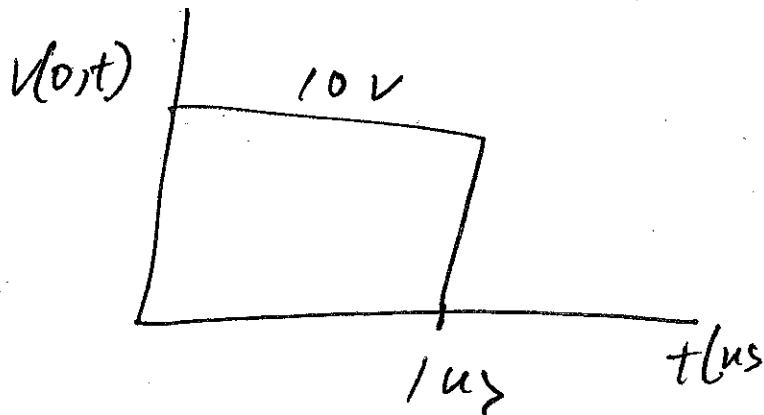
$$t = \frac{d}{v} = \frac{100}{200 \text{ m}/\mu\text{s}} = .5 \mu\text{s}$$




- 12) For the circuit of Fig. P2-12, plot the voltage  $v(0,t)$ ,

$$\Gamma_1 = \frac{R_1 - R_0}{R_0 + R_0} = \frac{75 - 75}{75 + 75} = 0$$

$$\Gamma_2 = \frac{R_2 - R_0}{R_2 + R_0} = \frac{0 - 75}{0 + 75} = -1$$
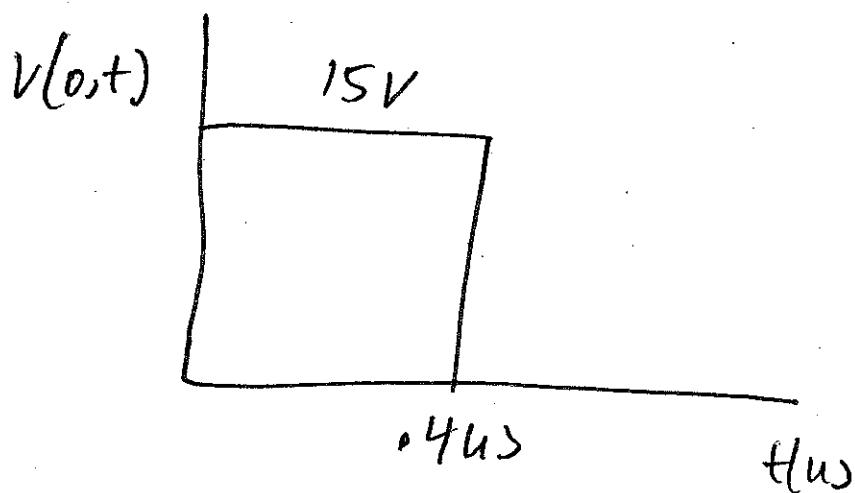
$$t = \frac{d}{v} = \frac{40}{200 \text{ m}/\mu\text{s}} = .20 \mu\text{s}$$



Mohammed Islam Homework Chapter 2


- 13) For the circuit of Fig. P2-13, plot the voltage  $v(0,t)$ .

$$\Gamma_1 = \frac{R_1 - R_0}{R_0 + R_0} = \frac{50 - 50}{50 + 50} = 0$$

$$\Gamma_2 = 1$$

$$t = \frac{d}{v} = \frac{200}{200 \text{ m}/\mu\text{s}} = 1 \mu\text{s}$$

$v(0,t)$

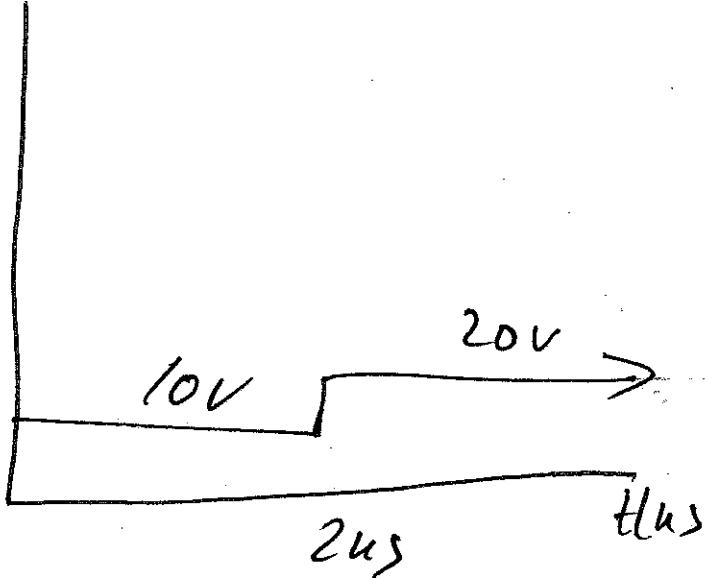


- 14) For the circuit of Fig. P2-14, plot the voltage  $v(0,t)$ .

$$\Gamma_1 = \frac{R_1 - R_0}{R_0 + R_0} = \frac{75 - 75}{75 + 75} = 0$$

$$\Gamma_2 = 1$$


$$t = \frac{d}{v} = \frac{80}{200 \text{ m}/\mu\text{s}} = .4 \mu\text{s}$$

$v(0,t)$

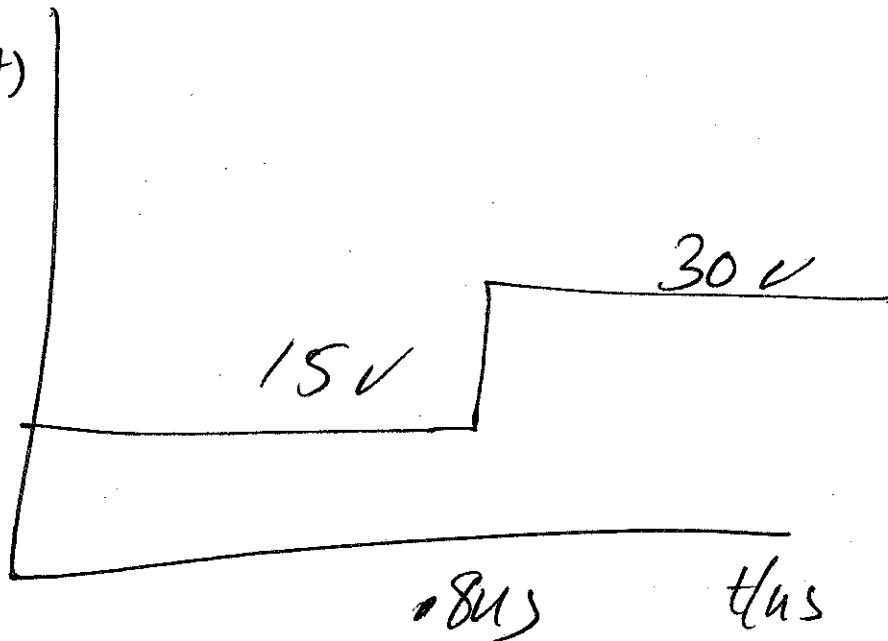


Mohammed Islam Homework Chapter 2

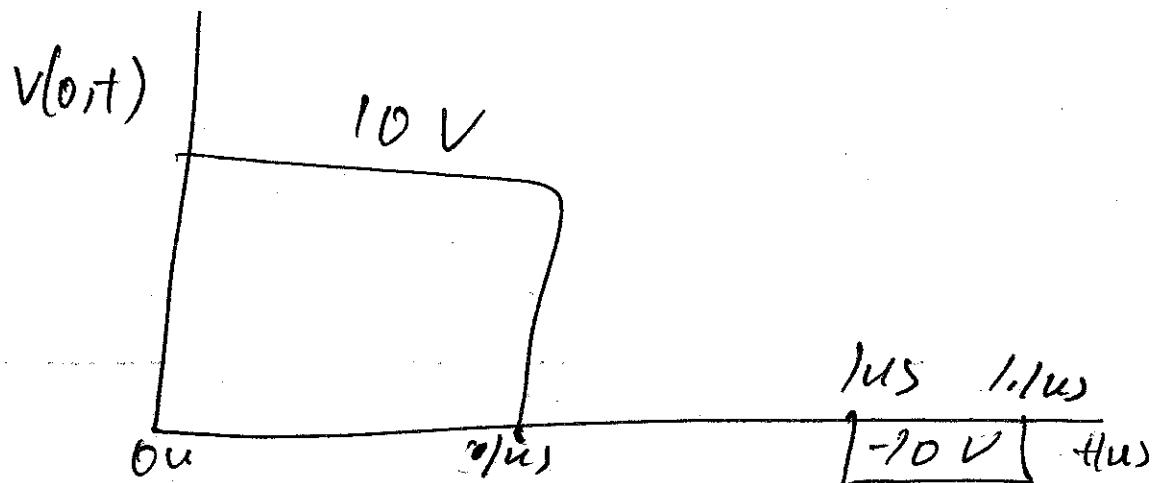
- 15) For the circuit of Problem 2-11 (Fig. P2-11), assume that the 20-V dc source is replaced by a 20-V pulse of width 0.1  $\mu$ s starting at t=0. Plot the voltage v(0,t).



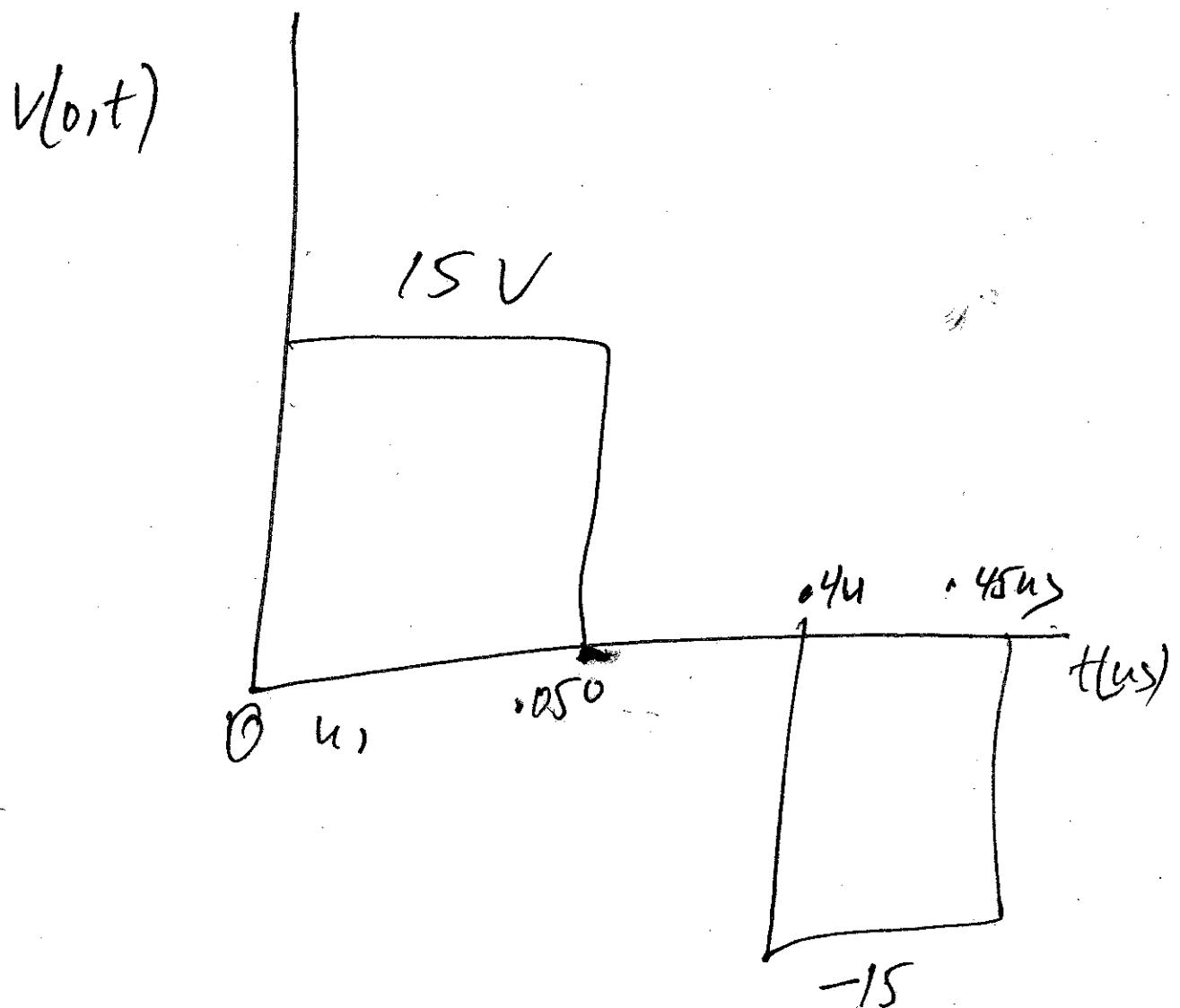
- 16) For the circuit of Problem 2-12 (Fig. P2-12), assume that the 30-V dc source is replaced by a 30-V pulse of width 50 ns starting at t=0. Plot the voltage v(0,t).



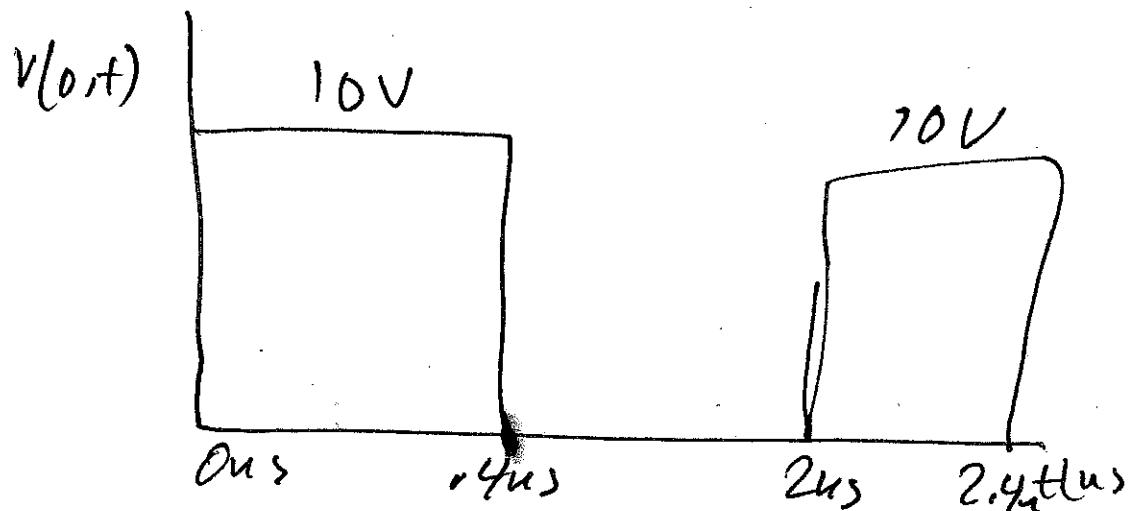- 17) For the circuit of Problem 2-13 (Fig. P2-13), assume that the 20-V dc source is replaced by a 20-V pulse width 0.4  $\mu$ s starting at t=0. Plot the voltage v(0,t).



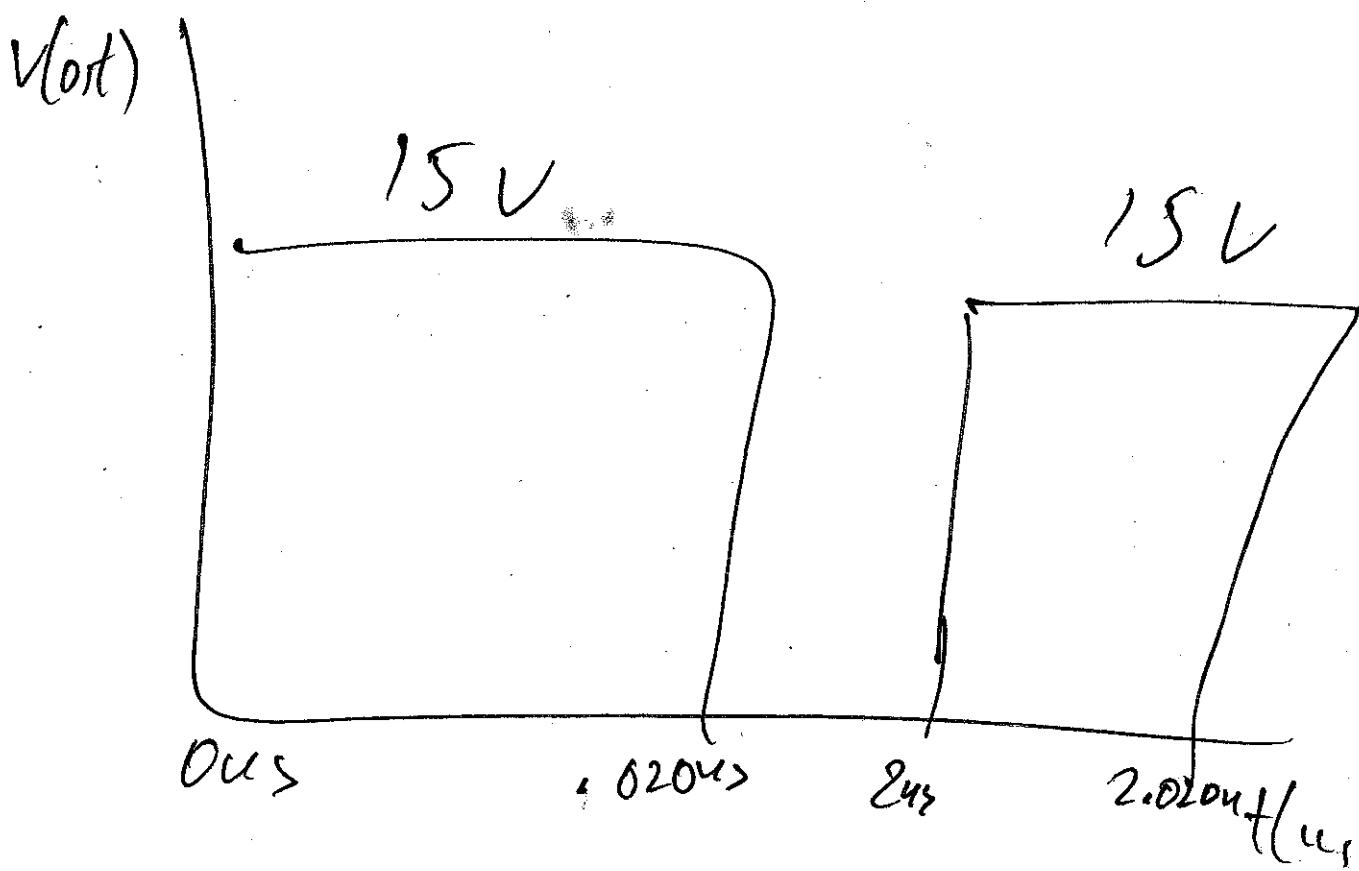- 18) For the circuit of Problem 2-14 (Fig. P2-14), assume that the 30-V dc source is replaced by a 30-V pulse width 20 ns starting at t=0. Plot the voltage v(0,t).




Mohammed Islam Homework Chapter 2

- 19) For the circuit of Fig. P2-19, plot the voltage  $v(0,t)$ .

$$\Gamma_1 = \frac{R_1 - R_0}{R_0 + R_1} = \frac{150 - 50}{50 + 150} = \frac{100}{200} = .5$$

$$\left( \frac{R_0}{R_0 + R_1} \right) * E = \left( \frac{50}{50 + 150} \right) * 40 = 10 \text{ Volts}$$
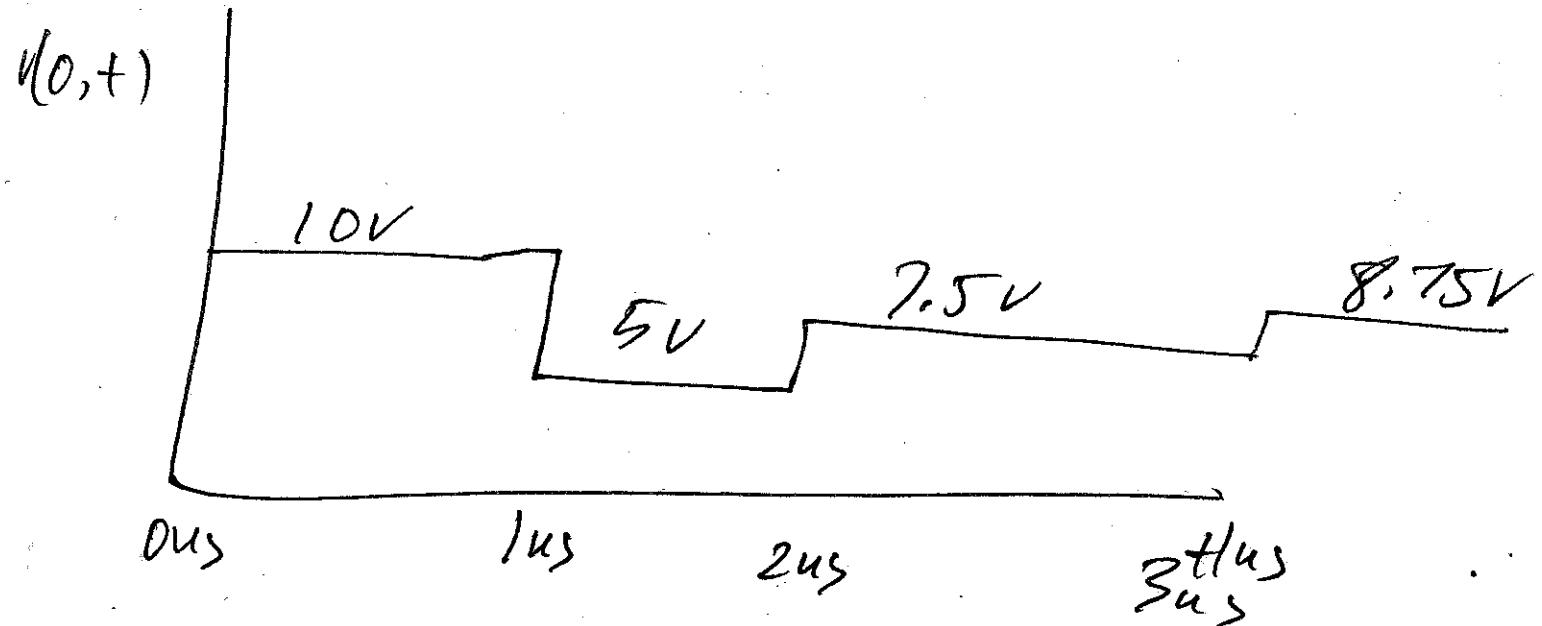
$$t = \frac{d}{v} = \frac{100}{2 * 10^8 \text{ m}/\mu\text{s}} = .5 \mu\text{s}$$




- 20) For the circuit of Fig. P2-20, plot the voltage  $v(0,t)$ .


$$\Gamma_1 = \frac{R_1 - R_0}{R_0 + R_1} = \frac{25 - 75}{25 + 75} = \frac{-50}{100} = -.2$$

$$\left( \frac{R_0}{R_0 + R_1} \right) * E = \left( \frac{75}{75 + 25} \right) * 40 = 30 \text{ Volts}$$

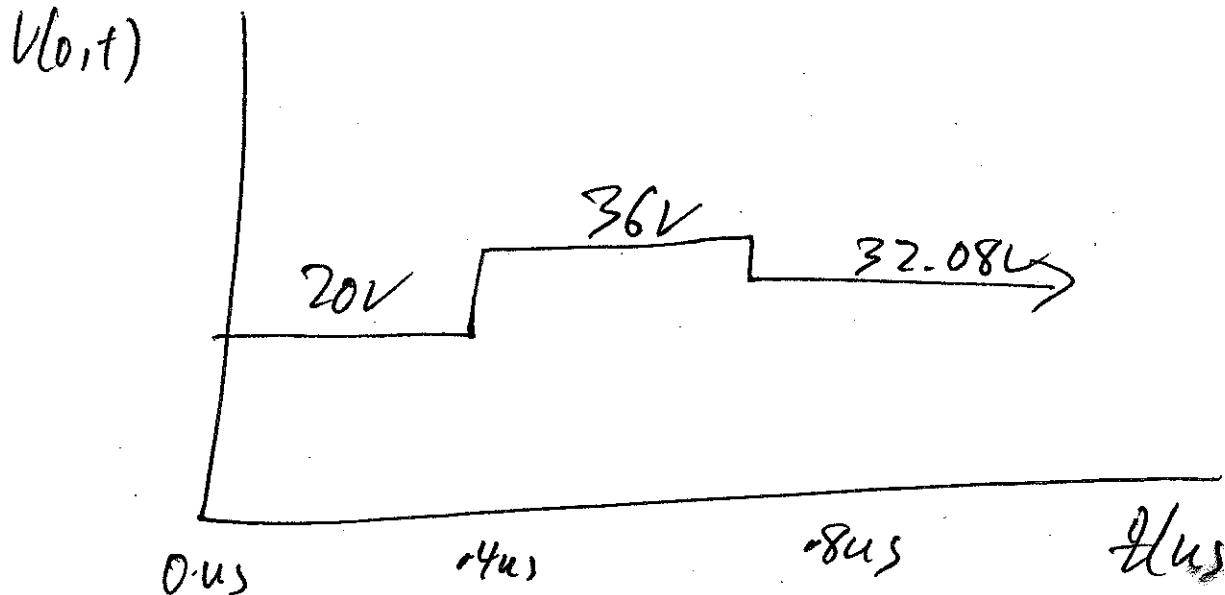
$$t = \frac{d}{v} = \frac{40}{2 * 10^8 \text{ m}/\mu\text{s}} = .2 \mu\text{s}$$



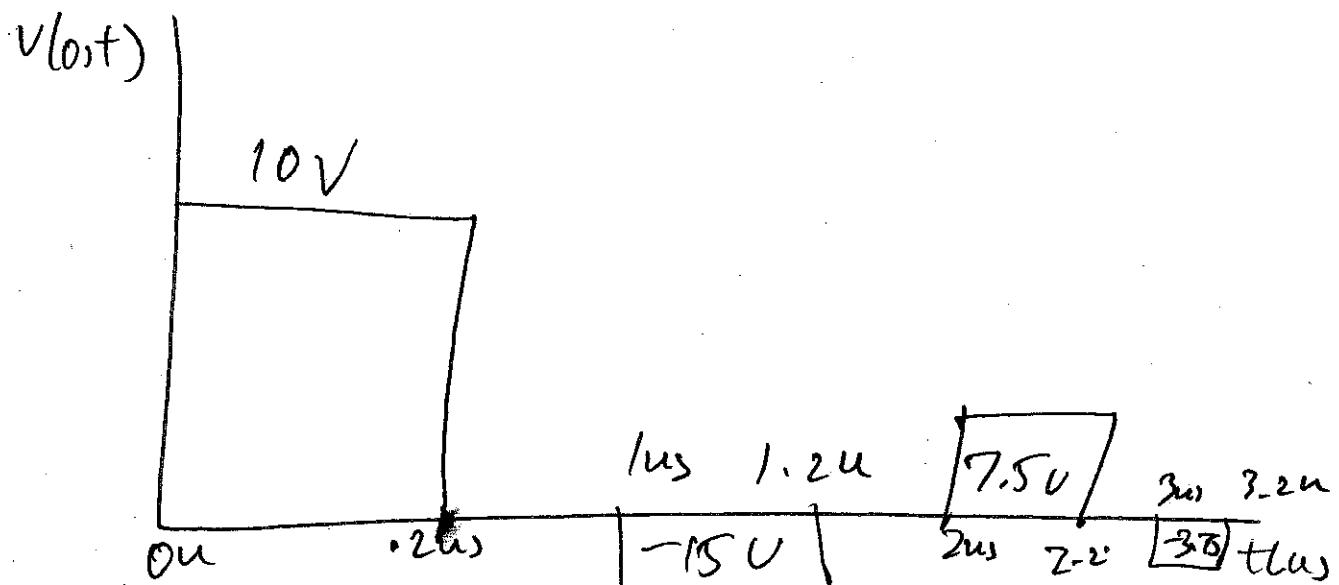- 21) For the circuit of Problem 2-19 (Fig. P2-19), assume that the 40-V dc source is replaced by a 40-V pulse width  $0.2\mu s$  starting at  $t=0$ . Plot the voltage  $v(0,t)$ .



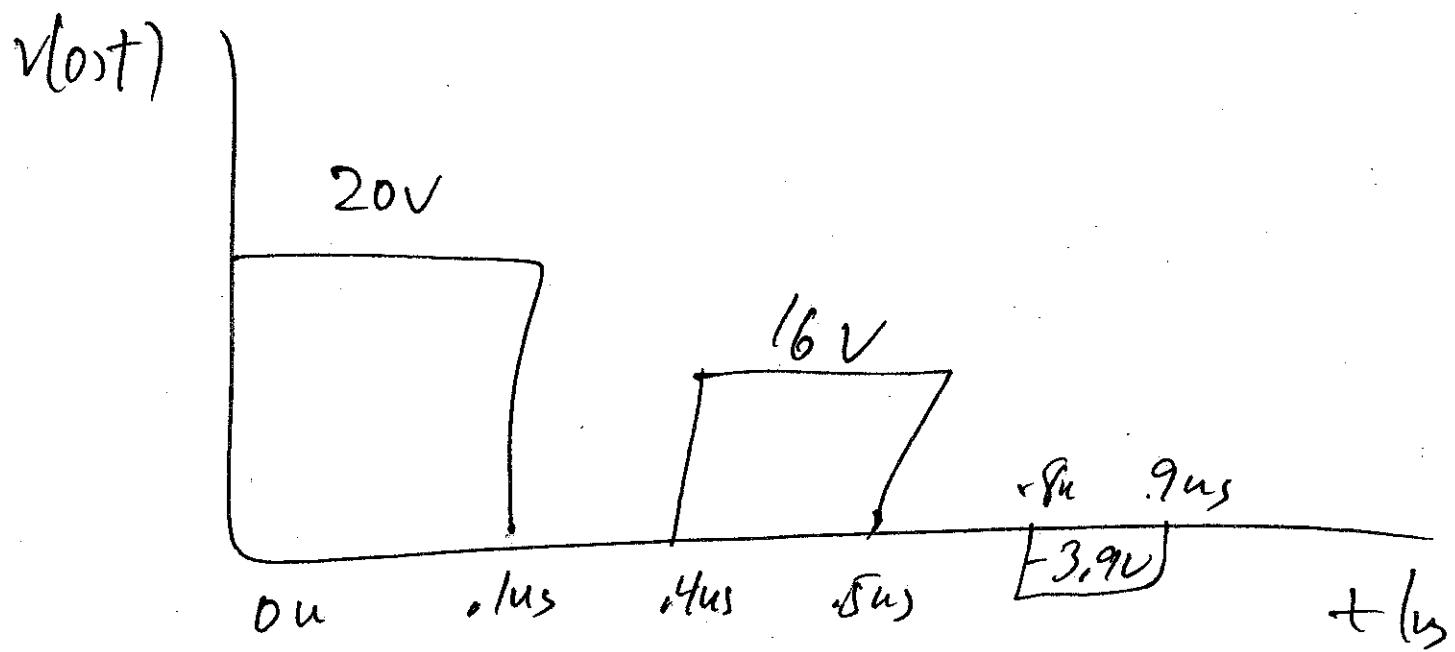- 22) For the circuit of Problem 2-20 (Fig. P2-20), assume that the 40-V dc source is replaced by a 40-V pulse width  $100\text{ ns}$  starting at  $t=0$ . Plot the voltage  $v(0,t)$ .



Mohammed Islam Homework Chapter 2

23) A 50- $\Omega$  line is terminated in an unknown load resistance  $R_2$ . The line is excited by a pulse generator with an output impedance of 50  $\Omega$  resistive. The waveform across the input to the line is shown in Fig. P2-23, and the velocity of propagation is 200 m/ $\mu$ s.

a) Determine the length of the line.

$$d=v*t_1 = 200 \frac{m}{\mu s} * (.25 * 10^6 \mu s) = 50 m$$

b) Determine the value of the load resistance.

$$r_2 = \frac{24}{40} = .6$$

$$R_2 = \left( \frac{1+r_2}{1-r_2} \right) * R_0 = \left( \frac{1+.6}{1-.6} \right) * 50 = 200 \Omega$$

24) Repeat the analysis of Problem 2-23 if the voltage across the input is as shown in Fig. P2-24.

$$d=v*t_1 = 200 \frac{m}{\mu s} * (1.2 * 10^6 \mu s) = 240 m$$

$$r_2 = \frac{-8}{40} = -.2$$

$$R_2 = \left( \frac{1+r_2}{1-r_2} \right) * R_0 = \left( \frac{1+(-.2)}{1-(-.2)} \right) * 50 = 75 \Omega$$