

Peter Franco  
 TCET 2220  
 Homework 4

**(3-1) A traveling wave of current in milliamperes is given by with t in seconds and x in meters. Determine the following:**

$$i = 8 \sin(2\pi \times 10^6 t - 0.025x)$$

**(a) Direction of propagation**

Since the argument of the function has the difference between the time and displacement terms, the wave is traveling in the positive x-direction

**(b) Peak value**

$$I_{\text{peak}} = 8 \text{ A}$$

**(c) Angular frequency**

$$2 \times 10^6 \text{ rad/sec}$$

**(d) Phase constant**

$$= 0.025 \text{ rad/m}$$

**(e) Cyclic frequency**

$$F = \frac{2}{2} = \frac{2 \times 10^6}{2} = 1 \text{ MHz}$$

**(f) Period**

$$T = \frac{1}{F} = \frac{1}{1 \text{ MHz}} = 1 \text{ us}$$

**(g) Wavelength**

$$= \frac{2}{0.025} = 251 \text{ meter}$$

**(h) Velocity of propagation**

$$V = F \times \lambda = 1 \text{ MHz} \times 251.2 \text{ m} = 251.2 \times 10^6 \text{ m/s}$$

**(3-2) A traveling wave of voltage in volts in given by**

$$v = 20 \sin(2\pi \times 10^6 t + 0.025x)$$

**with t in seconds and x in meters. Determine the following:**

**(a) Direction of propagation**

Since the argument of the function has the difference between the time and displacement terms, the wave is traveling in the negative x-direction

(b) Peak value

$$V_{\text{peak}} = 15 \text{ V}$$

(c) Angular frequency

$$10^3 \text{ rad/sec}$$

(d) Phase constant

$$= 0.35 \text{ rad/m}$$

(e) Cyclic frequency

$$F = \frac{10^3}{2\pi} = 15.9 \text{ MHz}$$

(f) Period

$$T = \frac{1}{F} = \frac{1}{15.9 \text{ MHz}} = 6.3 \times 10^{-8} \text{ s}$$

(g) Wavelength

$$= \frac{2\pi}{0.35} = 17.9 \text{ meter}$$

(h) Velocity of propagation

$$V = F \cdot \lambda = 15.9 \text{ MHz} \cdot 17.9 \text{ m} = 2.8 \times 10^3 \text{ m/s}$$

(3-3) A sinusoidal current with a peak value of 2 A and a frequency of 50 MHz is traveling in the positive x-direction with a velocity of  $2 \times 10^8 \text{ m/s}$ . Determine the following:

(a) Period

$$T = \frac{1}{F} = \frac{1}{50 \text{ MHz}} = 2 \times 10^{-8} \text{ s}$$

(b) Angular Frequency

$$2\pi \cdot 50 \text{ MHz} = 314 \times 10^3 \text{ rad/se}$$

(c) Phase constant

$$= \frac{314 \times 10^3}{2 \times 10^8} = 1.57 \text{ rad/m}$$

(d) Wavelength

$$= \frac{2\pi}{1.57} = 4 \text{ m}$$

(e) An equation for the current

$$v = 2 \cos(314 * 10^3 t - 1.57x)$$

(3-4) A sinusoidal voltage with a peak value of 25 V and a radian frequency of 20 Mrad/s is traveling in the negative x-direction with a velocity of  $3 * 10^8$  m/s. Determine the following:

(a) Cyclic frequency

$$F = \frac{\omega}{2\pi} = \frac{20 \text{ MHz}}{2} = 3.18 \text{ MHz}$$

(b) Period

$$T = \frac{1}{F} = \frac{1}{3.18 \text{ MHz}} = 3.14 * 10^{-7} \text{ s}$$

(c) Phase constant

$$k = \frac{\omega}{v} = \frac{20 * 10^6}{3 * 10^8} = 0.0667 \text{ rad/m}$$

(d) Wavelength

$$\lambda = \frac{2\pi}{k} = \frac{2}{0.0667} = 106.67 \text{ m}$$

(e) An equation for the current

$$V = 25 \cos(20 * 10^6 t + 0.0667x)$$

(3-5) Consider the current traveling wave of Problem 3-1. Determine the following:

(a) A fixed phasor representation in peak units as either  $\tilde{I}(t)$  or  $\tilde{I}(x)$  (You decide which label is appropriate.)

$$\tilde{I}(t) = 8 \angle 0^\circ \text{ A}$$

(b) The corresponding distance-varying phasor  $\tilde{I}(x)$  in peak units

$$\tilde{I}(x) = 8 e^{-j0.025x} \text{ A}$$

(c) The wave of the distances-varying phasor at  $x = 100$  m.

$$\tilde{I}(100) = 8 \angle -0.025(100) = 8 \angle -2.5^\circ$$

(3-6) Consider the voltage traveling wave of Problem 3-2. Determine the following:

(a) A fixed phasor representation in peak units as either  $\tilde{V}(t)$  or  $\tilde{V}(x)$  (You decide which label is appropriate.)

$$\tilde{V}(t) = 15 \angle 0^\circ \text{ V}$$

(b) The corresponding distance-varying phasor  $\tilde{V}(x)$  in peak units.

$$V_x = 15 \angle 0.35^\circ$$

(c) The wave of the distances-varying phasor at  $x = 4$  m

$$V_{4m} = 15 \angle 0.35^\circ * 4 = 15 \angle 1.40^\circ$$

(3-7) Repeat the analysis of Problem 3-5 if the current of Problem 3-1 has a fixed phase shift such that it is described by

$$i = 8 \cos(2\pi * 10^8 t - 2\pi x + \pi/2)$$

(a) A fixed phasor representation in peak units as either  $\tilde{I}$  or  $\hat{I}$  (You decide which label is appropriate.)

$$\tilde{I} = 8 \angle \pi/2 = 8 \angle 1.57$$

(b) The corresponding distance-varying phasor  $\tilde{I}(x)$  in peak units

$$\tilde{I}(x) = \tilde{I} * e^{-j2\pi x} = (8 \angle 1.57) * (1 \angle -0.025x) = 8 \angle 1.57 - 0.025x$$

(c) The wave of the distances-varying phasor at  $x = 100$  m.

$$\tilde{I}_{100m} = 8 \angle 1.57 - 0.025 * 100 = 8 \angle -1.0^\circ$$

(3-8) Repeat the analysis of Problem 3-6 if the voltage of Problem 3-2 has a fixed phase shift such that it is described by

$$v = 15 \cos(2\pi * 10^8 t + 2\pi x + \pi/3)$$

(a) A fixed phasor representation in peak units as either  $\tilde{V}$  or  $\hat{V}$  (You decide which label is appropriate.)

$$\tilde{V} = 15 \angle \pi/3 = 15 \angle \frac{\pi}{3}$$

(b) The corresponding distance-varying phasor  $\tilde{V}(x)$  in peak units.

$$V_x = 15 \angle \frac{\pi}{3} * 1 \angle 0.35x = 15 \angle \frac{\pi}{3} + 0.35x$$

(c) The wave of the distances-varying phasor at  $x = 4$  m

$$V_{4m} = 15 \angle \frac{\pi}{3} + 1.40^\circ$$

(3-9) Redefine the fixed phasor of Problem 3-5 so that the phasor magnitude is expressed in rms units, and determine the average power dissipated in a 50- $\Omega$  resistance.

$$I_{22} = I_{11} * 0.707 = 8 \text{ A} * 0.707 = 5.66 \text{ A}$$

$$P = I_{22} * R = (5.66 \text{ A}) * (50 \Omega) = 1,601.78 \text{ W}$$

**(3-10) Redefine the fixed phasor of Problem 3-6 so that the phasor magnitude is expressed in rms units, and determine the average power dissipated in a 75- $\Omega$  resistance.**

$$V_{22} = V_{11} * 0.707 = 15 \text{ V} * 0.707 = 10.61 \text{ V}$$

$$P = \frac{V_{22}^2}{R} = \frac{10.61^2 \text{ V}}{75} = 1.50 \text{ W}$$

**(3-11) Redefine the fixed phasor of Problem 3-7 so that the phasor magnitude is expressed in rms units. Would the power dissipated in a 50- $\Omega$  resistance be the same as in Problem 3-9?**

$$I_{22} = I_{11} * 0.707 = 8 \text{ A} * 0.707 = 5.66 \angle 1.5 \text{ A}$$

$$P = I_{22}^2 * R = (5.66 \text{ A})^2 * (50 \Omega) = 1,601.78 \text{ W}$$

Yes they are the same.

**(3-12) Redefine the fixed phasor of Problem 3-8 so that the phasor magnitude is expressed in rms units. Would the power dissipated in a 75- $\Omega$  resistance be the same as in Problem 3-10?**

$$V_{22} = V_{11} * 0.707 = 15 \text{ V} * 0.707 = 10.61 \text{ V}$$

$$P = \frac{V_{22}^2}{R} = \frac{10.61^2 \text{ V}}{75} = 1.50 \text{ W}$$

Yes they are the same.

**(3-13) Under steady-state ac conditions, the forward current wave on a certain lossless 50- $\Omega$  line is  $i_{f1} = 2 \angle 0^\circ \text{ A}$ . Determine the voltage forward wave.**

$$V_{f1} = 2 \angle 0^\circ \text{ A} * (50 \Omega) = 100 \angle 0^\circ \text{ V}$$

**(3-14) Under steady-state ac conditions, the forward current wave in 300- $\Omega$  lossless line is  $i_{f1} = 15 \angle 3^\circ \text{ A}$ . Determine the current forward wave.**

$$I_{f1} = \frac{V_{f1}}{R} = \frac{15 \angle 3^\circ}{50} = 300 \angle 3^\circ \text{ mA}$$

**(3-15) Under steady-state ac conditions, the reverse voltage wave on a lossless 50- $\Omega$  line is  $V_{r1} = 200 \angle 45^\circ \text{ V}$ . Determine the reverse current wave.**

$$I_{\text{ref}} = -\frac{V_{\text{ref}}}{Z_0} = -\frac{200 \angle 0}{50} = -4 \angle 0 \text{ A}$$

(3-16) Under steady-state ac conditions, the reverse current wave on a lossless 75- $\Omega$  line is  $I_{\text{ref}} = 2.7 \angle 0^\circ$ . Determine the reverse voltage wave.

$$V_{\text{ref}} = -Z_0 I_{\text{ref}} = (-0.5 \angle 2^\circ) * (2.7 \angle 0^\circ) = -37.5 \angle 0^\circ \text{ V}$$

(3-17) A table of specifications for one version of RG - 8/U 50- $\Omega$  coaxial cable indicates that the attenuation per 100 ft. at 50 MHz is 1.2 dB. At this frequency, determine the following:

(a) Attenuation factor in decibel per foot

$$\frac{1.2 \text{ dB}}{100} = 0.012 \text{ dB/foot}$$

(b) Attenuation factor in nepers per foot

$$\frac{0.012 \text{ dB}}{8.686} = 1.382 * 10^{-3} \text{ Np/ft}$$

For a length of 300 ft. determine the following:

(c) Total attenuation in decibel

$$L_{\text{dB}} = \alpha_{\text{dB}} * d = 0.012 * 300 = 3.6 \text{ dB}$$

(d) Total attenuation in nepers

$$L = \alpha * d = 1.3815 * 10^{-3} * 300 = 0.4145 \text{ nepers}$$

(e)  $V_{\text{ref}}/V_{\text{inc}}$  Ratio using both decibels and nepers for a single wave

$$\frac{V_{\text{ref}}}{V_{\text{inc}}} = e^{-L} = e^{-0.4145} = 0.6607$$

In terms of decibels, this ratio may be expressed as

$$\frac{V_{\text{ref}}}{V_{\text{inc}}} = 10^{-\frac{L_{\text{dB}}}{20}} = 10^{-\frac{3.6}{20}} = 10^{-0.18} = 0.6607$$

(3-18) A transmission line has an attenuation of 0.05 dB/m. Determine the following:

(a) Attenuation factor in nepers/m

$$\alpha = \frac{0.05 \text{ dB}}{8.686} = \frac{0.05}{8.686} = 5.756 * 10^{-3} \text{ Np/m}$$

For a length of 400 m, determine the following:

(b) Total attenuation in decibel

$$L_{\text{dB}} = \alpha_{\text{dB}} * d = 0.05 * 400 = 20 \text{ dB}$$

(c) Total attenuation

$$L = \alpha d = 5.756 \times 10^{-3} \times 400 = 2.303 \text{ Np}$$

(d) / Ratio using both decibels and nepers for a single wave

$$\frac{V_2}{V_1} = e^{-L} = e^{-2.303} = 0.1$$

In term of decibles:

$$\frac{V_2}{V_1} = 10^{-\frac{L_{dB}}{20}} = 10^{-\frac{20}{20}} = 10^{-1} = 0.1$$

(3-19) A single-Frequency wave is propagating in one direction on a transmission line of length 200m. with an input rms voltage of 50 V, the output rms voltage is measured as 20 V. Determine the following:

(a) Total attenuation in decibel

$$L_{dB} = 20 \log_{10} \frac{V_1}{V_2} = 20 \log_{10} \frac{50}{20} = 7.959 \text{ dB}$$

(b) Total attenuation in nepers

$$L = \frac{L_{dB}}{8.686} = \frac{7.959}{8.686} = 0.9163 \text{ Np}$$

(c) Attenuation factor in decibel/meter

$$= \frac{L_{dB}}{d} = \frac{7.959}{200} = 0.03980 \text{ dB/m}$$

(d) Attenuation factor

$$= - = \frac{0.9163}{200} = 4.581 \times 10^{-3} /$$

(3-20) A single-Frequency wave is propagating in one direction on a transmission line of length 400m. The input power to the line is 40 W, and the output power is 12 W. Determine the following:

(a) Total attenuation in decibel

$$L_{dB} = 20 \log_{10} \frac{V_1}{V_2} = 20 \log_{10} \frac{40}{12} = 5.229 \text{ dB}$$

(b) Total attenuation

$$L = \frac{L_{dB}}{8.686} = \frac{5.229}{8.686} = 0.6020 \text{ Np}$$

(c) Attenuation factor in decibel/meter

$$= \frac{L_{dB}}{d} = \frac{5.229}{400} = 0.01307 \text{ dB/m}$$

(3-21) A transmission line has the following parameters at 50 MHz:  $R = 0.15 \text{ } \Omega/\text{m}$ ,  $G = 4 \times 10^{-6} \text{ S/m}$ , and  $C = 10 \text{ pF/m}$ . Determine the following:

(a)  $Z$

$$Z = R + j\omega L = 0.15 + j(2\pi \times 50 \text{ MHz} \times 1.2 \mu\text{H})$$

$$0.15 + j376.99 \frac{\Omega}{\text{m}}$$

$$377.29 \angle 1.5310 \frac{\Omega}{\text{m}}$$

(b)  $Y$

$$Y = G + j\omega C = 4 \times 10^{-6} + j(2\pi \times 50 \text{ MHz} \times 10 \text{ pF})$$

$$4 \times 10^{-6} + j3.1416 \times 10^{-3} \text{ S/m}$$

$$3.1416 \times 10^{-3} \angle 1.5695 \text{ S/m}$$

(c)  $\alpha$

$$\alpha = \sqrt{ZY} = \sqrt{(377.29 \angle 1.5310)(3.1416 \times 10^{-3} \angle 1.5695)}$$

$$= \sqrt{1.1853 \angle 3.1005} = 1.0887 \angle 1.5503$$

$$= 22.36 \times 10^{-3} + j1.088$$

$$= 22.36 \times 10^{-3} \text{ Np/m}$$

$$= j1.008 \text{ rad/m}$$

(3-22) A lossy audio-frequency line has the following parameters at 2 kHz:  $R = 0.2 \text{ } \Omega/\text{m}$ ,  $G = 2 \times 10^{-6} \text{ S/m}$ , and  $C = 0.1 \mu\text{F/m}$ . Determine the following:

(a)  $Z$

$$Z = R + j\omega L = 0.20 + j(2\pi \times 2 \text{ KHz} \times 0.1 \mu\text{H})$$

$$0.20 + j1.2566 \frac{\Omega}{\text{m}}$$



$$0.200 \angle 6.283 \frac{\Omega}{\text{ft}}$$

(b) Y

$$Y = G + j\omega C = 0 + j(2\pi \times 2 \text{ KHz}) \times 2 \text{ pC/ft}$$

$$0 + j2.5133 \times 10^8 \frac{\Omega}{\text{ft}}$$

$$251.33 \times 10^{10} \angle 1.571 \frac{\Omega}{\text{ft}}$$

(c)  $Z \cdot Y$

$$= \sqrt{ZY} = \sqrt{(0.200 \angle 6.283)(251.33 \times 10^{10} \angle 1.5701)}$$

$$= \sqrt{50.27 \times 10^{10} \angle 1.58} = 70.9 \times 10^6 \angle 0.79$$

$$= 5 \times 10^{-5} + j5.029 \times 10^{-5}$$

$$= 5 \times 10^{-5} \text{ Np/ft}$$

$$= j5.029 \times 10^{-5} \text{ rad/ft}$$

(d) Attenuation in dB/ft

$$\text{dB} = 8.69 \times 5 \times 10^{2.5} = 4.34 \times 10^{2.4} \frac{\text{dB}}{\text{ft}}$$

(e) v

$$v = \frac{v}{\beta} = \frac{2 \times 2 \text{ kHz}}{5.029 \times 10^{2.5}} = 25 \times 10^7 \frac{\text{V}}{\text{ft}}$$

(f)  $Z$

$$Z = \frac{0.200 \angle 6.283}{251.33 \times 10^{10} \angle 1.571} = 8 \times 10^6 \angle -1.57$$

$$= 2821 \angle -0.783 \Omega = 2001 - j989 \Omega$$

(3-23) A coaxial cable has the following parameters at a frequency of 1 MHz:

series resistance = 0.3  $\Omega/\text{ft}$

series reactance = 2  $\Omega/\text{ft}$

shunt conductance = 0.5  $\mu\text{S}/\text{m}$

shunt susceptance = 0.6  $\text{mS}/\text{m}$

Determine the following:

$$Z = 0.3 + j2 \text{ } \Omega/\text{ft} = 2.022 \angle 1.419 \Omega/\text{ft}$$

$$Y = 0.5 \mu + j0.6 \text{ mS}/\text{m} = 0.6 \text{ m} \angle 1.57 \frac{\Omega}{\text{ft}}$$

(a)  $Z \cdot Y$

$$\begin{aligned}
&= \sqrt{ZY} = \sqrt{(2.02 \angle 1.422^\circ)(0.6 \angle 1.57^\circ)} \\
&= \sqrt{1.213 \angle 3^\circ} = 0.0348 \angle 1.5^\circ = 2.6\text{m} + j0.035 \\
&= 2.6\text{m Np/m} \\
\alpha &= 0.0348 \text{ rad/m}
\end{aligned}$$

**(b) Attenuation in dB/ft**

$$\alpha_{\text{dB}} = 8.69 \alpha \cdot 2.6\text{m} = 0.02263 \text{ dB/m}$$

**(c) v**

$$v = \frac{2 \times 1\text{MHz}}{0.0348} = 18.1 \times 10^7 \text{ m/s}$$

**(d) Z<sub>in</sub>**

$$\begin{aligned}
Z_{\text{in}} &= \frac{Z_0}{\frac{Z_0}{Z_L} + j \tan \beta l} = \frac{2.02 \angle 1.4219^\circ}{\frac{0.6 \angle 1.57^\circ}{2.02 \angle 1.4219^\circ} + j \tan \beta l} = \sqrt{3.37 \angle -0.148^\circ} \\
&= 58.06 \angle -0.074^\circ \Omega = 57.9 - j4.3 \Omega
\end{aligned}$$

**(3-24) For the coaxial cable of problem 3-23, repeat the analysis at 100 MHz if the series resistance increases to 1 Ω/m, but the shunt conductance remains essentially the same. (Note: You must apply basic ac circuit theory to determine the new values for the reactance and susceptance.)**

$$1. \quad L = \frac{X}{2 \times 1\text{MHz}} = \frac{2}{2 \times 1\text{MHz}} = 0.32 \mu\text{H/m}$$

$$B = \frac{G}{2 \times 1\text{MHz}} = \frac{0.6}{2 \times 1\text{MHz}} = 95.5 \text{ nS/m}$$

$$Z = Z_0 + j\omega L = 1 + j200 \times 10^8 \cdot 0.312 \cdot 10^{-6} \Omega/\text{m}$$

$$1 + j200 = 200 \angle 1.57 \text{ } \Omega/\text{m}$$

$$Y = G + jB = 0.5 \times 10^{-6} + j95.5 \times 10^{-12}$$

$$= 0.5 \times 10^{-6} + j0.06 = 0.06 \angle 1.571 \text{ S/m}$$

$$a. \quad = \sqrt{ZY} = \sqrt{(200 \angle 1.57)(0.06 \angle 1.571)}$$

$$= \sqrt{12 \angle 3.137} = 3.46 \angle 1.57$$

$$= 8.3\text{m} + j3.46$$

$$= 8.3 \text{ m Np/m}$$

$$= 3.46 \text{ rad/m}$$

b.  $\text{dB} = 8.69 \times 8.3 \times 10^{-3} = 0.072 \text{ dB/m}$

c.  $\lambda = \frac{v}{f} = \frac{2 \times 100 \text{ MHz}}{3.46} = 1.814 \times 10^8 \text{ m/s}$

d.  $\Gamma_{\text{in}} = \frac{Z_{\text{in}} - Z_0}{Z_{\text{in}} + Z_0} = \frac{200 \angle 1.57 - 0.06 \angle 1.571}{200 \angle 1.57 + 0.06 \angle 1.571} = \sqrt{3.33 \angle -0.0048}$   
 $= 57.74 \angle -0.0024 \text{ rad} = 57.74 \text{ } \hat{a} = 57.74 \text{ } \hat{o} j0.139$

**(3-25) For the circuit of fig. P3-25, determine the following:**

**(a) Input current  $I_1$**

$$I = \frac{E}{Z_1 + Z_0} = \frac{50 \angle 0}{300 + j290 - j60} = \frac{50 \angle 0}{590 - j60}$$

$$= \frac{50 \angle 0}{593 \angle -0.1011} = 84.31 \angle 0.1013 \text{ mA}$$

**(b) Input Voltage  $V_1$**

$$V_1 = I_1 * Z_1 = (290 - j60) * (0.84 \angle 0.101)$$

$$= (296.14 \angle -0.204) (0.084 \angle 0.101) = 24.97 \angle -0.103 \text{ V}$$

**(c) Input power  $P_1$**

$$P_1 = I_1^2 * R_1 = (0.084)^2 * 290 = 2.06 \text{ W}$$

**(d) Load current  $I_2$**

$$I_2 = 0.084 \angle 0.101 * (e^{-j1.5}) = 0.019 \angle -0.5$$

**(e) Load Voltage  $V_2$**

$$V_2 = (24.97 \angle (1.5)) (0.019 \angle -0.6) = 5.57 \angle -0.703 \text{ V}$$

**(f) Load Power  $P_2$**

$$P_2 = I_2^2 * R_2 = (0.019)^2 * 290 = 0.103 \text{ W}$$

**(g) Line loss in dB**

$$\Gamma_{\text{dB}} = 10 \log_{10} \frac{P_1}{P_2} = 10 \log_{10} \frac{2.026}{0.103} = 13.03 \text{ dB}$$

**(3-26) For the circuit of fig. P3-26, determine the following:**

(a) Input current  $I_i$

$$I_i = \frac{I_o}{1 + \beta} = \frac{80 \angle 0}{600 + 400 + (600 + 400)} = \frac{80 \angle 0}{1200 - 200}$$

(b) Input Voltage  $V_i$

$$Z_o = R_o + jX_o = 600 + j100 = 608.28 \angle 0.165 \text{ rad}$$

$$V_i = Z_o I_i = (608.28 \angle 0.165) (0.0658 \angle -0.165) = 40 \angle 0 \text{ V}$$

(c) Input power  $P_i$

$$P_i = I_i^2 * R_o = 0.066^2 * 600 = 2.59 \text{ W}$$

(d) Load current  $I_o$

$$I_o = \frac{V_i}{8.69} = \frac{24}{8.69} = 2.76 \text{ Np}$$

$$I_o = (0.066 \angle -0.165) (2.76^3) (1 \angle -3) = 4.150 \angle -3 \angle -3.165 \text{ rad}$$