Practice Circuits Problem 2 Sunday, November 29, 2020 11:30 PM (1 point) A series circuit has a capacitor of $\frac{1}{20} \times 10^{-6}$ F and an inductor of 5 H. If the initial charge on the capacitor is 3×10^{-3} C and there is no initial current, find the charge on the capacitor Q(t). What is the differential equation for this closed circuit? What is the formula for the charge on the capacitor? Q(t) = help (formulas) L = 5 H $Q(0) = 3 \times 10^{-3} C$ 1 Q" + BQ+ - Q = 0 $5Q'' + \frac{1}{\frac{1}{20} \cdot 10^{-6}}Q = 0$ 5Q" + 20.000,000Q = 0The Ditterential equation for the closed circuit 5Q"+20000000Q=0 5r2+20000000=0 r2 = -4000000 r=0±2000i λ=0 20-2000 $Q(t) = e^{\lambda t} (C, Sin(wt) + C_2 COS(wt))$ $Q(t) = e^{0t} (C_1 Sin(2000t) + C_2 Cos(2000t))$ $Q(t) = (C_1 Sin(20000t) + C_2 Cos(20000t))$ $Q'(+) = C_1 \cos(2000+) \cdot 2000 - 2000 C_2 \sin(2000+)$ $Q(0) = 3 \times 10^{-3} C$ $C_1Sin(2000t) + C_2Cos(2000t) = 3 \times 10^{-3}$ $C_1 Sin(2000(0)) + C_2(0S(2000(0)) = 3 \times 10^{-3}$ $C_1 \sin(0) + C_2 \cos(0) = 3 \times 10^{-3}$ $C_2 = 3 \times 10^{-3}$ $0 = C_1 (05(2000t), 2000 - 2000 C_2 Sin(2000t)$ + -> 0 (105(2000t), 2000 - 2000 (25in(2000t) = 0) $(1) \cdot 2000 - 0 = 0$ $\frac{1}{2}$ Put everything together $Q(t) = C_1 \sin(2000t) + C_2 \cos(2000t)$ $C_1 = 0 \qquad \text{and} \qquad C_2 = 3 \times 10^{-3}$ $Q(t) = (0) \sin(2000t) + (3 \times 10^{-3})\cos(2000t)$ $Q(t) = 0.003 \cos(2000t)$ Formula for the charge on the Capacitor