

Benjamin Tolbert – MAT 2680 Differential Equations

Project #2 – Section 6.3 – Problem #2 – 11/20/2023

Find the current in the RLC circuit, assuming that $E(t) = 0$ for $t > 0$.

2) $R = 2$ ohms; $L = .05$ henrys; $C = .01$ farads; $Q_0 = 2$ coulombs; $I_0 = -2$ coulombs

Since we know the values for R , L , and C , & $E(t) = 0$ for $t > 0$, that must mean the RLC circuit is in free oscillation. In that case, the values must be plugged into the equation:

$$LQ'' + RQ' + \frac{1}{C}Q = 0$$

$$0.5Q'' + 2Q' + 100Q = 0$$

When converted, the characteristic equation is:

$$0.5r^2 + 2r + 100 = 0$$

Afterwards, the roots for the characteristic equation must be found:

$$r = \frac{-R \pm \sqrt{R^2 - 4L/C}}{2L}$$

$$r = \frac{-(2) \pm \sqrt{(2)^2 - 4(0.5)(100)}}{2(0.5)}$$

$$r = -2 \pm \sqrt{-196}$$

$$r = -2 \pm 14i$$

$$r_1 = -\frac{R}{2L} + i\omega_1; r_2 = -\frac{R}{2L} - i\omega_1$$

$$r_1 = -2 + 14i; r_2 = -2 - 14i$$

In the case of this circuit, it is underdamped as $R < \sqrt{4L/C}$ ($2 < \sqrt{200}$). The roots, r_1 and r_2 have also been found. From there, the general solution is:

$$Q = e^{-Rt/2L}(c_1 \cos \omega_1 t + c_2 \sin \omega_1 t)$$

$$Q = e^{-2t}(c_1 \cos(14t) + c_2 \sin(14t))$$

Differentiating the solution and collecting like terms gives:

$$Q' = -2e^{-2t}(c_1 \cos(14t) + c_2 \sin(14t)) + 14e^{-2t}(-c_1 \sin(14t) + c_2 \cos(14t))$$

To solve the initial value problem of $Q_0 = 2 \text{ coulombs}$; $I_0 = -2 \text{ coulombs}$, t must be set to 0 for Q and Q' to equal Q_0 and I_0 respectively.

$$Q(0) = e^{-2(0)} (c_1 \cos(14(0)) + c_2 \sin(14(0))) = 2$$

$$Q(0) = e^0 (c_1 \cos(0) + c_2 \sin(0)) = 2$$

$$Q(0) = 1(c_1 \cos(0) + c_2 \sin(0)) = 2$$

$$Q(0) = 1(c_1 + 0) = 2$$

$$Q(0) = c_1 = 2$$

$$c_1 = 2$$

With c_1 found, it can be plugged into Q' to find c_2 .

$$Q'(0) = -2e^{-2(0)} (c_1 \cos(14(0)) + c_2 \sin(14(0))) + 14e^{-2(0)} (-c_1 \sin(14(0)) + c_2 \cos(14(0))) = -2$$

$$Q'(0) = -2e^0 (c_1 \cos(0) + c_2 \sin(0)) + 14e^0 (-c_1 \sin(0) + c_2 \cos(0)) = -2$$

$$Q'(0) = -2(c_1 + 0) + 14(0 + c_2) = -2$$

$$Q'(0) = -2(c_1 + 0) + 14(0 + c_2) = -2$$

$$Q'(0) = -2c_1 + 14c_2 = -2$$

$$Q'(0) = -2(2) + 14c_2 = -2$$

$$Q'(0) = -4 + 14c_2 = -2$$

$$Q'(0) = 14c_2 = 2$$

$$Q'(0) = c_2 = \frac{2}{14}$$

$$c_2 = \frac{1}{7}$$

With both c_1 and c_2 found, it can be plugged into the solution, Q to give:

$$Q = e^{-2t} (2\cos(14t) + \frac{1}{7}\sin(14t))$$

Finally, differentiating Q will yield the current, I .

$$Q' = -2e^{-2t} \left(2\cos(14t) + \frac{1}{7} \sin(14t) \right) + 14e^{-2t} \left(-2\sin(14t) + \frac{1}{7} e^{-2t} \cos(14t) \right)$$

$$Q' = -4e^{-2t} \cos(14t) - \frac{2}{7} e^{-2t} \sin(14t) - 28e^{-2t} \sin(14t) + 2e^{-2t} \cos(14t)$$

$$Q' = -4e^{-2t} \cos(14t) - \frac{2}{7} e^{-2t} \sin(14t) - 28e^{-2t} \sin(14t) + 2e^{-2t} \cos(14t)$$

$$Q' = -2e^{-2t} \cos(14t) - \frac{198}{7} e^{-2t} \sin(14t)$$

$$I = e^{-2t} \left(-2\cos(14t) - \frac{198}{7} \sin(14t) \right)$$