Section 6.3 The RLC Circuit

Question 3: Find the current in the RLC circuit, assuming that E(t) = 0 for t > 0, given R = 2 Ω L = 0.1H C = 0.01F Q₀ = 2C I₀ = 0A

This problem involves free oscillation as E(t) = 0 for t > 0 and thus we use equation 6.3.8 from our book:

$$LQ^{\prime\prime} + RQ^{\prime} + \frac{1}{C}Q = 0.$$

Plugging our given values we get end with equation:

$$0.1Q'' + 2Q' + \frac{1}{0.01}Q = 0.$$

First, we will look at the characteristic polynomial of our equation, which is:

$$0.1r^2 + 2r + \frac{1}{0.01} = 0,$$

which has complex roots given by the quadratic formula

$$r = \frac{-2 \pm \sqrt{2^2 - (4 * 0.1 * \frac{1}{0.01})}}{2 * 0.1}; r_1 = -10 + 30i \text{ and } r_2 = -10 - 30i.$$

Then, we plug this into our solution for constant coefficients homogenous second order differential equations and we obtain:

$$Q = e^{-10t} (C_1 \cos(30t) + C_2 \sin(30t)).$$

Let's differentiate the equation so that we can then plug in our initial values and obtain our C_1 and C_2 . Using the Power rule to differentiate:

$$Q' = \frac{dQ}{dt} \left(e^{-10t} \left(C_1 \cos(30t) + C_2 \sin(30t) \right) \right)$$
$$Q' = \frac{dQ}{dt} \left(e^{-10t} \right) * \left(C_1 \cos(30t) + C_2 \sin(30t) \right) + e^{-10t} * \frac{dQ}{dt} \left(C_1 \cos(30t) + C_2 \sin(30t) \right)$$
$$Q' = -10e^{-10t} \left(C_1 \cos(30t) + C_2 \sin(30t) \right) + e^{-10t} \left(30C_2 \cos(30t) - 30C_1 \sin(30t) \right).$$

Our initial values are $Q_0 = 2C$ and $I_0 = -2A$, solve for C_1 and C_2 :

$$Q(0) = e^{-10(0)} (C_1 \cos(30(0)) + C_2 \sin(30(0))) = 2;$$
$$e^0 (C_1 \cos(0) + C_2 \sin(0)) = 2;$$
$$1 (C_1(1) + C_2(0)) = 2; C_1 = 2$$

Using our now found C_1 and $I_0 = 2A$:

$$Q'(0) = -10e^{0}(2\cos(0) + C_{2}\sin(0)) + e^{0}(30C_{2}\cos(0) - 30(2)\sin(0)) = 0$$
$$Q'(0) = -10(2 + 0) + (30C_{2}) = -20 + 30C_{2} = 0; C_{2} = \frac{20}{30} = \frac{2}{3}.$$

Plugging our C_1 and C_2 back into our general solution gives us:

$$Q = e^{-10t} (2\cos(30t) + \frac{2}{3}\sin(30t)),$$

which now we differentiate by power rule once again to obtain our current and our solution:

$$\frac{dQ}{dt} = \frac{dQ}{dt} (e^{-10t} (2\cos(30t) + \frac{2}{3}\sin(30t)))$$

$$\frac{dQ}{dt} = (\frac{dQ}{dt} (e^{-10t}) * (2\cos(30t) + \frac{2}{3}\sin(30t))) + (e^{-10t} * \frac{dQ}{dt} ((2\cos(30t) + \frac{2}{3}\sin(30t))))$$

$$Q' = -10e^{-10t} (2\cos(30t) + \frac{2}{3}\sin(30t)) + e^{-10t} (20\cos(30t) - 60\sin(30t))$$

$$Q' = -e^{-10t} (10 (2\cos(30t) + \frac{2}{3}\sin(30t)) - 20\cos(30t) + 60\sin(30t))$$

$$Q' = -e^{-10t} (20\cos(30t) + \frac{20}{3}\sin(30t) - 20\cos(30t) + 60\sin(30t))$$

$$Q' = -e^{-10t} (\frac{180 + 20}{3}\sin(30t))$$

$$I = -\frac{200}{3}e^{-10t}\sin(30t)$$