

3-1. A traveling wave of current in milliamperes is given by $i=8 \cos(2\pi * 10^6 t - 0.025x)$ with t in seconds and x in meters. Determine the following :

(a) Direction of propagation:

Positive

(b) Peak value

8

(c) Angular frequency:

$$2\pi * f = 2\pi * 10^6 = 6.28 * 10^6$$

(d) Phase constant:

$$\beta = .025$$

(e) Cyclic frequency:

$$f = \frac{\omega}{2\pi} = \frac{6.28 * 10^6}{2\pi} = 1 * 10^6$$

(f) Period:

$$T = \frac{1}{f} = \frac{1}{10^6} = 1 * 10^{-6}$$

(g) Wavelength:

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{.025} = 251.327 \text{ m}$$

(h) Velocity of propagation:

$$V = f * \lambda = 10^6 * 251.327 = 2.51 * 10^8$$

3-2. A traveling wave of voltage in volts is given by $v= 15 \cos(10^8 t + 0.35x)$ with t in seconds and x in meters. Determine the following:

(a) Direction of propagation:

Negative

(b) Peak value:

15

(c) Angular frequency:

10^8

(d) Phase constant

$\beta = .35$

(e) Cyclic frequency:

$$f = \frac{\omega}{2\pi} = \frac{10^8}{2\pi} = 1.59 * 10^7$$

(f) Period:

$$T = \frac{1}{f} = \frac{1}{1.59 * 10^7} = 6.289 * 10^{-8}$$

(g) Wavelength:

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{.35} = 17.952$$

(h) Velocity of propagation:

$$V = f * \lambda = 1.59 * 10^7 * 17.952 = 2.86 * 10^8$$

3-3. A sinusoidal current with a peak value of 2 A and a frequency of 50 MHz is traveling in the positive x-direction with a velocity of 2×10^8 m/s. Determine the following:

(a) Period

$$T = \frac{1}{f} = \frac{1}{50 * 10^6} = 20 * 10^{-9}$$

(b) Angular frequency

$$\omega = 2 * \pi * f = 2 * \pi * 50 * 10^6 = 3.14 * 10^8$$

(c) Phase constant

$$\beta = \frac{\omega}{v} = \frac{3.14 * 10^8}{2 * 10^8} = 1.57$$

(d) Wavelength

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{1.57} = 4.00203$$

(e) An equation for the current

$$= 2 * \cos(3.14 * 10^8 t - 1.57x)$$

3-4. A sinusoidal voltage with a peak value of 25 V and a radian frequency of 20 Mrad/s is traveling in the negative x-direction with a velocity of 3×10^8 m/s. Determine the following:

(a) Cyclic frequency:

$$f = \frac{\omega}{2\pi} = \frac{20 * 10^6}{2\pi} = 3.18 * 10^6$$

(b) Period:

$$T = \frac{1}{f} = \frac{1}{3.18 * 10^6} = 3.14 * 10^{-7}$$

(c) Phase constant:

$$\beta = \frac{\omega}{v} = \frac{20 * 10^6}{3 * 10^8} = .06667$$

(d) Wavelength:

$$\lambda = \frac{2\pi}{.06667} = 94.2$$

(e) An equation for the voltage:

$$= 25 \cos(20 * 10^6 t + (.06667x))$$

3-5. Consider the current traveling wave of Problem 3-1. Determine the following:

$$i = 8 \cos(2\pi * 10^6 t - 0.025x)$$

(a) a fixed phasor representation in peak units as either \bar{I}^+ or \bar{I}^- (You decide which label is appropriate.)

$$\bar{I}^+ = 8 * e^0 = 8 \angle 0$$

(b) the corresponding distance-varying phasor $\bar{I}(x)$ in peak units

$$\begin{aligned} \bar{I}(x) &= \bar{I}^+ = 8 * e^0 * e^{j\beta x} \\ &= 8 * e^0 * e^{j-0.025x} \\ &= (8 \angle 0) * (1 \angle -.0025x) \\ &= (8 \angle -.0025x) \end{aligned}$$

(c) the value of the distance-varying phasor at $x=100$ m.

$$\begin{aligned} &= (8 \angle -.0025x) \\ &= (8 \angle -.0025 * 100) \\ &= 8 \angle -2.5 \end{aligned}$$

3-6. Consider the voltage traveling wave of Problem 3-2. Determine the following:

$$15 \cos(10^8 t + 0.35x)$$

(a) a fixed phasor representation in peak units as either \bar{V}^+ or \bar{V}^- (You decide which label is appropriate.)

$$\bar{V}^- = 15 * e^{j0} = 15 \angle 0$$

(b) the corresponding distance-varying phasor $\bar{V}(x)$ in peak units

$$\begin{aligned} \bar{V}(x) &= \bar{V}^- * e^{j\beta x} \\ &= 15 * e^{j0} * e^{j0.35x} \\ &= 15 \angle -0.35 * x \end{aligned}$$

(c) the value of the distance-varying phasor at $x=4$ m.

$$\begin{aligned} \bar{V}(4) &= 15 \angle -0.35 * x \\ \bar{V}(4) &= 15 \angle -0.35 * 4 \\ \bar{V}(4) &= 15 \angle -1.20 \end{aligned}$$

3-7. Repeat the analysis of Problem 3-5 if the current of Problem 3-1 has a fixed phase shift such that it is described by

$$i = 8 \cos(2\pi \cdot 10^6 t - 0.025x + 1.5)$$

$$(a) \bar{I}^+ = 8 * e^{1.5} = 8 \angle 1.5$$

$$(b) \bar{I} = \bar{I}^+ * e^{j \cdot 0.025x}$$

$$= 8 * e^{1.5} * e^{j \cdot 0.025x}$$

$$= 8 \angle 1.5 - 0.25 * x$$

$$(c) \bar{I}(100) = 8 \angle 1.5 - 0.25 * 100$$

$$= 8 \angle 1.5 - 0.25 * 100$$

$$= 8 \angle -1$$

3-8. Repeat the analysis of Problem 3-5 if the current of Problem 3-1 has a fixed phase shift such that it is described by

$$v = 15 \cos(10^8 t + 0.35x - \frac{\pi}{3})$$

$$a) \bar{V} = 15 * e^{j \cdot \frac{\pi}{3}}$$

$$b) \bar{V} = 15 * e^{j \cdot \frac{\pi}{3}} * e^{j \cdot 0.35x}$$

$$= 15 \angle -\frac{\pi}{3} + 0.35x$$

$$c) \bar{V}(4) = 15 \angle -\frac{\pi}{3} + 0.35 * 4$$

$$= 15 \angle -58.6$$

3-9. Redefine the fixed phasor of Problem 3-5 so that the phasor magnitude is expressed in rms units, and determine the average power dissipated in 50-Ω resistance.

$$a) I_{rms} =$$

$$\frac{\bar{I}^+ = 8 * e^{j0} = 8 \angle 0}{\sqrt{2}}$$

$$= 5.65$$

$$b) \text{Power dissipated} = (I)^2 * R = (5.65)^2 * 50 = 1600 \text{ watts}$$

3-10. Redefine the fixed phasor of Problem 3-6 so that the phasor magnitude is expressed in rms units, and determine the average power dissipated in 75-Ω resistance.

a) $V_{rms} =$

$$\begin{aligned} \bar{V}^- &= \frac{8 * e^{j0} = 15 \angle 0}{\sqrt{2}} \\ &= 10.61 \angle 0 \end{aligned}$$

b) Power dissipated = $\frac{V^2}{R} = \frac{(10.61)^2}{75} = 1.501$ watts

3-11. Redefine the fixed phasor of Problem 3-7 so that the phasor magnitude is expressed in rms units. Would the power dissipated in a 50-Ω resistance be the same as in Problem 3-9?

a) $I_{rms} =$

$$\begin{aligned} \bar{I}^+ &= \frac{8 * e^{j1.5} = 8 \angle 1.5}{\sqrt{2}} \\ &= 5.56 \angle 1.5 \end{aligned}$$

b) Power dissipated = $(I)^2 * R = (5.56)^2 * 75 = 1600$ watts

3-12. Redefine the fixed phasor of Problem 3-8 so that the phasor magnitude is expressed in rms units. Would the power dissipated in a 75-Ω resistance be the same as in Problem 3-10?

a) $V_{rms} =$

$$\begin{aligned} \bar{V}^- &= \frac{15 * e^{j-\frac{\pi}{3}} = 15 \angle -\frac{\pi}{3}}{\sqrt{2}} \\ &= 10.61 \angle -\frac{\pi}{3} \end{aligned}$$

b) Power dissipated = $\frac{V^2}{R} = \frac{(10.61)^2}{75} = 1.501$ watts ; same as Problem 3-10

3-13. Under steady-state ac conditions, the forward current wave on a certain lossless 50-Ω line is $\bar{I}^+ = 2 \angle 0$ A. Determine the voltage forward wave.

a) $\bar{I}^+ = 2 \angle 0$ A.

b) $\bar{V}^+ = R_0 * \bar{I}^+$

$$\begin{aligned} &= 2 \angle 0 \text{ A} * 50 \\ \bar{V}^+ &= 100 \angle 0 \end{aligned}$$

3-14. Under steady-state ac conditions, the forward voltage wave in a 300-Ω lossless line is $\bar{V}^+ = 15\angle 3$ A. Determine the current forward wave.

$$\bar{I}^+ = \frac{\bar{V}^+}{R_0} = \frac{15\angle 3}{300} = .05\angle 3 \text{ A}$$

3-15. Under steady-state ac conditions, the reverse voltage wave on a lossless 50-Ω line is $\bar{V}^- = 200\angle 0$ A. Determine the reverse current wave.

$$\bar{I}^- = -\frac{\bar{V}^-}{R_0} = \frac{200\angle 0}{-50} = -4\angle 0 \text{ A}$$

3-16. Under steady-state ac conditions, the reverse current wave on a lossless 75-Ω line is $\bar{I}^- = .5\angle 2$. Determine the reverse voltage wave.

$$\bar{V}^- = R_0 * \bar{I}^- = 75 * (.5\angle 2 \text{ A}) = -37.5\angle 2$$

3-17. A table of specifications for one version of RG-8/U 50-Ω coaxial cable indicates that the attenuation per 100 ft at 50MHz is 1.2 dB. At this frequency, determine the following:

(a) attenuation factor in decibels per foot.

$$\alpha = \frac{1.2 \text{ dB}}{100 \text{ ft}} = .012$$

(b) attenuation factor in nepers per foot.

$$L_{NP} = \frac{.012 \text{ dB}}{8.686 \text{ ft}} = 1.382 * 10^{-3}$$

For a length of 300 ft, determine the following:

(c) total attenuation in decibels.

$$300 \text{ ft} * .012 = 3.6 \text{ dB}$$

(d) total attenuation in nepers

$$L_{NP} = (1.382 * 10^{-3}) * 300 = .4146$$

(e) $\frac{V_2}{V_1}$ ratio using both decibels and nepers for a single wave

$$\frac{V_2}{V_1} = e^{-L} = e^{-(1.382 * 10^{-3})} = .999$$

$$\frac{V_2}{V_1} = 10 * \frac{-3.6}{20} = .661$$

3-18. A transmission line has an attenuation of 0.05 dB/m. Determine the following:

(a) attenuation factor in nepers/m

For a length of 400 m, determine the following:

$$\frac{L_{dB}}{m} = \frac{.005}{8.686} = 5.76 * 10^{-4}$$

(b) total attenuation in decibels.

$$L_{db} = .05 * 400 = 20$$

(c) total attenuation in nepers

$$5.76 * 10^{-3} * 400 = 2.304$$

(d) $\frac{V_2}{V_1}$ ratio using both decibels and nepers for a single wave.

$$\frac{V_2}{V_1} = 10 * \frac{-20}{20} = .1$$

3-19. A single frequency wave is propagating in one direction on a transmission line of length of 200 m. With an input rms voltage of 50 V, the output rms voltage is measured as 20 V.

Determine the following:

(a) total attenuation in decibels.

$$1) = 20 \log_{10} \frac{V_1}{V_2}$$

$$8 L_{db} = 20 \log_{10} \left(\frac{50}{20} \right)$$

$$2) \alpha \frac{N_p}{m} = \frac{L_{db}}{8.686 * d} = \frac{8}{8.686 * 200} = .004511$$

$$3) \alpha_{db} = 8.686 * .004511 = .039991$$

$$4) L_{db} = .039991 * 200 = 7.9982$$

(b) total attenuation in nepers.

$$L_{NP} = \alpha * d = .004511 * 200 = .9022$$

(c) attenuation factor in decibels/meter

$$\alpha_{db} = 8.686 * .004511 = .039991$$

(d) attenuation factor in nepers/meter

$$\alpha_{Np} = 4.511 * 10^{-3} \frac{N_p}{m}$$

3-20. A single frequency wave is propagating in one direction on a transmission line of length 400 m. The input power to the line is 40 W, and the output power is 12 W. Determine the following:

(a) total attenuation in decibels.

$$1) L_{db} = 10 \log_{10} \left(\frac{P_1}{P_2} \right)$$

$$L_{db} = 10 \log_{10} \left(\frac{40}{12} \right) = 5.228$$

$$2) \alpha \frac{N_p}{m} = \frac{L_{db}}{8.686 * d} = \frac{5.228}{8.686 * 200} = .00334 = 3.34 * 10^{-3} \frac{N_p}{m}$$

$$3) \alpha_{db} = 8.686 * .00334 = .029011$$

$$4) .029011 * 400 = 11.6044$$

(b) total attenuation in nepers.

$$L_{NP} = \alpha * d = .00334 * 400 = 1.34$$

(c) attenuation constant in decibels/meters

$$\alpha_{db} = 8.686 * .004511 = .039991$$

(d) attenuation factor in nepers/meter

$$\alpha \frac{N_p}{m} = \frac{L_{db}}{8.686 * d} = \frac{5.228}{8.686 * 200} = .00334 = 3.34 * 10^{-3} \frac{N_p}{m}$$

3-21. A transmission line has the following parameters at 50 MHz: $L = 1.2 \mu\text{H}/\text{m}$, $R = 15 \Omega/\text{m}$, $C = 10 \text{ pF}/\text{m}$, and $G = 4 \mu\text{S}/\text{m}$. Determine the following:

$$(a) Z = R + j\omega L = 15 + j((2 * \pi * 50 * 10^6) * 1.2 * 10^{-6}) = 15 + j(376.991) \\ = 377 \angle 1.5$$

$$(b) Y = G + j\omega C = 4 * 10^{-6} + j((2 * \pi * 50 * 10^6) * 10 * 10^{-12}) = .000004 + j(.003142) \\ = .003142 \angle 1.5$$

(c) γ , α , and β

$$\gamma = \sqrt{ZY} = \sqrt{(377 \angle 1.5) * (.00314 \angle 1.57)} = .0223341 + j(1.08855) \\ \alpha = .0223341 \\ \beta = 1.08855$$

(d) attenuation in dB/m

$$\alpha_{db} = 8.686 * .0223341 = .193994 \frac{dB}{m}$$

$$(e) v = \frac{\omega}{\beta} = \frac{2 * \pi * 50 * 10^6}{1.08855} = 2.885 * 10^8 \frac{m}{s}$$

$$(f) Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{15 + j(376.991)}{.000004 + j(.003142)}} = 346.46 - j(6.67) = 346.525 \angle -.02$$

3-22. A lossy audio-frequency line has the following parameters at 2 kHz: $L = 0.1 \mu\text{H}/\text{ft}$, $R = 0.2 \Omega/\text{ft}$, $C = 2 \text{ pF}/\text{ft}$, and G is negligible. Determine the following:

$$(a) Z = R + j\omega L = .2 + j((2 * \pi * 2000) * .1 * 10^{-6}) = .2 + j(0.12566) = .200394 \angle .0627$$

$$(b) Y = G + j\omega C = j((2 * \pi * 2000) * 2 * 10^{-12}) = j(2.513 * 10^{-8}) = \\ = 2.513 * 10^{-8} \angle 1.5$$

(c) $\gamma, \alpha,$ and β

(d) $\gamma, \alpha,$ and β

$$\gamma = \sqrt{Z \angle Y} = \sqrt{(.2 + j(0.12566)) * (.j (2.513 * 10^{-8}))} = .000049 + j (.000052)$$

$$\alpha = .000049$$

$$\beta = .000052$$

(e) attenuation in dB/ft

$$\alpha_{db} = 8.686 * .000049 = .000426 \frac{dB}{ft}$$

$$(f) v = \frac{\omega}{\beta} = \frac{2 * \pi * 2000}{.000052} = 2.42 * 10^8 \frac{m}{s}$$

$$(g) Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{.2 + j(0.12566)}{j(2.513 * 10^{-8})}} = 2823.88 \angle -.754$$

3-23. A coaxial cable has the following parameters at a frequency of 1 MHz:

series resistance = 0.3 Ω/m

series reactance = 2 Ω/m

shunt conductance = 0.5 $\mu S/m$

shunt susceptance = 0.6 mS/m

Determine the following:

$$1) Z = R + jL = .3 + j 2 = 2.022 \angle 1.4$$

$$2) Y = G + jC = .5 * 10^{-6} + j (.6 * 10^{-3}) = .5 * 10^{-6} + j.0006 \\ = .0006 \angle 1.57$$

(a) $\gamma, \alpha,$ and β

$$\gamma = \sqrt{Z \angle Y} = \sqrt{2.022 \angle 1.4 * (.0006 \angle 1.57)} = .002985 + j (.034703)$$

$$\alpha = .002985$$

$$\beta = .034703$$

(b) attenuation in dB/ft

$$\alpha_{db} = 8.686 * .002985 = .025928 \frac{dB}{m}$$

$$(c) v = \frac{\omega}{\beta} = \frac{2 * \pi * 1 * 10^6}{.034703} = 1.81 * 10^8 \frac{m}{s}$$

$$(d) Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{.3 + j 2}{.5 * 10^{-6} + j.0006}} = 333.337 - j(490972) = 337.062 \angle -.14$$

3-24. For the coaxial cable of Problem 3-23, repeat the analysis at 100 MHz if the series resistance increases to 1 Ω /m, but the shunt conductance remains essentially the same. (Note : You must apply basic ac circuit theory to determine the new values for the reactance and susceptance.) (Not Answered)

3-25. For the circuit of Fig. P3-25, determine the following:

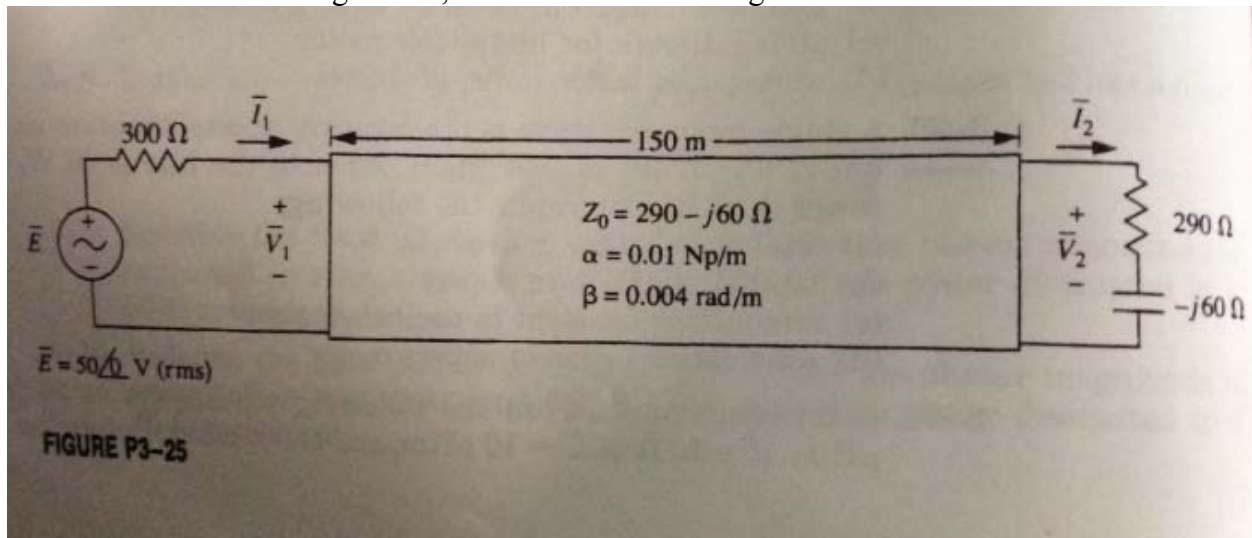


FIGURE P3-25

$$\alpha * d = 0.01 * 150 = 1.5$$

$$\beta * d = 0.004 * 150 = 0.6$$

(a) input current \bar{I}_1

$$\bar{I}_1 = \frac{E}{Z_1 + z_0} = \frac{50 \angle 0}{300 + 290 - j60} = 0.799903 + j0.081066 = 0.084 \angle 10.1$$

(b) input voltage \bar{V}_1

$$\bar{V}_1 = z_0 * \bar{I}_1 = (290 - j60) * (0.799903 + j0.081066) = 236.836 - j24.485 = 238.098 \angle -10.3$$

(c) input power P_1

$$P_1 = (\bar{I}_1)^2 * R_0 = (0.084)^2 * 290 = 2.04 \text{ w}$$

(d) load current \bar{I}_2

$$\bar{I}_2 = \bar{I}_1 * e^{-\alpha * d} * e^{-j\beta * d} = (0.084 \angle 10.1) * e^{-1.5} * e^{-j0.6} = 0.01794 \angle -4.99$$

(e) load voltage \bar{V}_2

$$\bar{V}_2 = \bar{V}_1 * e^{-\alpha * d} * e^{-j\beta * d} = (238.098 \angle -10.3) * e^{-1.5} * e^{-j0.6} = 55.5 \angle -7.03$$

(f) load power P_2

$$P_2 = (\bar{I}_2)^2 * R_0 = (0.01794)^2 * 290 = 0.0933 \text{ w}$$

(g) line loss in dB

$$L_{db} = 10 \log_{10} \left(\frac{P_1}{P_2} \right) = 10 \log_{10} \left(\frac{2.04}{0.0933} \right) = 13.41$$

3-26. For the circuit of Fig. P3-26, determine the following: (Not sure)

$$\alpha \frac{N_p}{mi} = \frac{L_{db}}{8.686 * d} = \frac{4}{8.686 * 6} = .077$$

$$\alpha * d = .077 * 6 = .462$$

$$\beta * d = .5 * 6 = .6$$

(a) input current \bar{I}_1

$$\bar{I}_1 = \frac{E}{Z_1 + z_0} = \frac{80 \angle 0}{1216 \angle -1.165} = .0649 - j.010806 = .0658 \angle -1.165$$

(b) input voltage \bar{V}_1

$$\bar{V}_1 = z_0 * \bar{I}_1 = (600 + j100) * (.0649 - j.010806) = 606.484 + j38.94 = 607.732 \angle .064118$$

(c) input power P_1

$$P_1 = (\bar{I}_1)^2 * R_0 = (.0658)^2 * 290 = 1.2556 \text{ w}$$

(d) load current \bar{I}_2

(e) load voltage \bar{V}_2

(f) load power P_2

(g) line loss in nepers

