

Chapter 7

EMT1150

Introduction to Circuit Analysis

Department of Computer
Engineering Technology

Fall 2018

Prof. Rumana Hassin Syed




Chapter7 Series and Parallel Networks

- Identify Series-Parallel Networks
- Understand Reduce and Return Approach
- Use Block Diagram Approach
- Descriptive Examples
- Solve Ladder Networks

Series and Parallel Networks

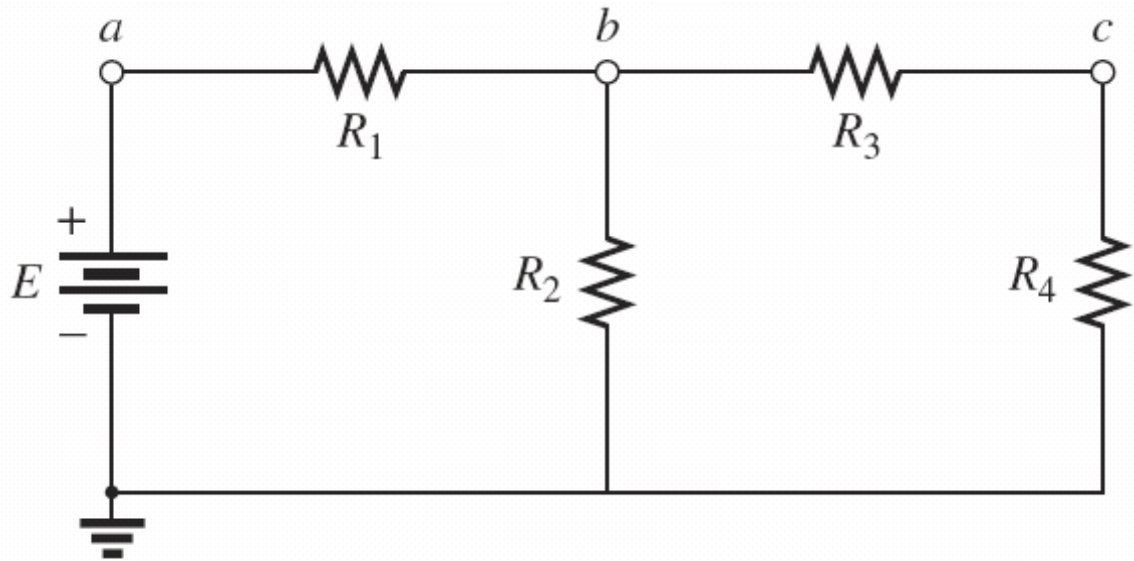- What is the relationship for circuit elements?
- How to find voltage and current for each element?




Series-parallel networks are networks that contain both series and parallel circuit configurations



Basic principle

- Take a moment to study the problem “**in total**”, find the relationship.
- Examine each region of the network independently, then combine them together.
- **Redraw the network** as often as possible with reduced branches.
- When you have a solution, check whether it is reasonable or not.

Reduce and Return Approach

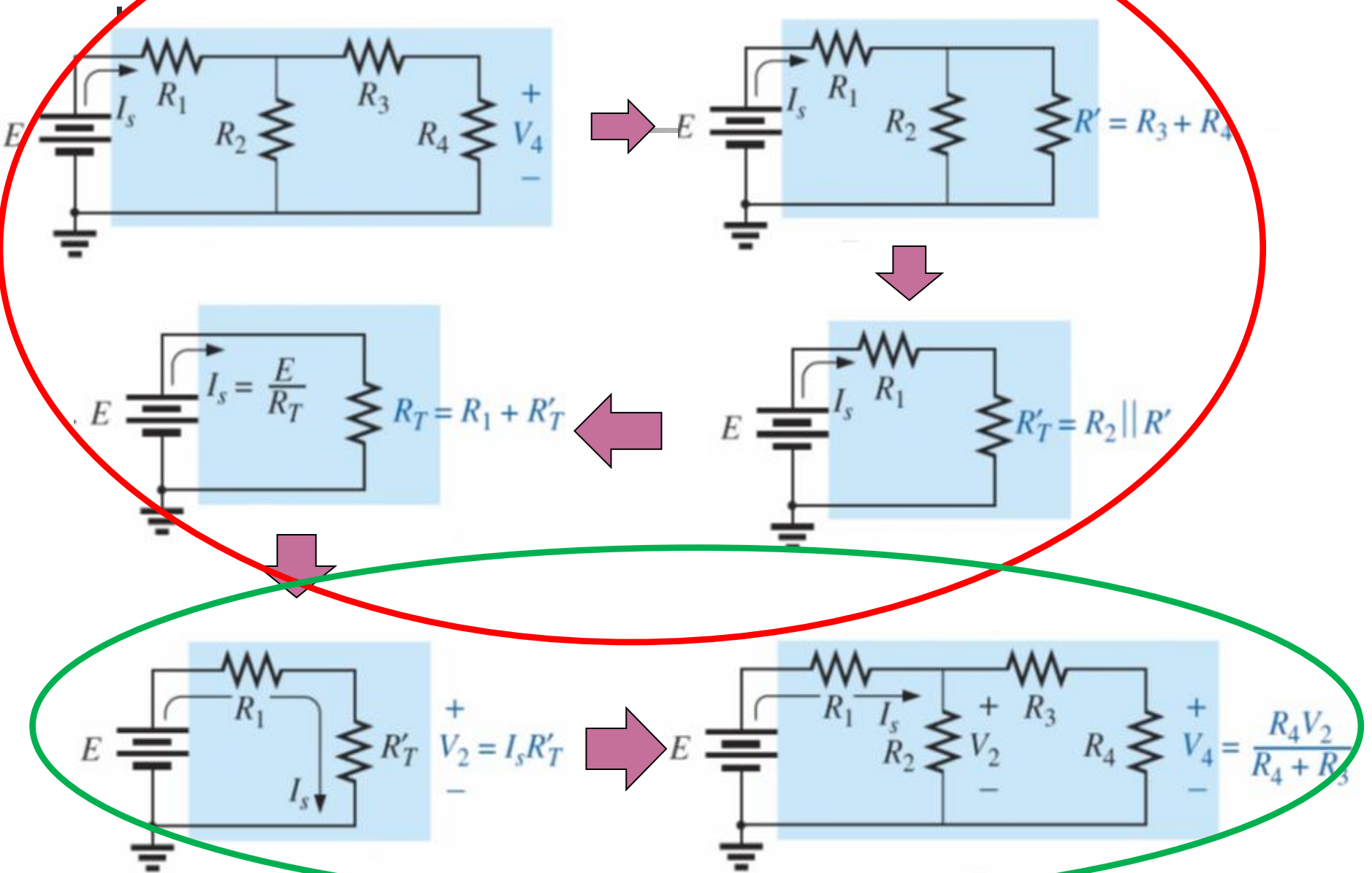




Reduce and Return Approach

- **Reduce phase:** reduce the network to its simplest form across the source, then determine the source current.
- **Return phase:** use the resulting source current to work back to the desired unknowns.

Exp1: Find current I_3 for the series-parallel network.
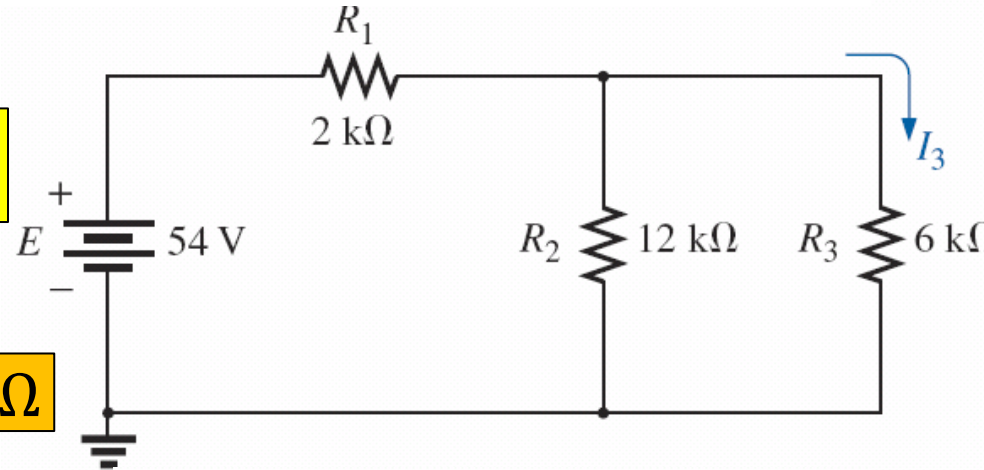
$$R' = R_2 // R_3 = \frac{(12k\Omega)(6k\Omega)}{12k\Omega + 6k\Omega} = 4k\Omega$$




$$R_T = R' + R_1 = 4k\Omega + 2k\Omega = 6k\Omega$$

$$I_s = \frac{E}{R_T} = \frac{54V}{6k\Omega} = 9(mA)$$

Current Divider Rule:
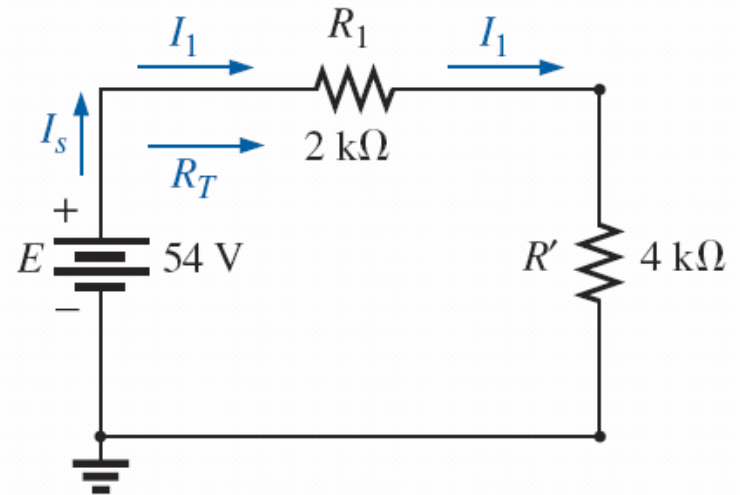
$$I_3 = I_s \frac{R'}{R_3} = 9mA \frac{4k\Omega}{6k\Omega} = 6(mA)$$




Common
mistake:

$$I_3 = I_s \frac{R_T}{R_3} = 9mA \frac{6k\Omega}{6k\Omega} = 9(mA)$$

Block diagram approach

- Group elements together according to their relationships.
- Then reveal the voltage and current relation between groups.
- Lastly, examine the impact of the individual component in each group.


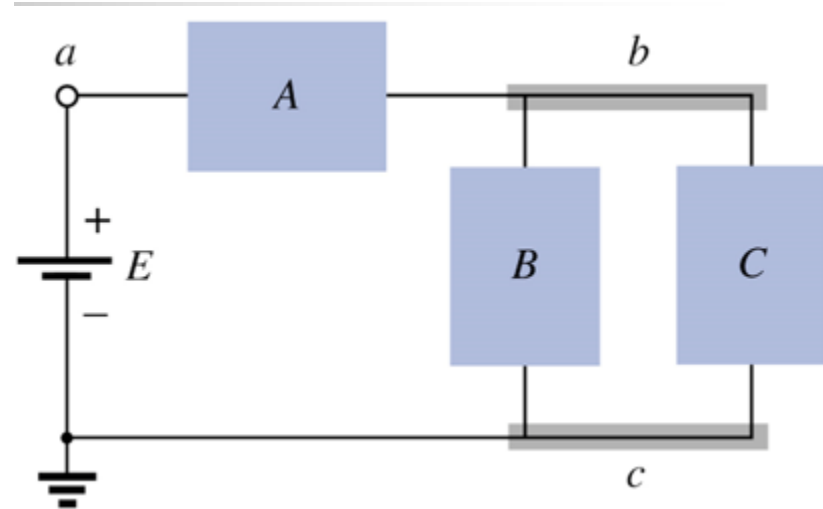


Exp2: Determine all currents and voltage of the network.

$$A: R_A = 4 \Omega$$

$$B: R_B = R_2 // R_3 = \frac{R}{N} = \frac{4 \Omega}{2} = 2 \Omega$$


$$C: R_C = R_4 + R_5 = 2 \Omega$$

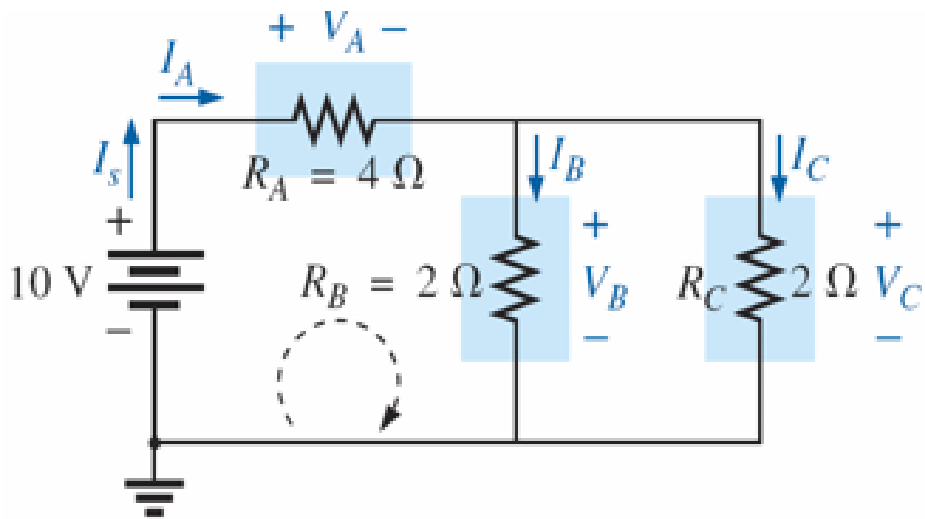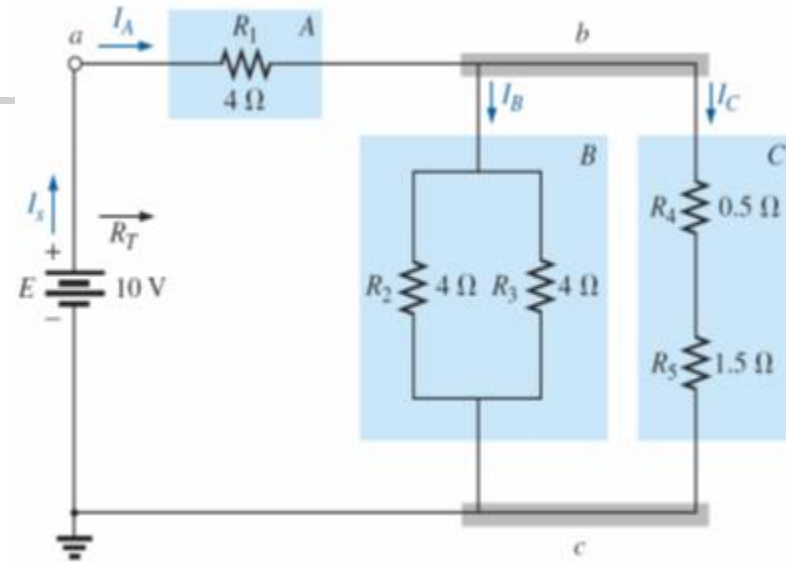

$$R_{B//C} = \frac{R}{N} = \frac{2 \Omega}{2} = 1 \Omega$$

$$R_T = R_A + R_{B//C} = 4 \Omega + 1 \Omega = 5 \Omega$$
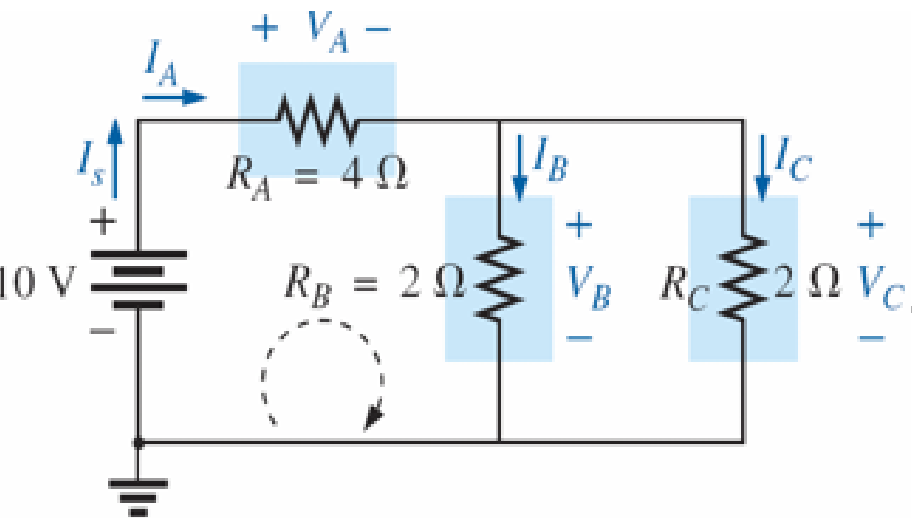
$$I_s = \frac{E}{R_T} = \frac{10V}{5 \Omega} = 2 A$$



$$I_A = I_s = 2 A$$

$$I_B = I_C = \frac{I_A}{2} = \frac{I_s}{2} = \frac{2 A}{2} = 1 A$$

$$I_{R_2} = I_{R_3} = \frac{I_B}{2} = 0.5 A$$


$$V_A = I_A R_A = (2 A)(4 \Omega) = 8 V$$

$$V_B = I_B R_B = (1 A)(2 \Omega) = 2 V$$

$$V_C = V_B = 2 V$$

$$VDR : V_{R_4} = V_C \frac{R_4}{R_C} = 2V \frac{0.5\Omega}{2\Omega} = 0.5 V$$

$$V_{R_5} = V_C \frac{R_5}{R_C} = 2V \frac{1.5\Omega}{2\Omega} = 1.5 V$$

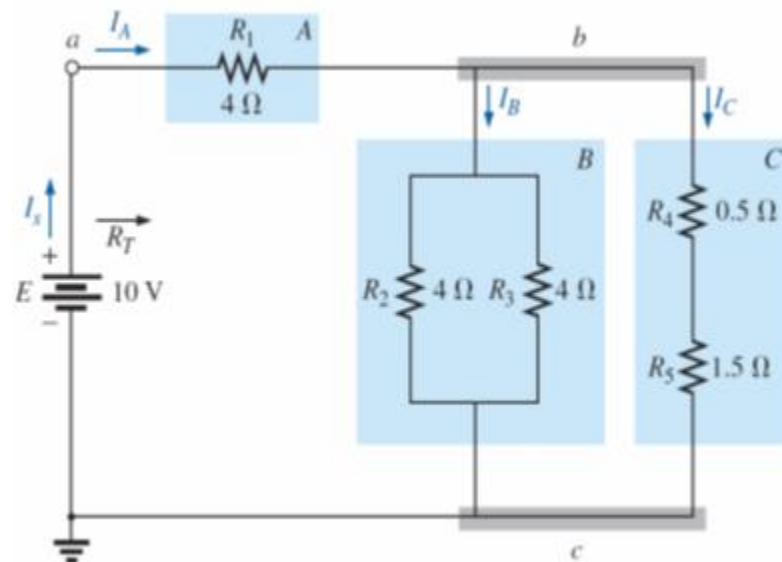

Exp3: Determine all currents and voltage.


$$R_A = R_{1//2} = \frac{(9\Omega)(6\Omega)}{9\Omega + 6\Omega}$$

$$= \frac{54\Omega}{15\Omega} = 3.6\Omega$$

$$R_B = R_3 + R_{4//5} = 4\Omega + \frac{(6\Omega)(3\Omega)}{6\Omega + 3\Omega}$$

$$= 4\Omega + 2\Omega = 6\Omega$$

$$R_C = 3\Omega$$

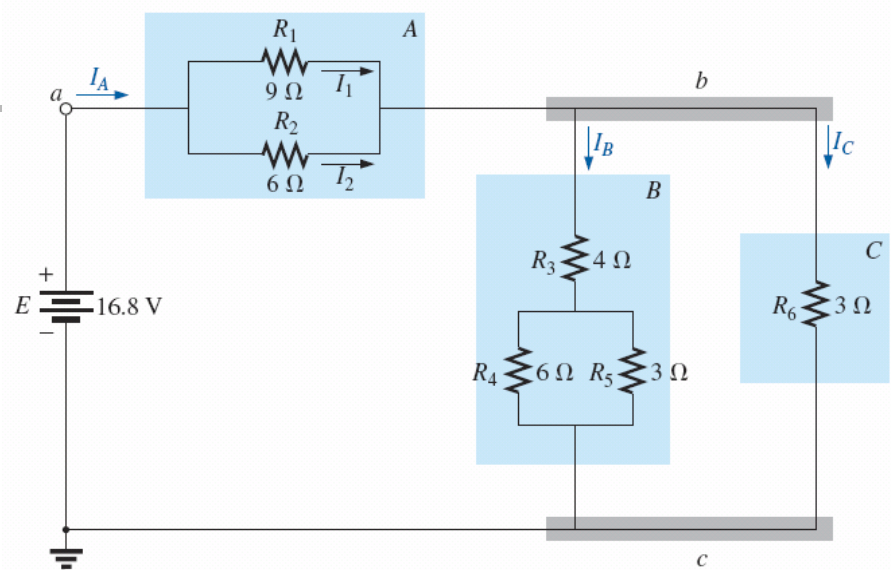


$$R_T = R_A + R_{B//C} = 3.6\Omega + \frac{(6\Omega)(3\Omega)}{6\Omega + 3\Omega}$$

$$= 3.6\Omega + 2\Omega = 5.6\Omega$$

$$I_s = \frac{E}{R_T} = \frac{16.8V}{5.6\Omega} = 3A$$

$$I_A = I_s = 3A$$

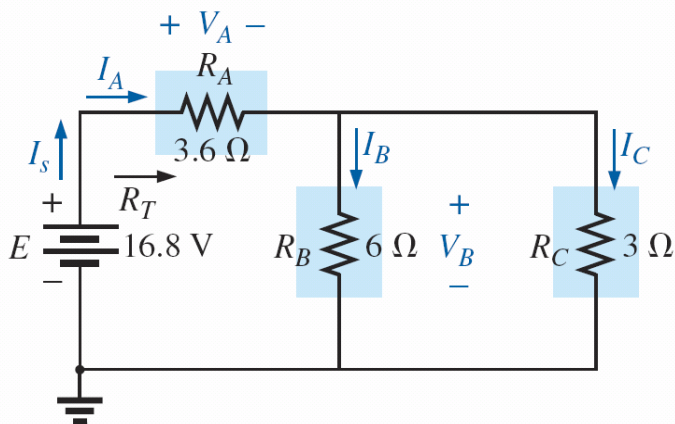

Applying the current divider rule yields

$$I_B = \frac{R_C I_A}{R_C + R_B} = \frac{(3\Omega)(3A)}{3\Omega + 6\Omega} = 1A$$


By Kirchhoff's current law,

$$I_C = I_A - I_B = 3A - 1A = 2A$$

By Ohm's law,

$$V_A = I_A R_A = (3A)(3.6\Omega) = 10.8V$$
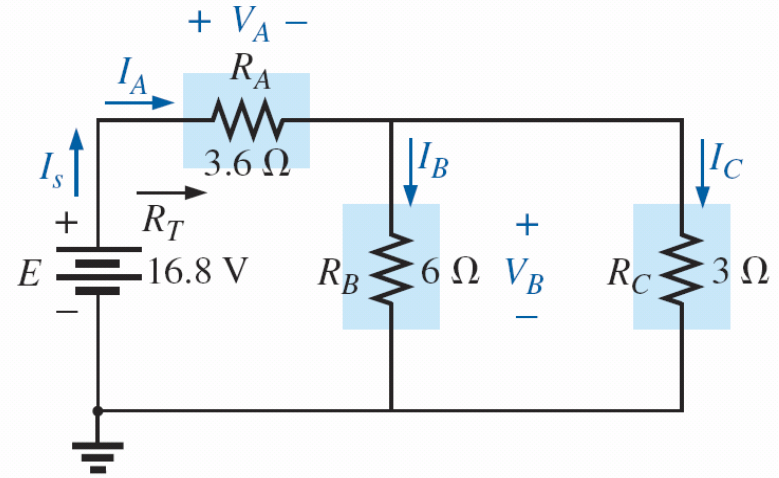
$$V_B = I_B R_B = V_C = I_C R_C = (2A)(3\Omega) = 6V$$



$$I_1 = \frac{R_2 I_A}{R_2 + R_1} = \frac{(6\Omega)(3A)}{6\Omega + 9\Omega} = 1.2A$$


$$I_2 = I_A - I_1 = 3A - 1.2A = 1.8A$$

$$I_{R_4} = \frac{R_5 I_B}{R_4 + R_5} = \frac{(3\Omega)(1A)}{6\Omega + 3\Omega} = 0.33A$$

$$I_{R_5} = I_B - I_{R_4} = 1A - 0.33A = 0.67A$$





$$V_{R_3} = \frac{R_3 V_B}{R_3 + R_{4//5}} = \frac{(4\Omega)(6V)}{4\Omega + 2\Omega} = 4(V)$$
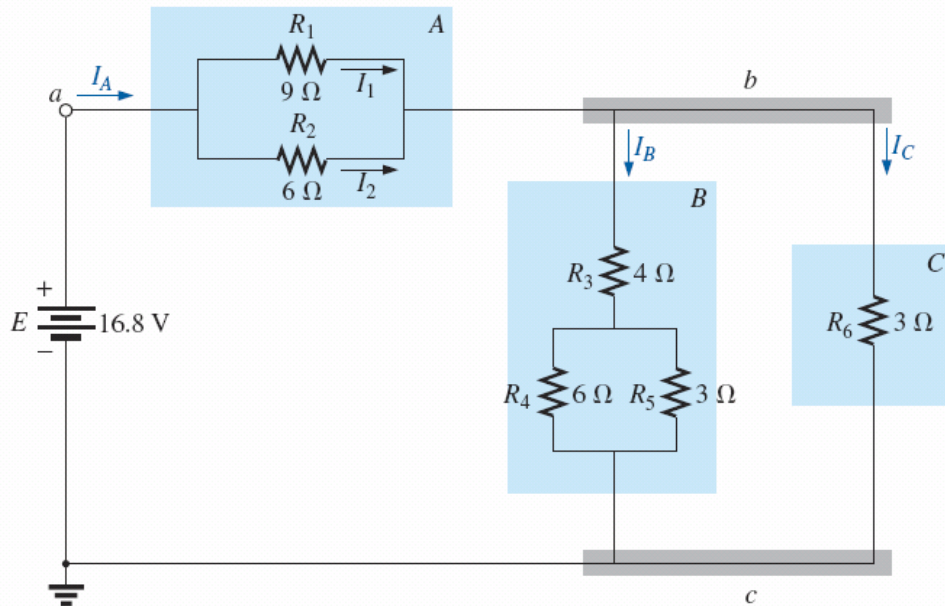
$$V_{R_{4//5}} = \frac{R_{4//5} V_B}{R_3 + R_{4//5}} = \frac{(2\Omega)(6V)}{4\Omega + 2\Omega} = 2(V)$$



More descriptive examples

- Other possible block models

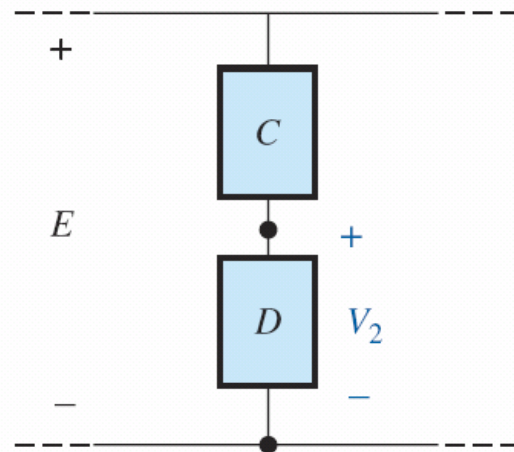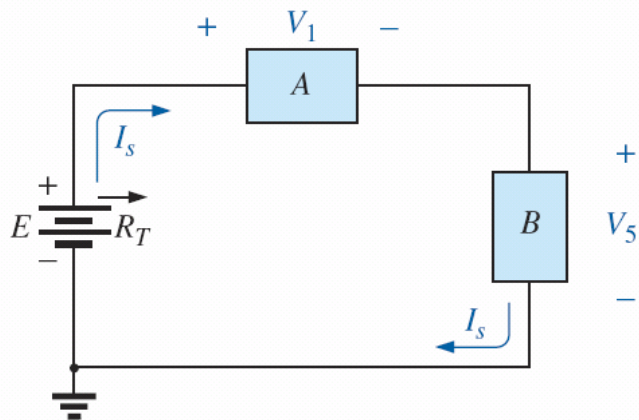
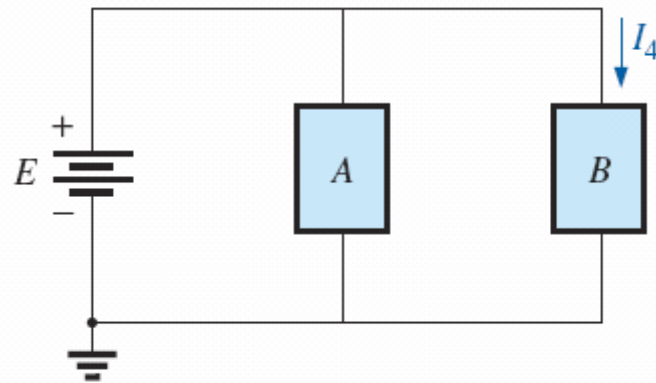
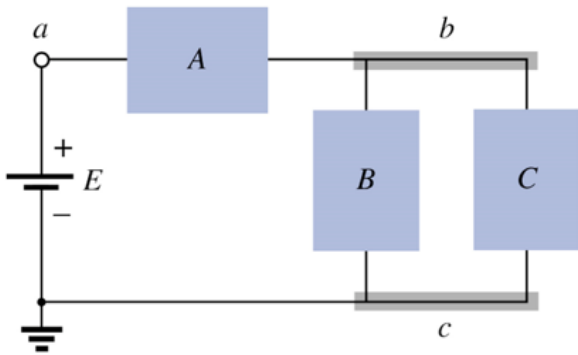


Exp4: Find the current I_4 and the voltage V_2 for the network.


$$I_4 = \frac{E}{R_B} = \frac{E}{R_4} = \frac{12V}{8\Omega} = 1.5 A$$

$$R_D = R_2 // R_3 = \frac{6\Omega \cdot 3\Omega}{6\Omega + 3\Omega} = 2\Omega$$

$$V_2 = \frac{R_D E}{R_D + R_C} = \frac{(2\Omega)(12V)}{2\Omega + 4\Omega} = 4 V$$

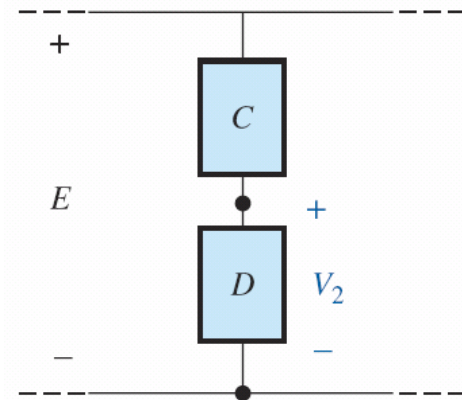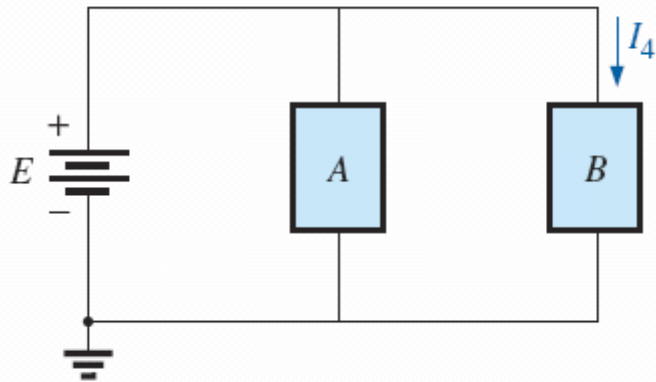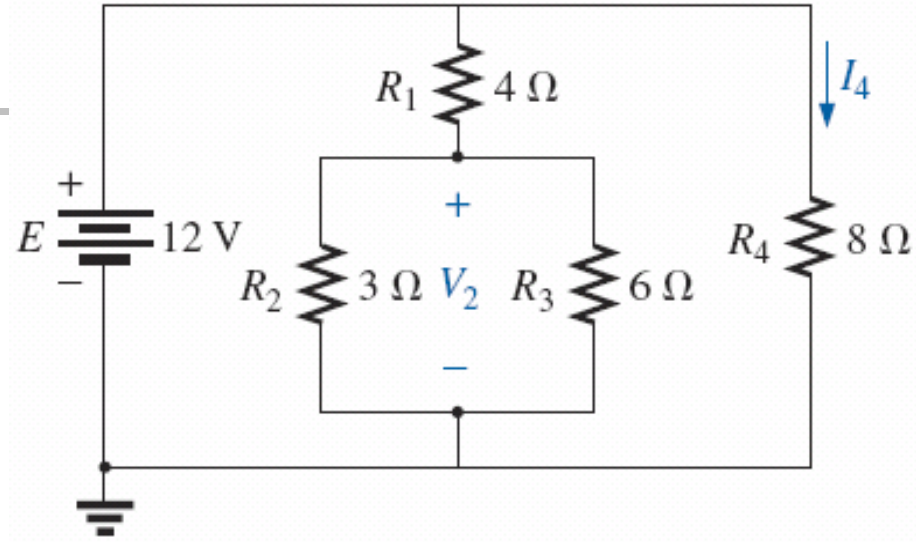

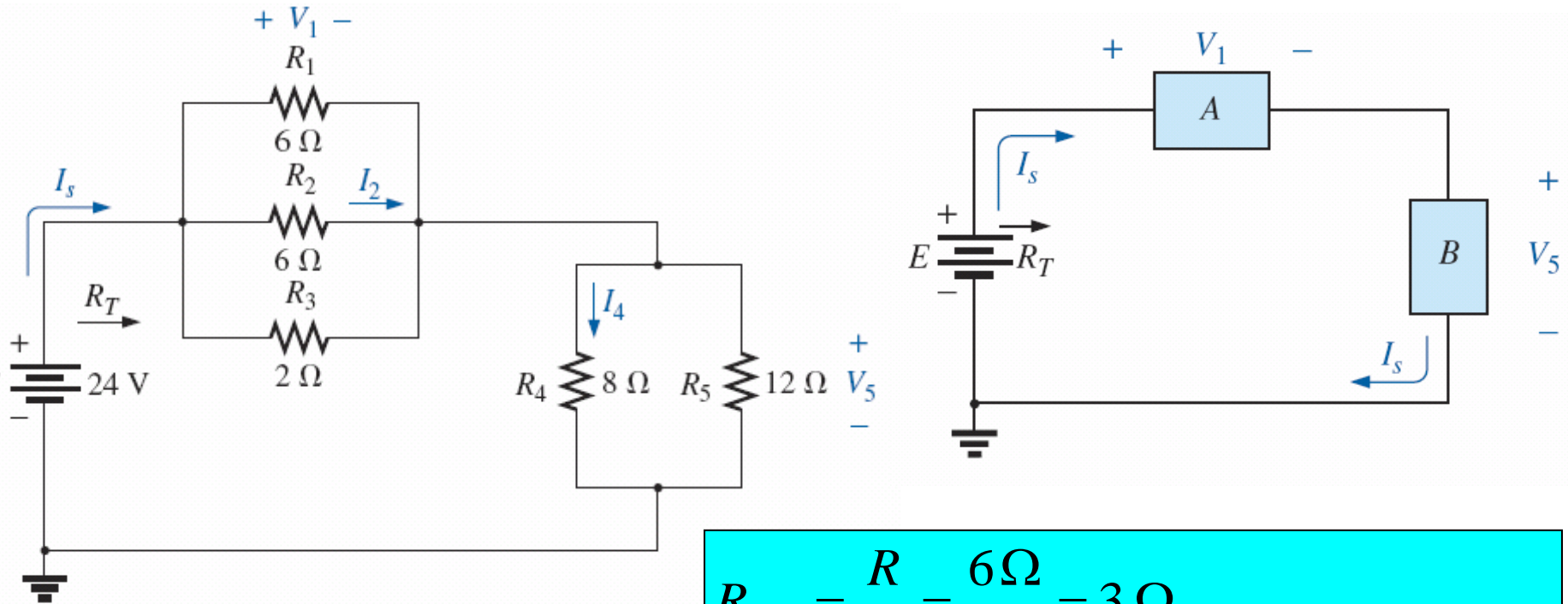
Exp5: Find the indicated currents and voltages for the network.



$$R_{1//2} = \frac{R}{N} = \frac{6\Omega}{2} = 3\Omega$$

$$R_A = R_{1//2//3} = \frac{(3\Omega)(2\Omega)}{3\Omega + 2\Omega} = \frac{6\Omega}{5} = 1.2\Omega$$
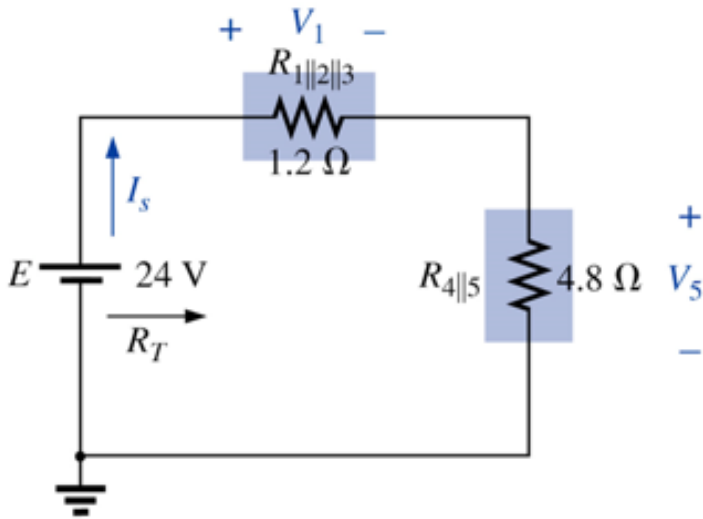
$$R_B = R_{4//5} = \frac{(8\Omega)(12\Omega)}{8\Omega + 12\Omega} = \frac{96\Omega}{20} = 4.8\Omega$$




$$R_T = R_{1//2//3} + R_{4//5}$$

$$= 1.2\Omega + 4.8\Omega = 6\Omega$$

$$I_s = \frac{E}{R_T} = \frac{24V}{6\Omega} = 4A$$

$$V_1 = I_s R_{1//2//3} = (4A)(1.2\Omega) = 4.8V$$


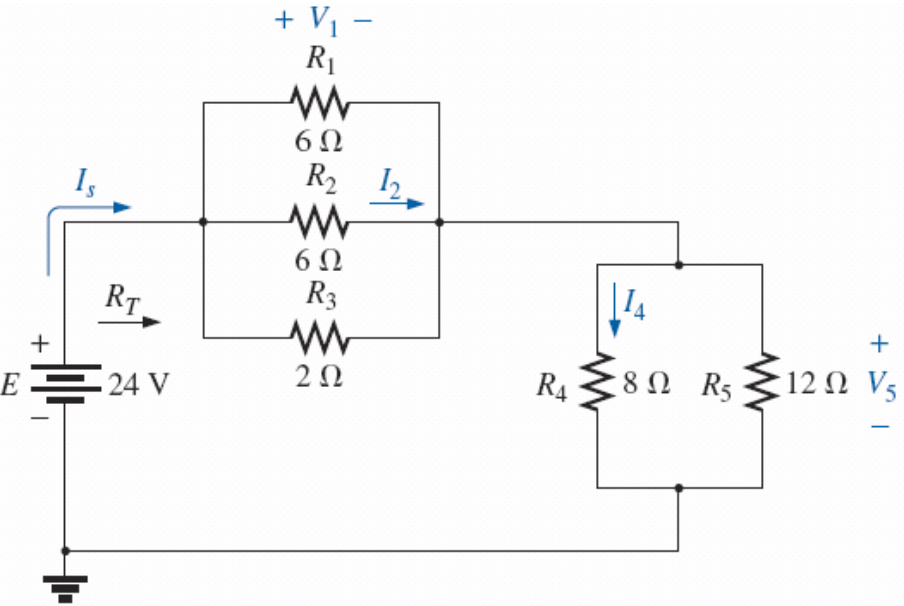
$$V_5 = I_s R_{4//5} = (4A)(4.8\Omega) = 19.2V$$



$$I_4 = \frac{V_5}{R_4} = \frac{19.2V}{8\Omega} = 2.4A$$

$$I_2 = \frac{V_2}{R_2} = \frac{V_1}{R_2} = \frac{4.8V}{6\Omega} = 0.8A$$

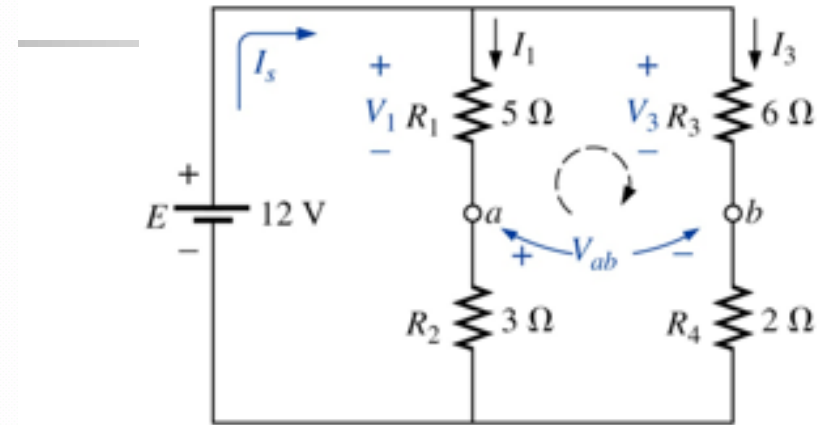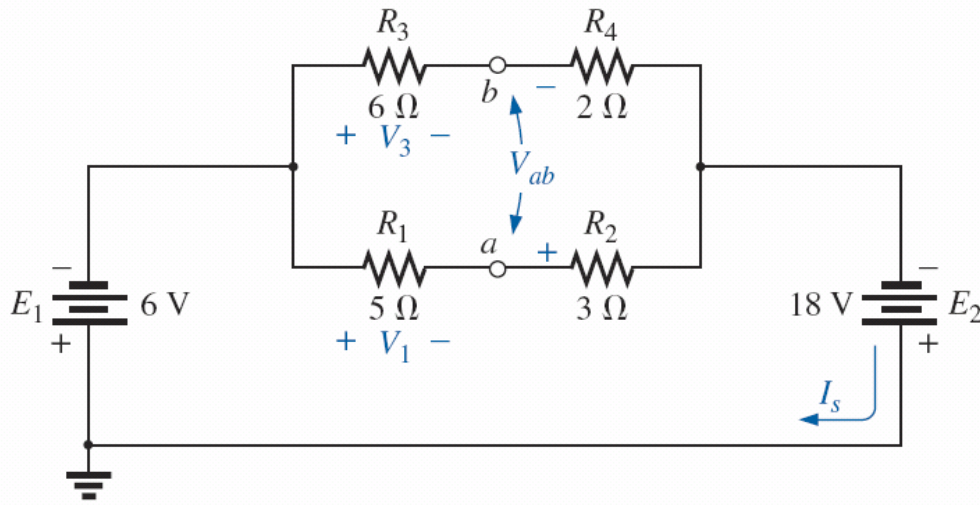- Exp6: a. Find the voltages V_1 , V_3 , and V_{ab} for the network.
 b. Calculate the source current I_s



Applying the voltage divider rule yields


$$V_1 = \frac{R_1 E}{R_1 + R_2} = \frac{(5\Omega)(12V)}{5\Omega + 3\Omega} = 7.5V$$

$$V_3 = \frac{R_3 E}{R_3 + R_4} = \frac{(6\Omega)(12V)}{6\Omega + 2\Omega} = 9V$$

Applying Kirchhoff's voltage law around the indicated loop of Fig.

$$-V_1 + V_3 - V_{ab} = 0$$
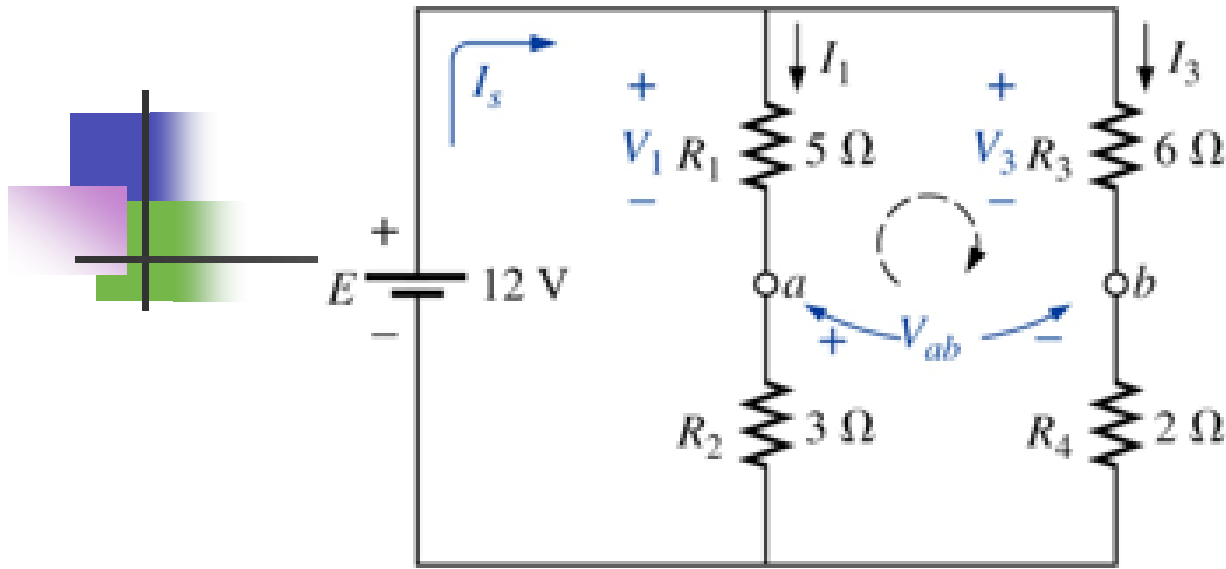
$$V_{ab} = V_3 - V_1 = 9V - 7.5V = 1.5V$$



b.

By Ohm's law,



$$I_1 = \frac{V_1}{R_1} = \frac{7.5V}{5\Omega} = 1.5A$$

$$I_3 = \frac{V_3}{R_3} = \frac{9V}{6\Omega} = 1.5A$$

Applying Kirchhoff's current law,


$$I_s = I_1 + I_3 = 1.5A + 1.5A = 3A$$

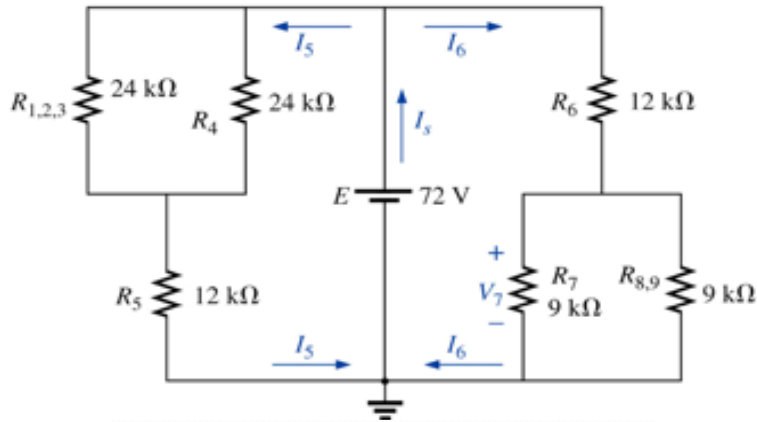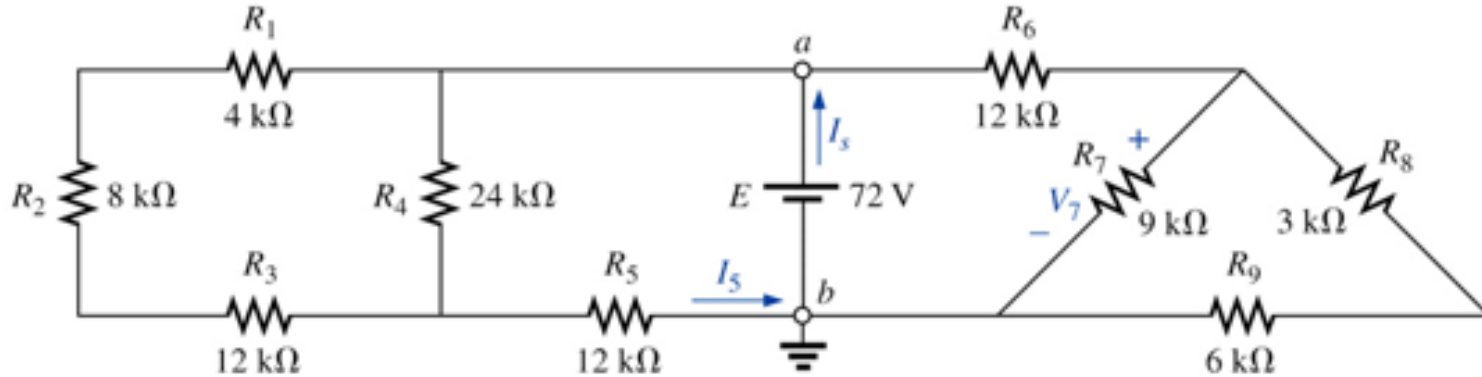Exp7: Calculate the indicated currents and voltage



$$I_5 = \frac{E}{R_{(1,2,3)//4} + R_5} = \frac{72V}{12k\Omega + 12k\Omega} = \frac{72V}{24k\Omega} = 3mA$$
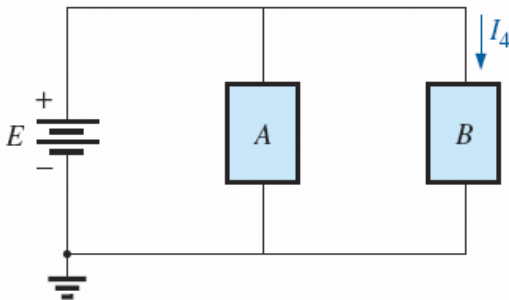
$$V_7 = \frac{R_{7//(8,9)}E}{R_{7//(8,9)} + R_6} = \frac{(4.5k\Omega)(72V)}{4.5k\Omega + 12k\Omega} = \frac{324V}{16.5} = 19.6V$$




$$I_6 = \frac{E}{R_{6,7//(8,9)}} = \frac{72V}{12k\Omega + 4.5k\Omega} = 4.36mA$$





$$I_s = I_5 + I_6 = 3mA + 4.36mA = 7.36mA$$

Ladder Network


- The name comes from the repetitive structure.
- Use the reduce and return approach

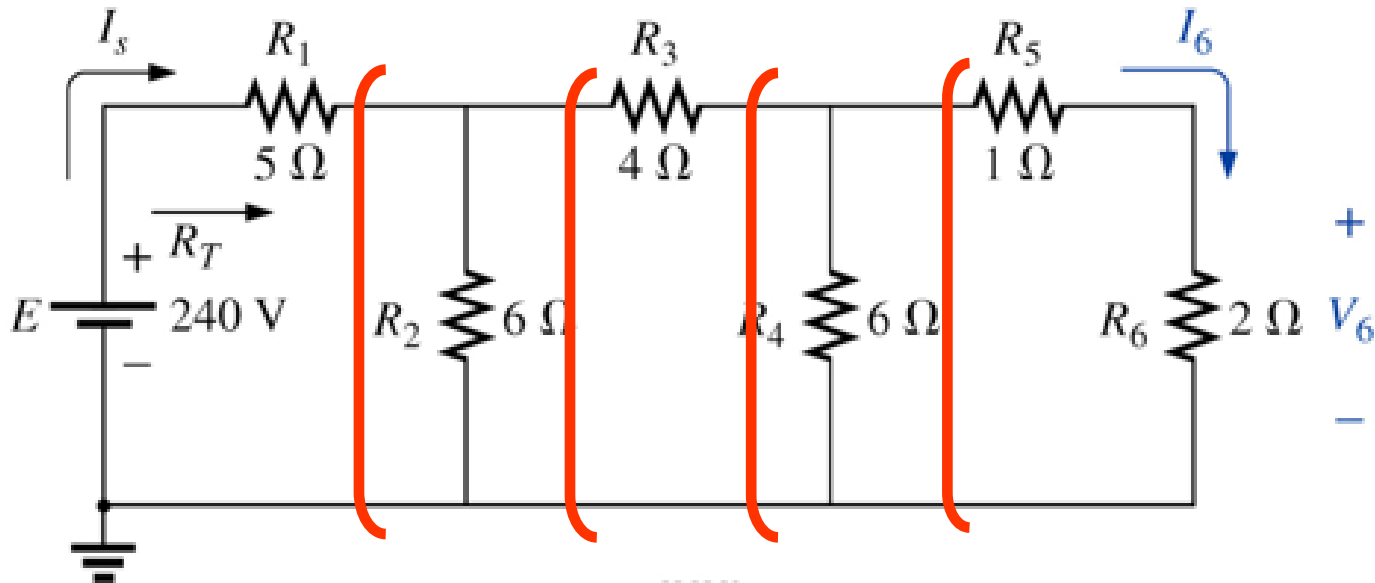

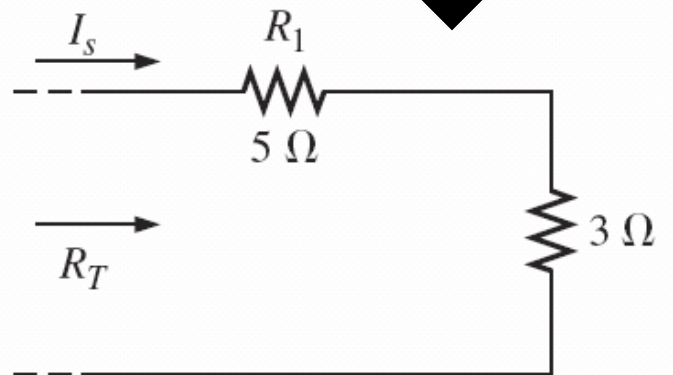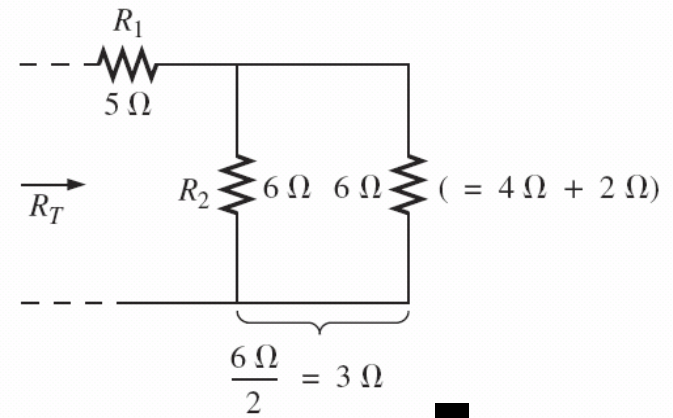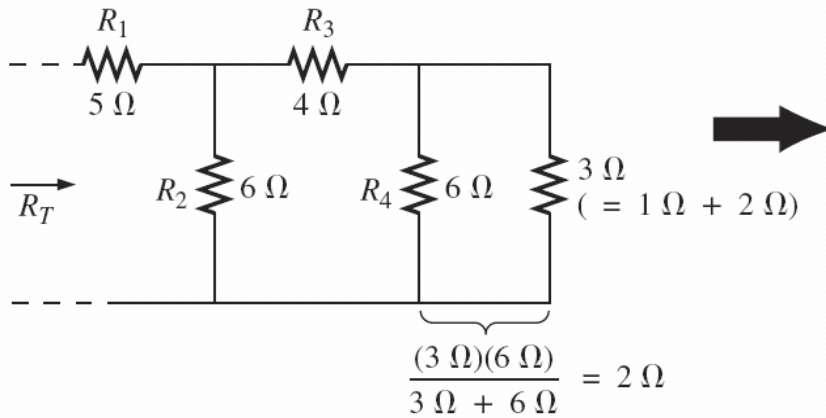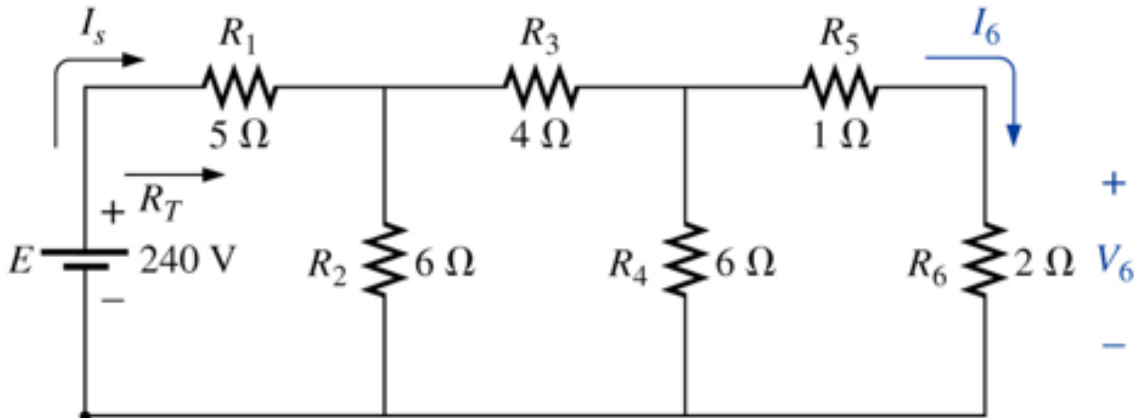Exp8: Calculate the indicated currents and voltage




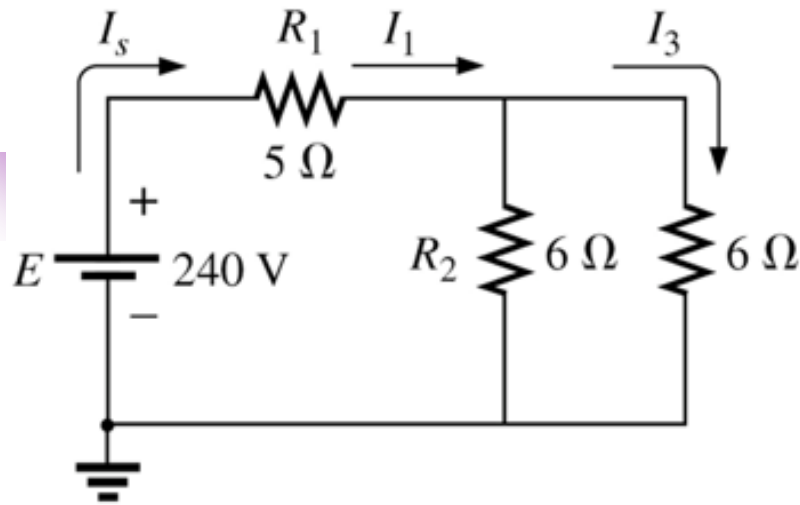$R_T = 5\ \Omega + 3\ \Omega = 8\ \Omega$
 $I_s = \frac{E}{R_T} = \frac{240\text{ V}}{8\ \Omega} = 30\ \text{ A}$



$$I_1 = I_s$$
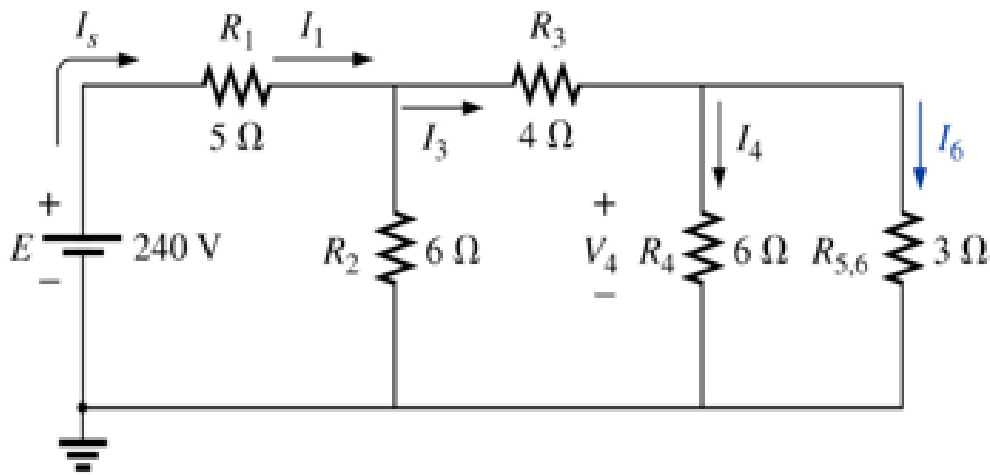
$$I_3 = \frac{I_s}{2} = \frac{30\text{ A}}{2} = 15\text{ A}$$



$$I_6 = \frac{(6\ \Omega) I_3}{6\ \Omega + 3\ \Omega} = \frac{6}{9} (15\text{ A}) = 10\text{ A}$$

$$V_6 = I_6 R_6 = (10\text{ A})(2\ \Omega) = 20\text{ V}$$