

Midterm Review

EMT1150

Introduction to Circuit Analysis

Department of Computer
Engineering Technology



Fall 2018


Prof. Rumana Hassin Syed



Key points

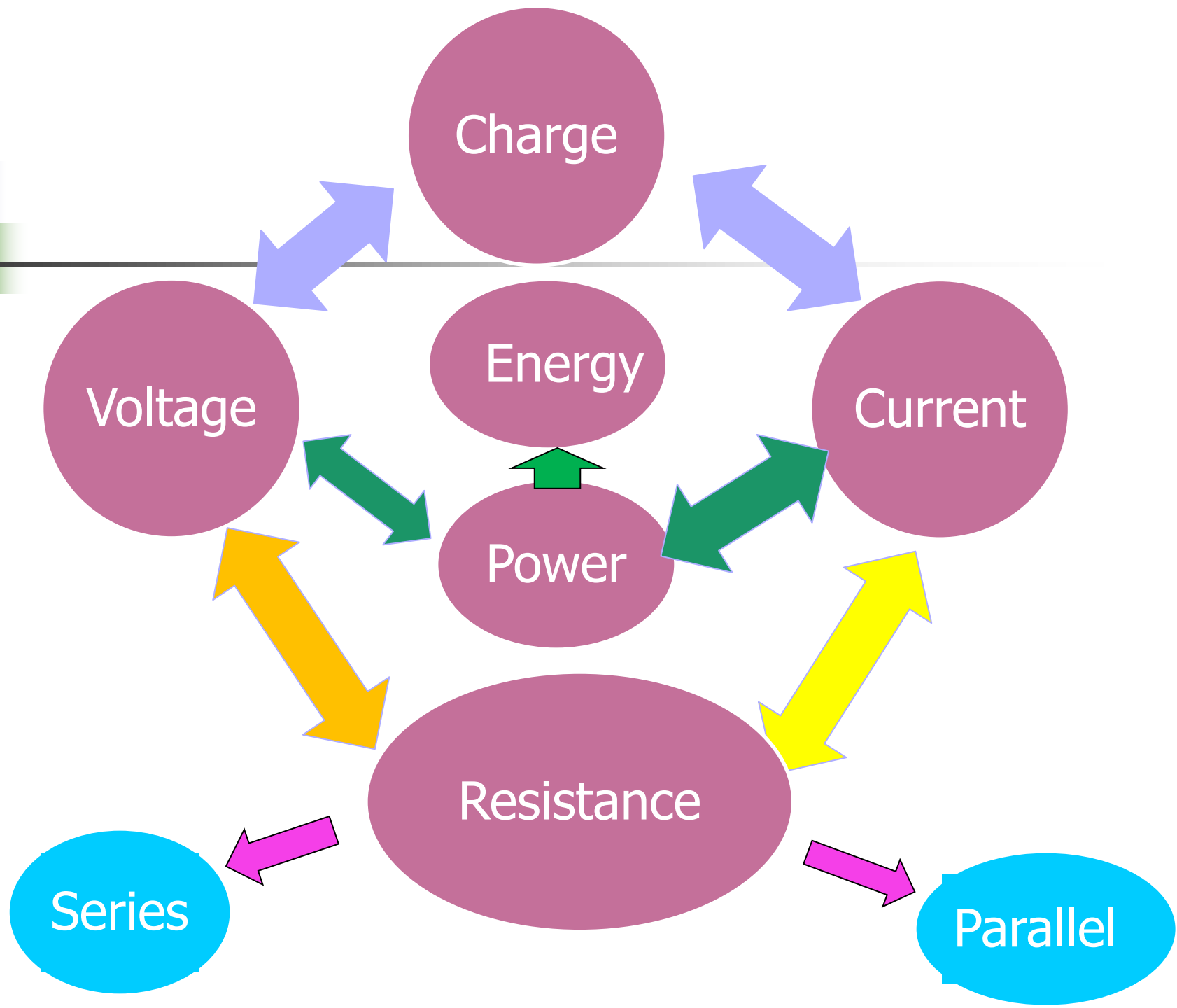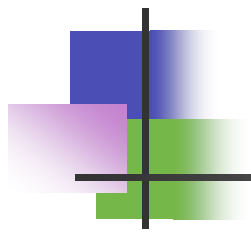- Basic concept
 - Unit, unit conversion, notations, power of ten
 - Current, voltage, power, energy
- Resistance
 - Measurements,
 - Ohm's law
- Parallel and series circuit
 - Total resistance
 - Circuit analysis, CDR, VDR
 - KCL, KVL



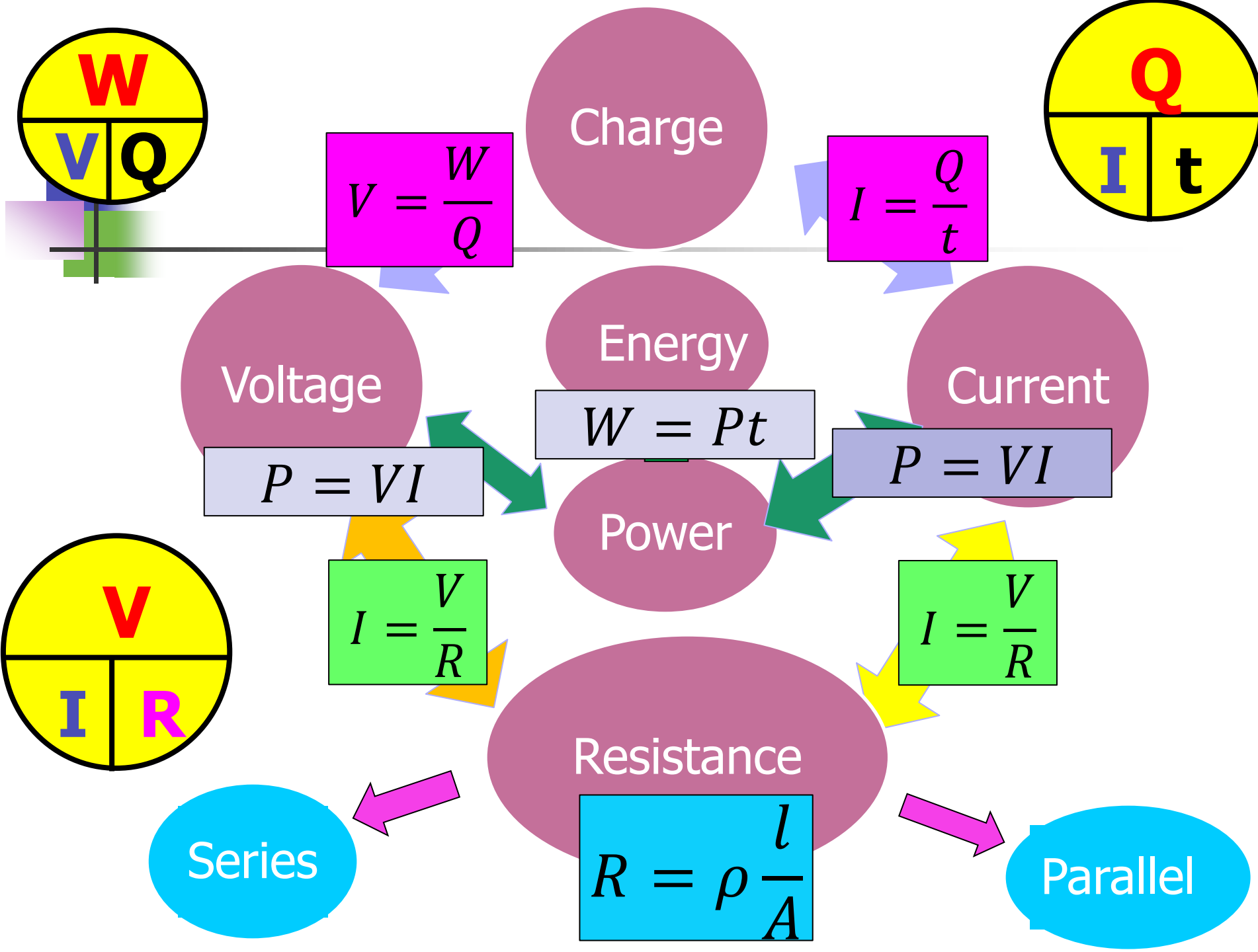



Parallel and series circuit

	Series	Parallel
Definition	One node in common and same current	Two nodes in common
Equivalent resistance	$R_T = R_1 + R_2 + \dots + R_N$	$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$ $G_T = G_1 + G_2 + G_3 + \dots + G_N$
V & I	same current, voltage depends Ohm's law	same voltage, current depends Ohm's law
Rules	Voltage divider: $V_i = E \left(\frac{R_i}{R_T} \right)$	Current divider: $I_i = I \left(\frac{R_T}{R_i} \right)$
Kirchhoff's Law	KVL, closed path, $\sum V_i = 0$	KCL, single node, $\sum I_{in} = \sum I_{out}$