

# Lecture 11

**EMT1150**

## **Introduction to Circuit Analysis**

---

Department of Computer  
Engineering Technology

Fall 2018

Prof. Rumana Hassin Syed




# Chapter11 Inductors



---

- Introduction to Inductors
- The magnetic Field
- Inductance
- Inductors in Series and Parallel
- R-L Transients

# Introduction

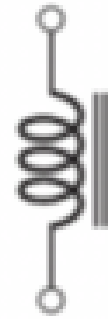

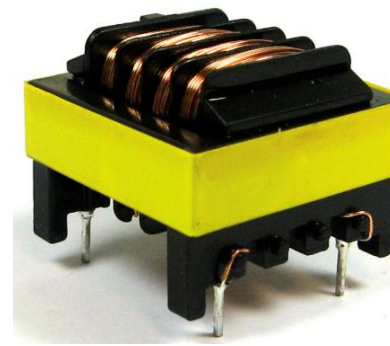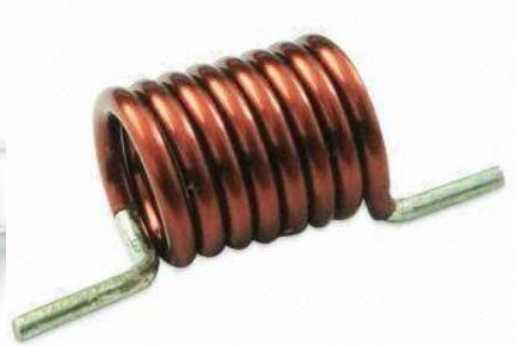- Always compare with resistors
- Always compare with capacitors
- Two-terminal device
- Symbol



RF Inductors/ Choke 2.2uH







# Intro Contd..

---





- Inductor **does not dissipate energy** as does the resistor but **store it**.
- Inductor stores energy in the form of **magnetic field**, but capacitor stores energy in the form of **electric field**.
- Inductor displays its true characteristics only when **a change** in the voltage or current is made in the network.
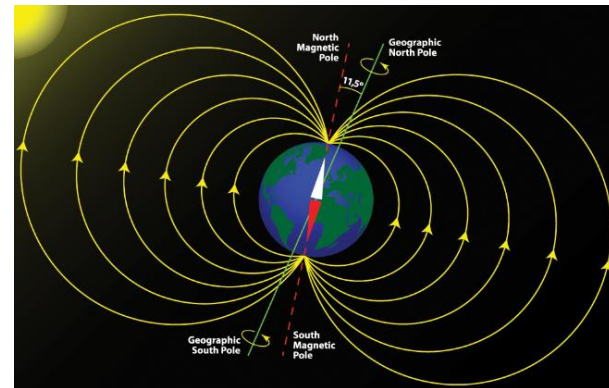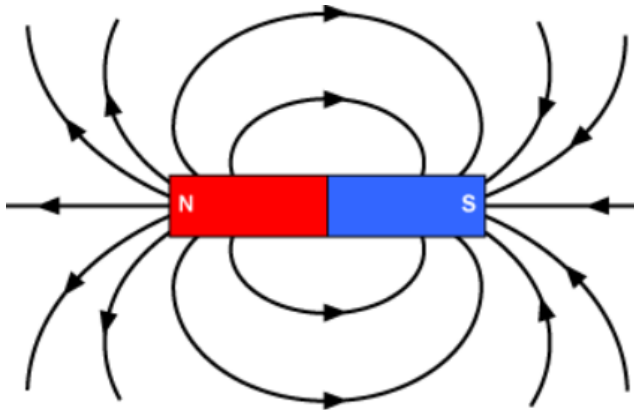
# Magnetic field

- A magnetic field is the magnetic effect of **magnetic materials** and **electric currents**.
- It is represented by **magnetic flux lines**, which indicate the strength of the magnetic field at any point around any charged body.
- The denser the lines of flux, the stronger is the magnetic field.



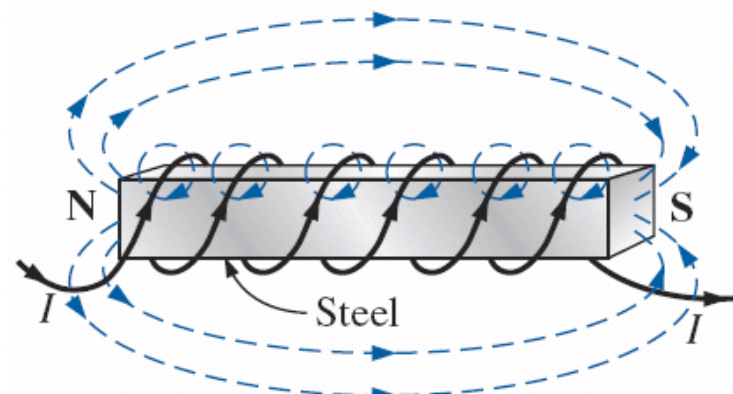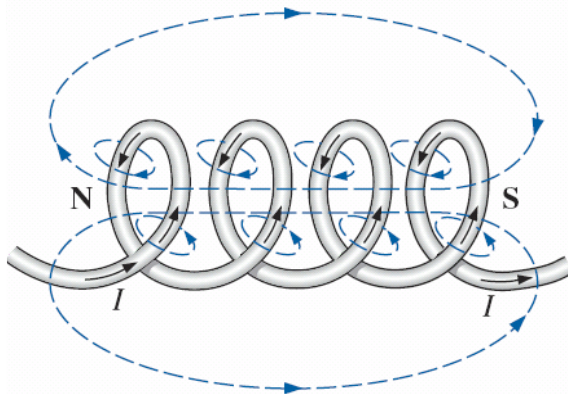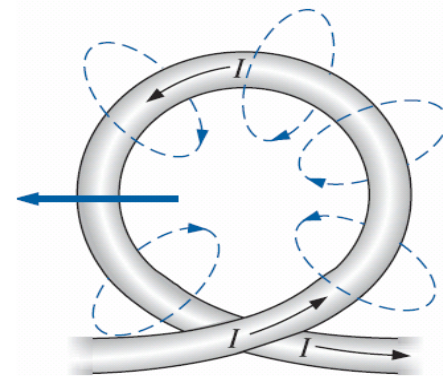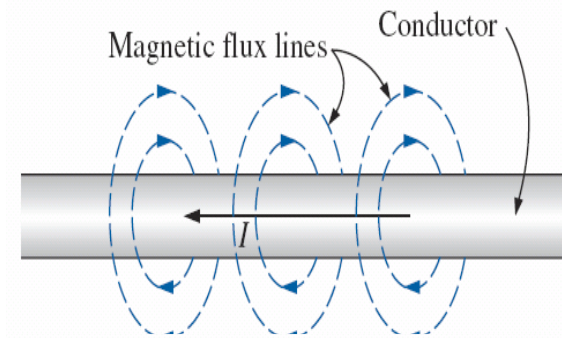- Magnetic effect induced by flow of charge or charges are called electromagnetism.
- The direction of the magnetic flux lines follow the right hand rule.
- Electromagnet





- Magnetic field is measured by magnetic flux density.

$$B = \frac{\phi}{A}$$

$\phi$ : Magnetic flux, Webers (Wb)



A: Area, m<sup>2</sup>

B: Flux density, Tesla (T)

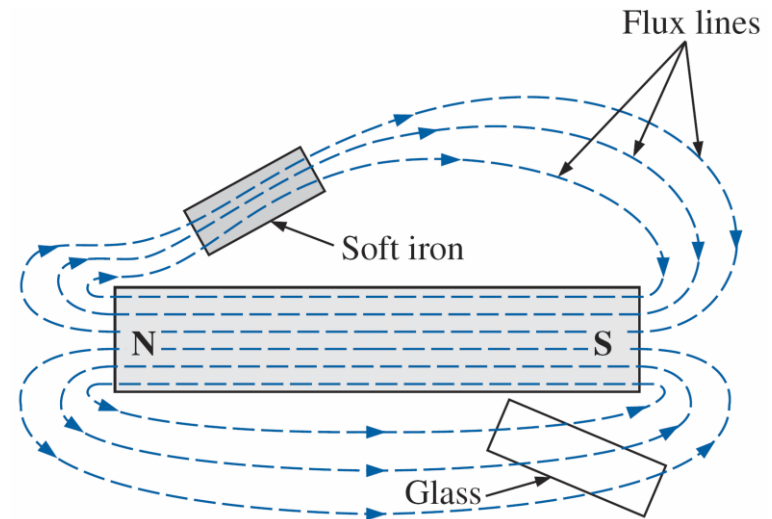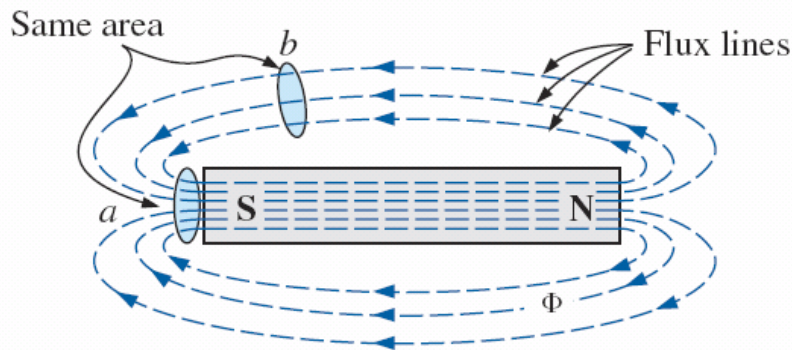
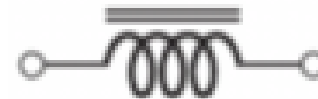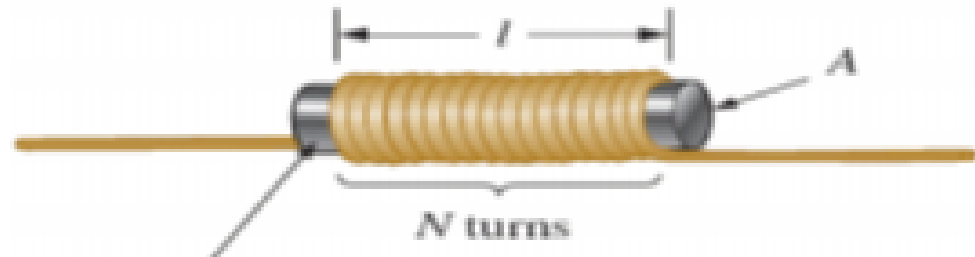
# Inductor

- An inductor can set up a strong magnetic field.
- The structure of inductor consists of a coil of conducting material, typically insulated copper wire, wrapped around a core, either of air, plastic material or a ferromagnetic material.





**Inductance** (L) is a measure of a inductor's ability to store energy in its coils.

Unit: **Henry** (H)

**Inductance** is a measure of the amount of magnetic flux produced for a given electric current.

$$L = \frac{\phi}{i}$$

$\phi$  : magnetic flux, Webbers (Wb)

$i$ : current, Amperes (I)

L: Inductance, Henry (L)

$$L = \frac{d\phi}{di}$$

For general case, with ferromagnetic core



# Inductance

■ The inductance of any inductor is due primarily to four factors:

- Magnetic Permittivity (core material)
- Length of wire
- Area within the coil
- Number of turns

$$L = \frac{\mu N^2 A}{l}$$

L: Henry(H)


$\mu$  : Magnetic Permittivity (Wb/Am)

N: number of turns

A: m<sup>2</sup>

l: m

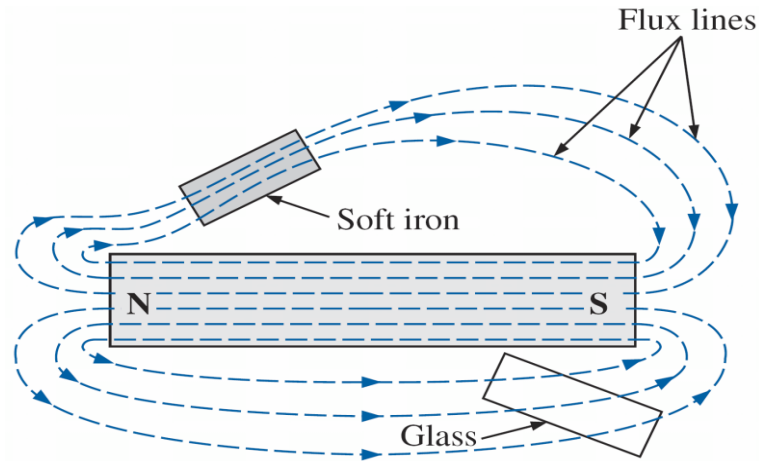- **Magnetic Permittivity** is the measure of the ease with which magnetic flux lines can be established in the material.




- In general, magnetic permeability of other materials can compare to the magnetic permeability of air.

$$\mu_r = \frac{\mu}{\mu_0}$$



$$\mu_0 = 4\pi \times 10^{-7} \text{ Wb/Am}$$

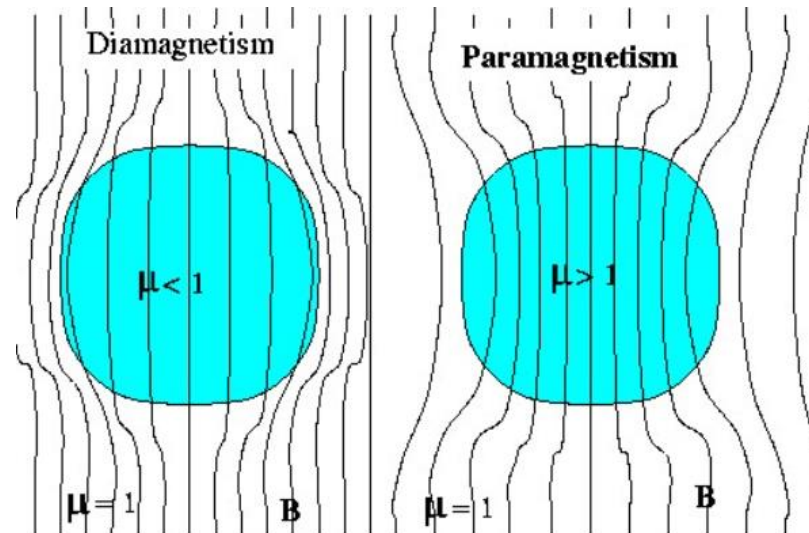- If  $\mu_r$  is slightly less than 1, materials are called **diamagnetic**, such as wood, glass.
- If  $\mu_r$  is slightly greater than 1, materials are called **paramagnetic**, such as copper, aluminum.
- If  $\mu_r$  is hundreds or thousands larger than 1, materials are called **ferromagnetic**, such as iron.





$$L = \frac{\mu_r \mu_0 N^2 A}{l}$$

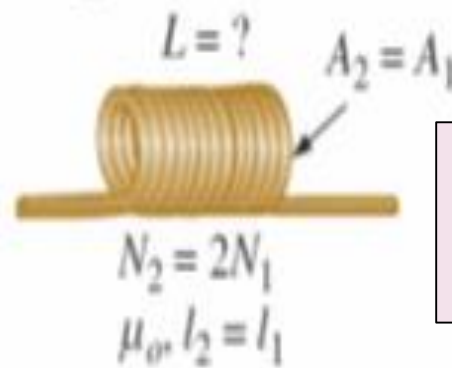
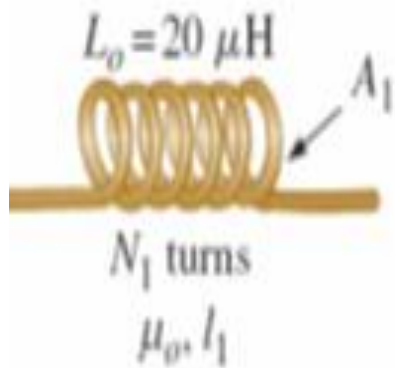
# Example 1: Determine the inductance on the right side.


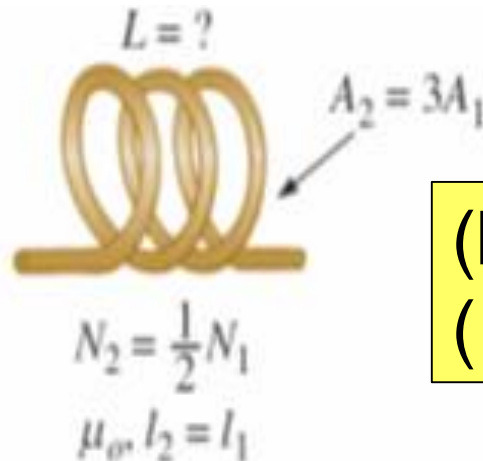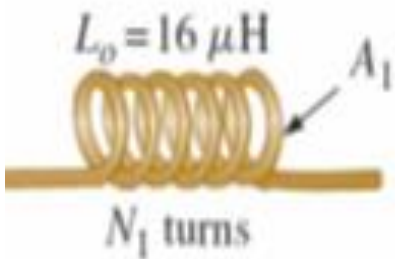
$$(a) L = 2^2 \times (20 \mu\text{H}) = 80 (\mu\text{H})$$



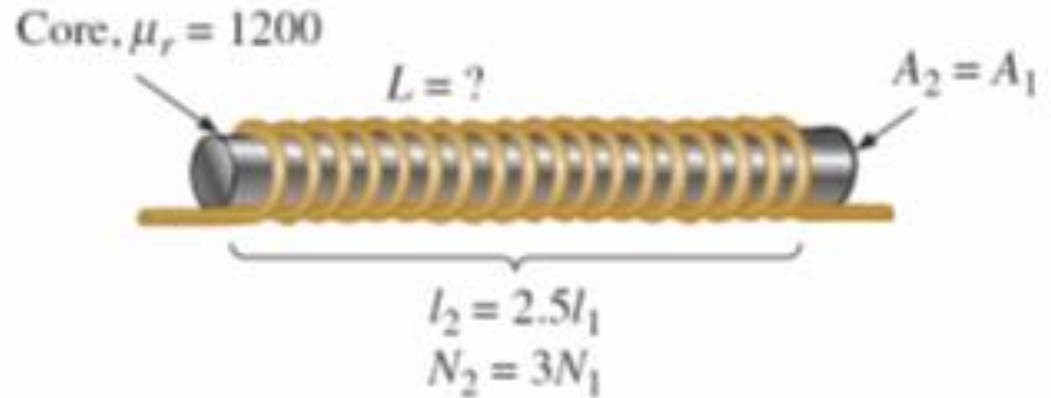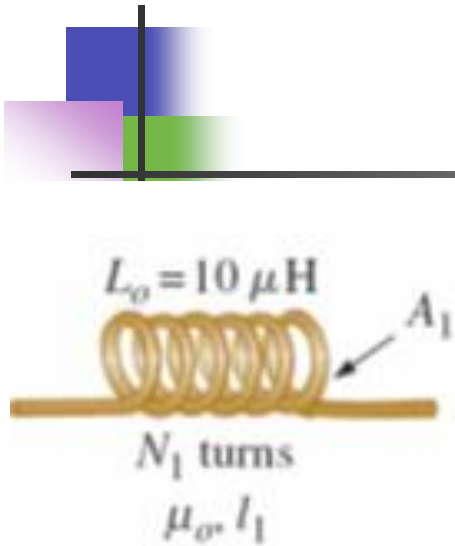
$$(b) L = 3 \times \left(\frac{1}{2}\right)^2 \times (16 \mu\text{H}) = 12 (\mu\text{H})$$



$$(c) \quad L = 1200 \times 3^2 \times (10 \mu\text{H}) / 2.5 \\ = 43200 (\mu\text{H}) = 43.2 \text{ mH}$$

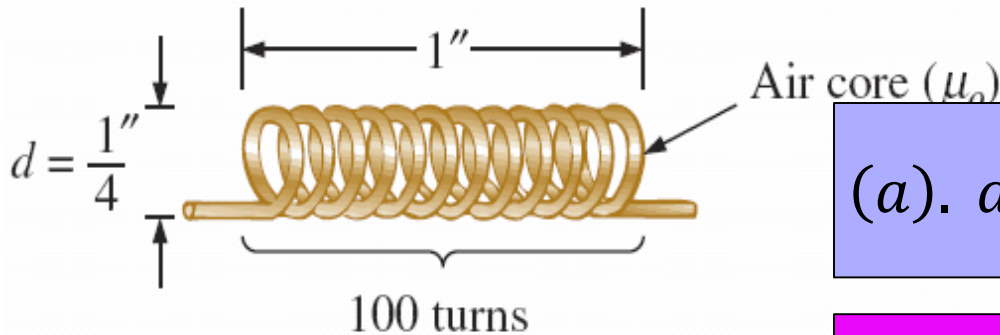**Example2:** (a) Find the inductance of inductor.  
 (b) If the metal core with  $\mu_r = 2000$  is used, find the inductance.



$$(a). d = \frac{1}{4} \text{ in} \left( \frac{1 \text{ m}}{39.37 \text{ in}} \right) = 6.35 \text{ (mm)}$$

$$A = \frac{\pi d^2}{4} = \frac{\pi (6.35 \text{ mm})^2}{4} = 31.67 \mu\text{m}^2$$

$$l = 1 \text{ in} \left( \frac{1 \text{ m}}{39.37 \text{ in}} \right) = 25.4 \text{ (mm)}$$


$$L = \frac{\mu_r \mu_0 N^2 A}{l} = \frac{4\pi \times 10^{-7} \times 100^2 \times 31.67}{25.4} = 15.68 \text{ (}\mu\text{H)}$$

$$(b). L = \frac{\mu_r \mu_0 N^2 A}{l} = 2000 \times 15.68 = 31.36 \text{ (mH)}$$

# Type of inductors

- Fixed inductor
  - *Air-core inductors*
  - *Toroid coil*
  - Phenolic (resin or plastic core)
  - Ferrite core inductor


- Variable Inductor

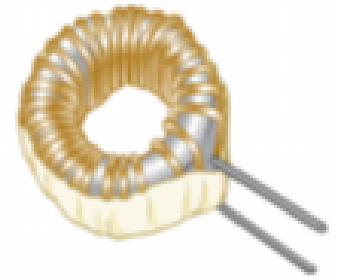

1  $\mu$ H  
350 mA,  $R_{dc} = 6 \Omega$



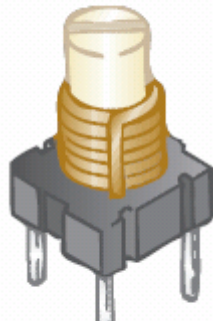100,000  $\mu$ H = 100 mH  
11 mA,  $R_{dc} = 0.7 \text{ k}\Omega$







# Properties of an Inductor


---

- Acts like an short circuit at **steady state** when connected to a DC voltage or current source.
- **Current through an inductor must be continuous**
  - There are no abrupt changes to the current, but there can be abrupt changes in the voltage across an inductor.
- An ideal inductor does not dissipate energy, it takes power from the circuit when storing energy and returns it when discharging.


# Faraday's Law

- Any **change** in the magnetic field of a coil will cause a voltage to be "induced" in the coil.
- The induced effect always oppose the cause that produced it

$$v_L = L \frac{di_L}{dt}$$

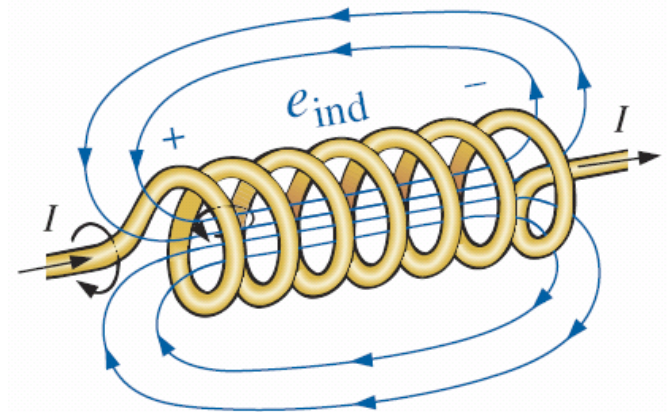

# Inductors in Series

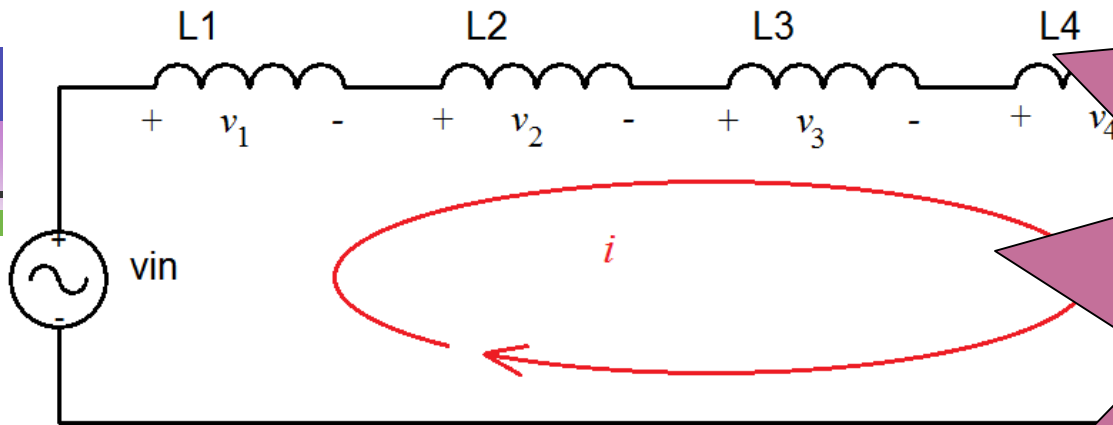

Similar format to series-connected resistor

Apply KVL to CP

$$v_{in} = v_1 + v_2 + v_3 + v_4$$


$$v_1 = L_1 \frac{di}{dt}$$

$$v_{in} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt} + L_4 \frac{di}{dt}$$

$$v_{in} = L_T \frac{di}{dt}$$

$$L_T = L_1 + L_2 + L_3 + L_4$$

# Inductors in parallel

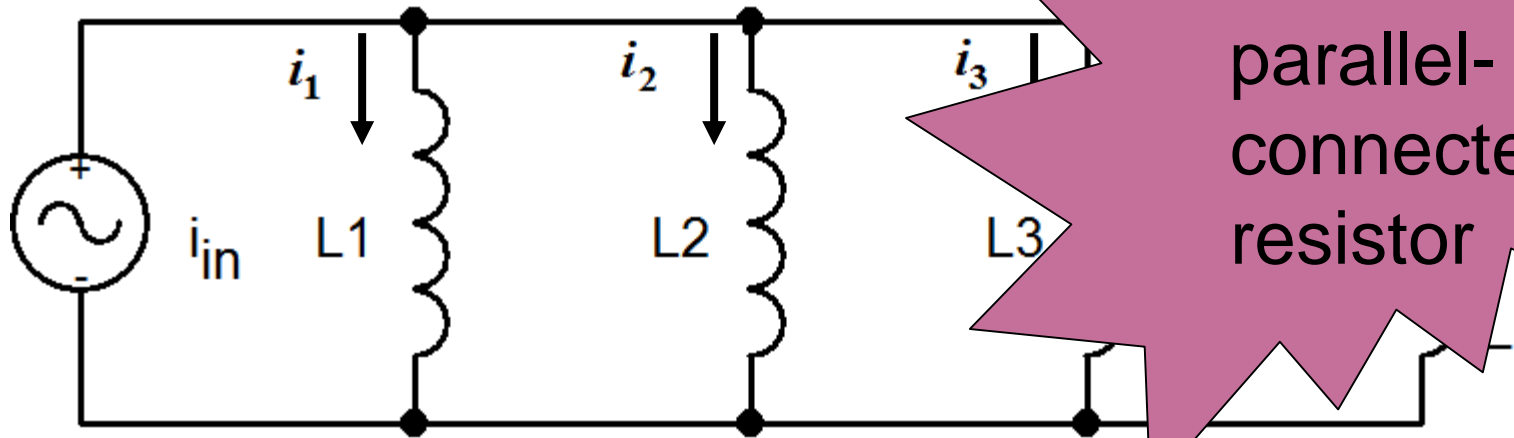


Similar  
format to  
parallel-  
connected  
resistor

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \frac{1}{L_4}$$

$$L_T = \frac{L_1 L_2}{L_1 + L_2}$$
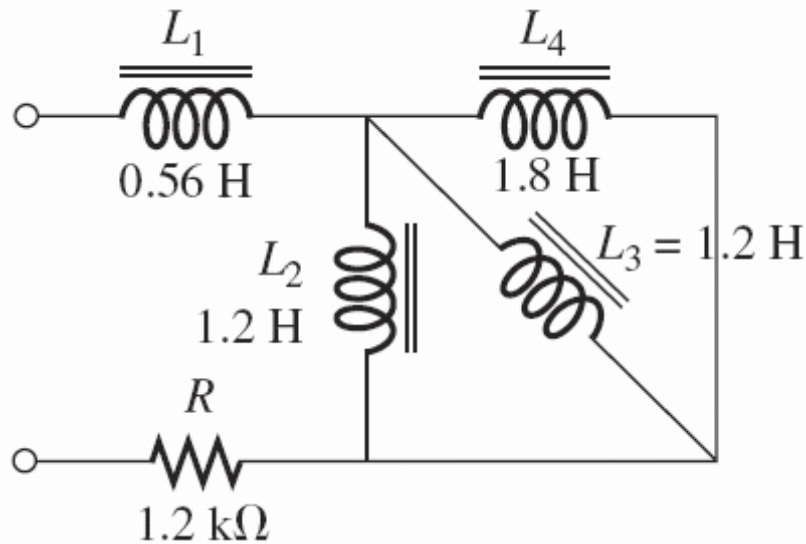
### Example 3: Reduce the network to its simplest form.




$$\frac{1}{L'_T} = \frac{1}{L_2} + \frac{1}{L_3} + \frac{1}{L_4}$$

$$\frac{1}{L'_T} = \frac{1}{1.8H} + \frac{1}{1.2H} + \frac{1}{1.2H}$$

$$L'_T = 0.45H$$

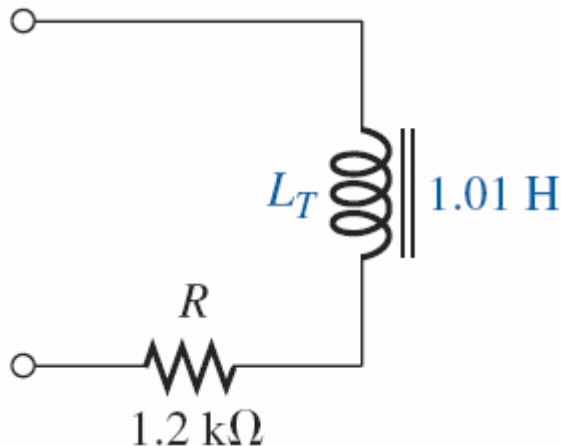
$$L_T = L'_T + L_1 = 0.56H + 0.45H = 1.01H$$





# Transients in RL Networks
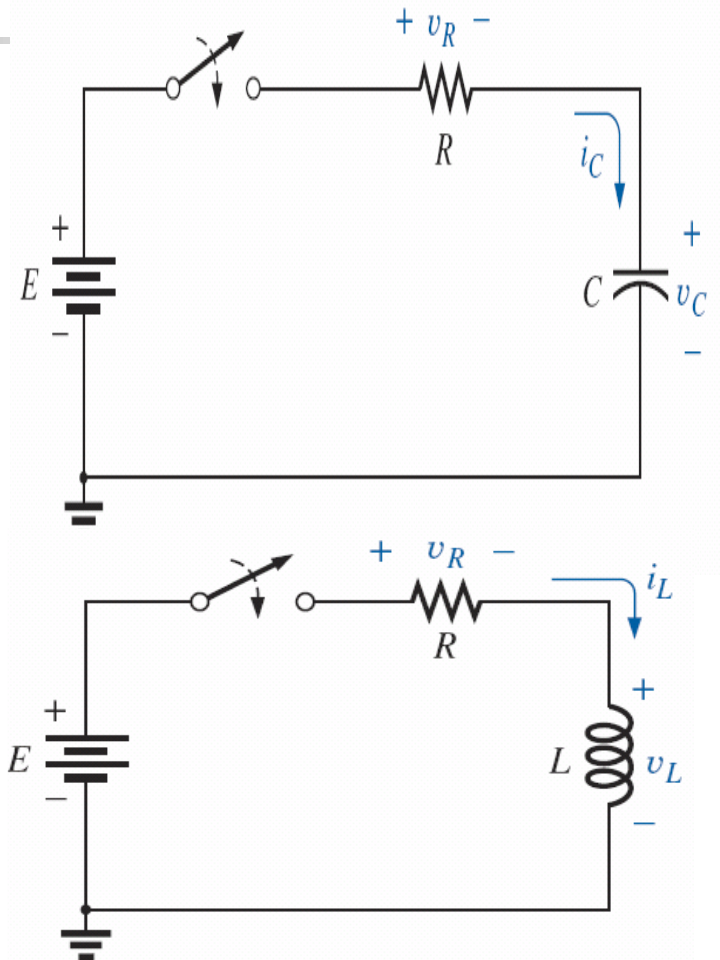
## Storage phase


- similarities exist between the analyses of inductive and capacitive networks.
- The behavior for the voltage of a capacitor is the same for the current of an inductor



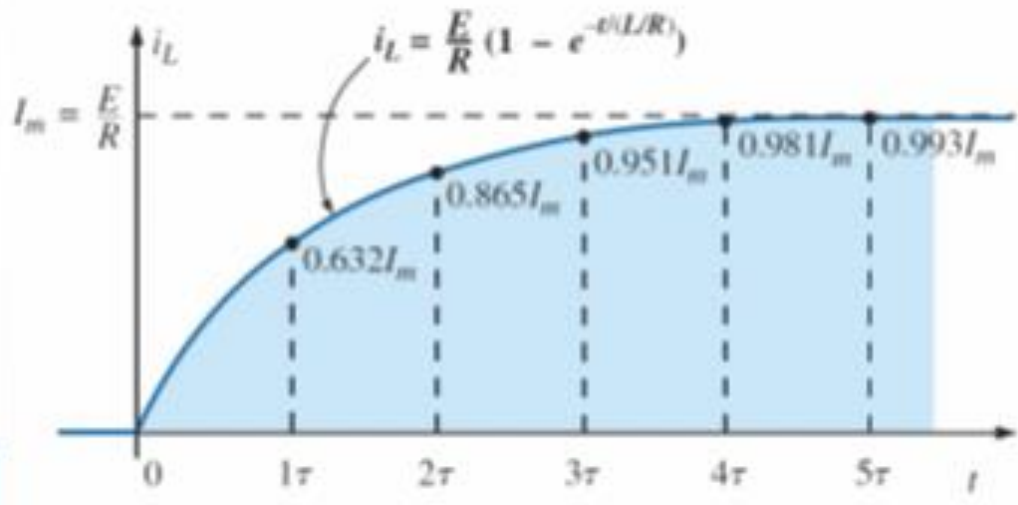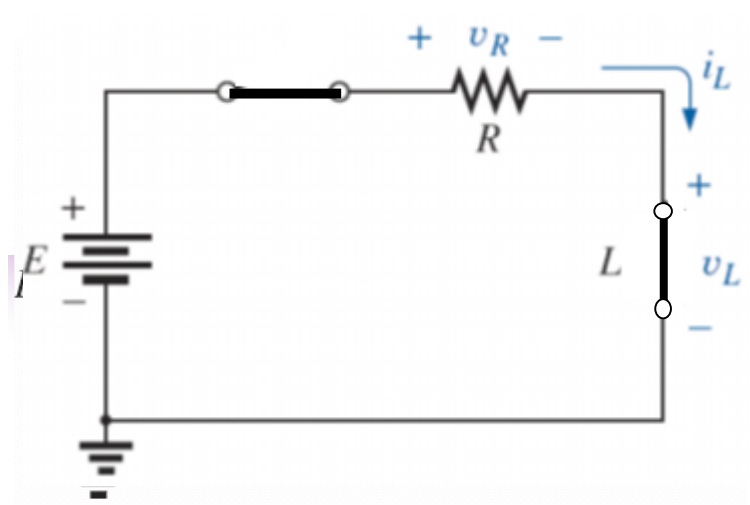

$$i_L = \frac{E}{R} (1 - e^{-t/\tau})$$


$$\tau = \frac{L}{R}$$

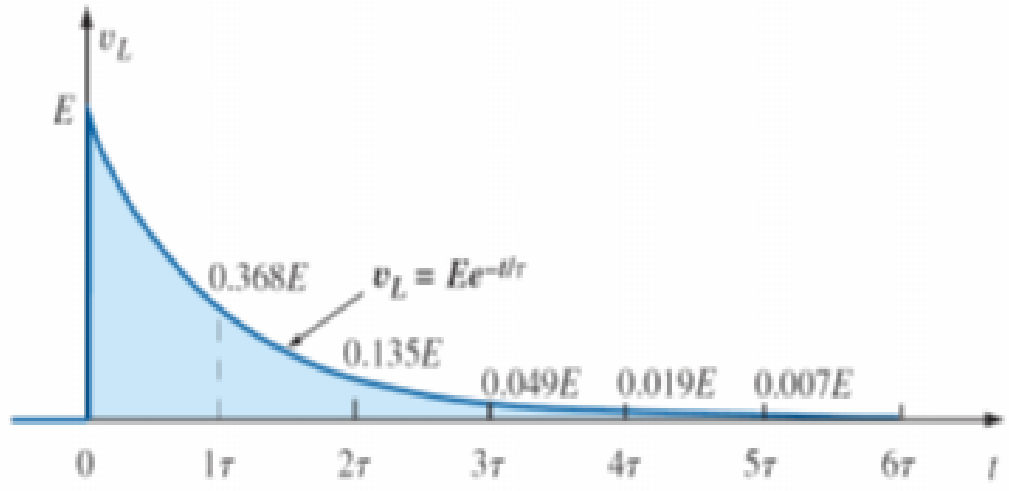

$$v_L = Ee^{-t/\tau}$$



(b)

# Release phase

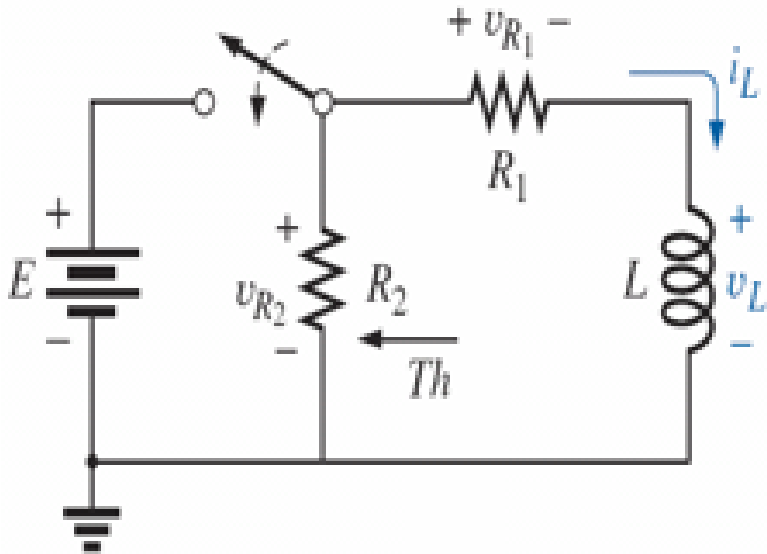


$$i_L = \frac{E}{R_1} e^{-\frac{t}{\tau'}}$$


$$\tau' = \frac{L}{R_1 + R_2}$$

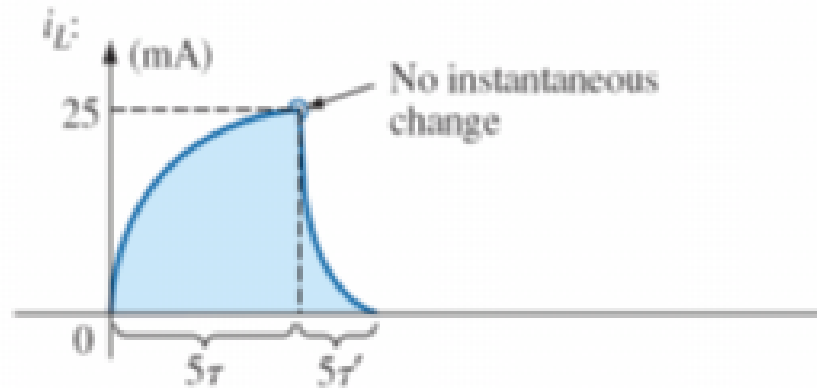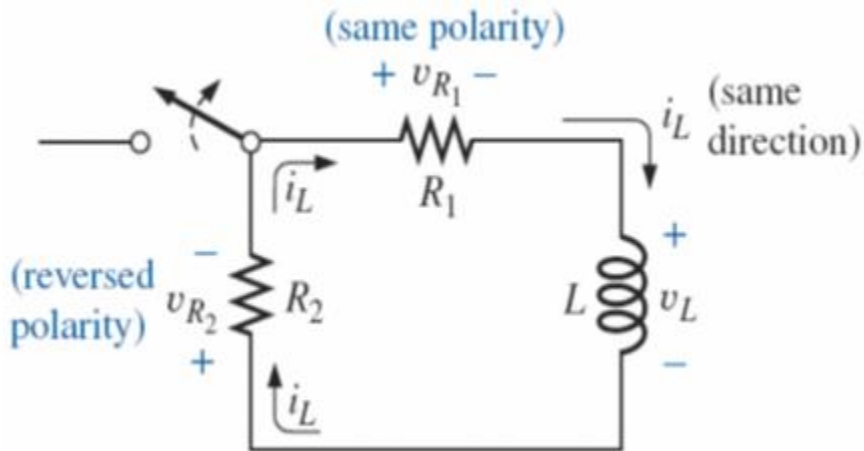



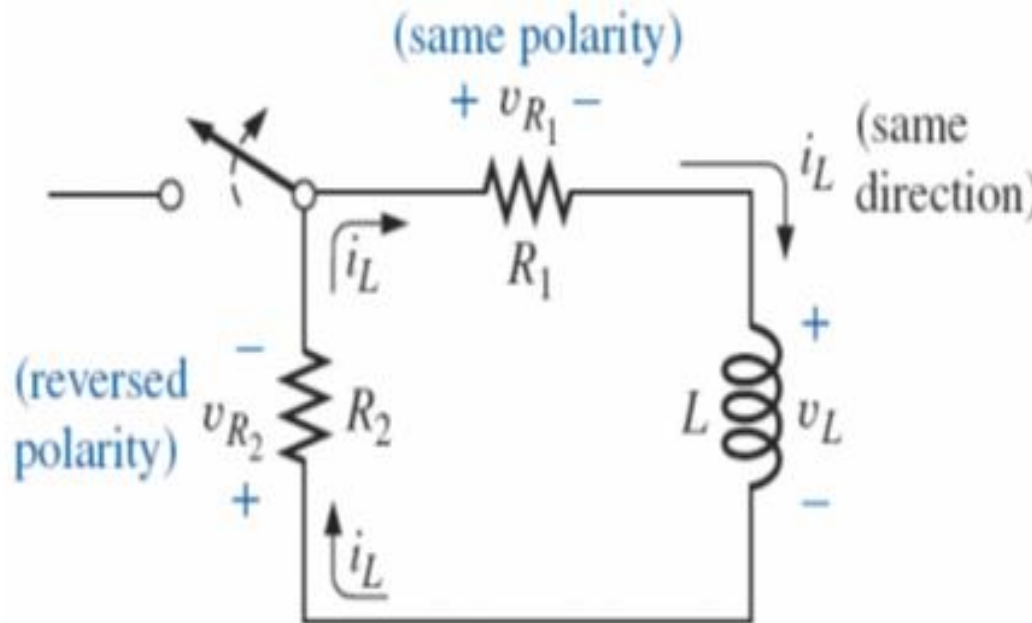
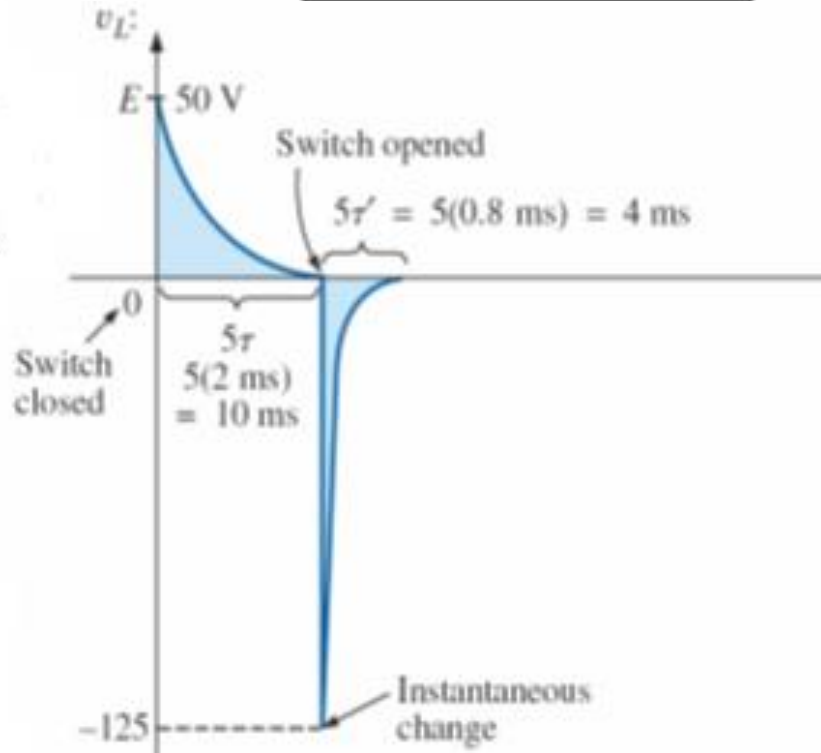
$$\begin{aligned}
 v_L &= -(v_1 + v_2) \\
 &= -i_L(R_1 + R_2) \\
 &= -\frac{E}{R_1}(R_1 + R_2) \\
 &= -\left(1 + \frac{R_2}{R_1}\right)E
 \end{aligned}$$



$$v_L = -\left(1 + \frac{R_2}{R_1}\right)Ee^{-\frac{t}{\tau'}}$$