

Student First Name: _____ Last name EMPLID _____ Session Number _____.

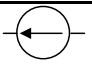
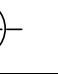
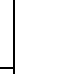

Please submit this page with your answer and question sheets

Must circle the correct answer on the answer sheet.

1. A B C D	10. A B C D	19. A B C D
2. A B C D	11. A B C D	20. A B C D
3. A B C D	12. A B C D	21. A B C D
4. A B C D	13. A B C D	22. A B C D
5. A B C D	14. A B C D	23. A B C D
6. A B C D	15. A B C D	24. A B C D
7. A B C D	16. A B C D	25. A B C D
8. A B C D	17. A B C D	26. A B C D
9. A B C D	18. A B C D	

Student First Name: _____ Last name EMPLID _____ Session Number _____.

1. Which of the following is AC voltage source?

A	
B	
C	
D	

2. Capacitor is measured in

A	Watts
B	Ohms
C	Farads
D	Henries

3. What is 1,780.5 kJ in engineering notation?

A	$1.7805 \times 10^6 \text{ J}$
B	$1.7805 \times 10^4 \text{ J}$
C	$1780.5 \times 10^3 \text{ J}$
D	1.7805 MJ

4. Thevenin's Theorem can be applied only to:

A	Resistive circuits
B	Capacitive circuits
C	Inductive Circuits
D	All of the above

5. Based on 4 band resistor color chart, find the **value and tolerance** in which a resistor has the following color bands to satisfy the manufacturer's tolerance
 1st band 2nd band 3rd band 4th band
 red brown yellow gold

A	214k Ohm ±5%
B	120k Ohm x 5%
C	210k Ohm ±5%
D	2100 Ohm x5%

4 band resistor color chart		
color	Band value	tolerance
Black	0	
Brown	1	1%
Red	2	2%
Orange	3	3%
Yellow	4	4%
Green	5	0.5%
Blue	6	0.25%
Gold		5%
Silver		10%

6. A student measures resistance with a Digital Mutimeter (Volt/Amp/Ohm Meter). He places this Mutimeter on an ohmmeter setting x200kΩ. Then he takes a resistor with the following color bands:
 1st band 2nd band 3rd band 4th band
 brown black yellow gold


Which value is correct for his Ohmmeter reading to satisfy the manufacturer's tolerance? In your test procedure, show your work how you decide the correct answer (refer to **4 band resistor color chart above**)

A	200 kΩ
B	98.2 kΩ
C	92.5 kΩ
D	109 kΩ

Student First Name: _____ Last name EMPLID _____ Session Number _____


7. Resistors of $R_1 = 10k\Omega$, $R_2 = 1k\Omega$, $R_3 = 1k\Omega$, $R_4 = 10k\Omega$ are connected in combinational circuit to a 12-Volt supply V_s . Choose correct answer.

A	R_1 is in series with R_4
B	R_1 is in parallel with R_2
C	R_1 is in series with R_3
D	R_1 is in parallel with R_3

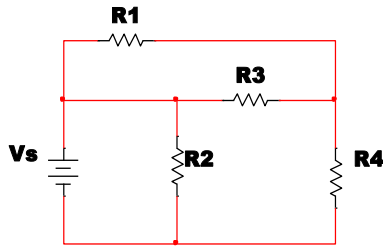


8. Find the voltage V_1 for the network below

A	2V
B	4V
C	6V
D	24V

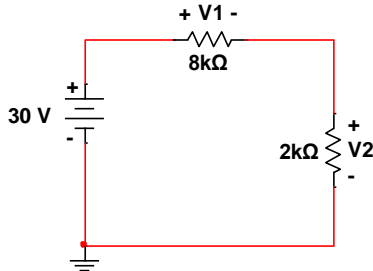


9. How much resistance is needed to limit the current from a $V_s = 110V$ source to 20mA?

A	5.5kΩ
B	550Ω
C	55 kΩ
D	550 kΩ

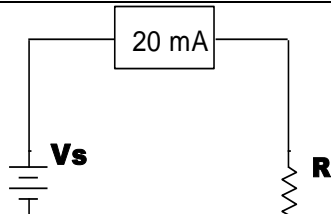


10. Determine current I_1 for the circuit below

A	1 A
B	2 A
C	4 A
D	6 A

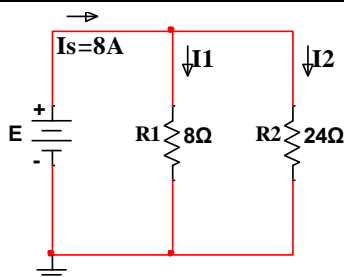


11. $I_s = 3.5$ mA. You measured I_2 to be 1 mA. What is current I_1 ?

A	1.5 mA
B	2.0m A
C	2.5mA
D	6 A

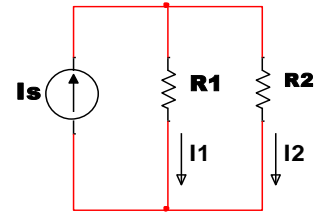


12. For the network, $R_1 = 3.0$ kΩ, $R_2 = 3.0$ kΩ, $R_3 = 6.0$ kΩ, $R_4 = 6.0$ kΩ. What is the total resistance R_{AB} between A and B?

A	2.0 kΩ
B	9.0 kΩ
C	1.5 kΩ
D	3.0kΩ

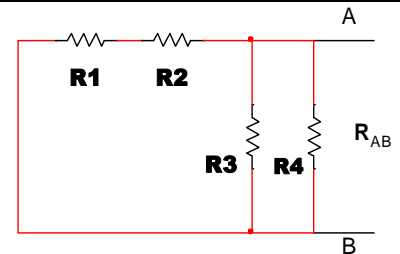

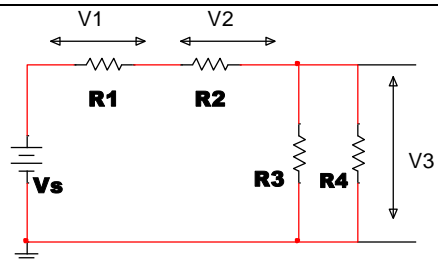13. A voltage source $V_s = 6.0V$, two resistors are equal $R_1 = R_2$, $R_3 = R_4$, and the voltage between A and B (V_3 across R_3 and R_4) is 2.2V. What are the voltage V_1 and V_2 ?




A	$V_1 = 3.8V$, $V_2 = 3.8V$
B	$V_1 = 1.1V$, $V_2 = 1.1V$
C	$V_1 = 1.9V$, $V_2 = 3.8V$
D	$V_1 = 1.9V$, $V_2 = 1.9V$

Show your work here

Student First Name: _____ Last name EMPLID _____ Session Number _____


14. Assume a resistor R is rated for 2W (2 Watts). What is the maximum voltage can be applied to the resistor R to without exceeding its power rating.

A	110V
B	220 V
C	100 V
D	40 V

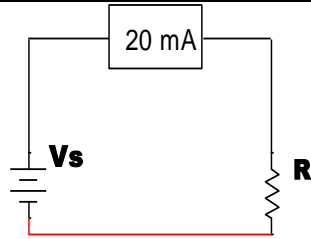


15. Three equal resistors of 1000 ohms each ($R_1 = R_2 = R_3$) are connected in series to a $V_s = 60V$ power supply. If one of the resistors is shorted, the total resistance and current is:

A	3k Ω , 20 mA
B	1k Ω , 60 mA
C	2k Ω , 30 mA
D	1.5k Ω , 40 mA

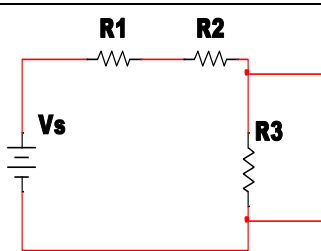


16. For the network below, what is the voltage source E that has to be applied to this circuit?

A	30 V
B	21 V
C	21 mV
D	30 mV

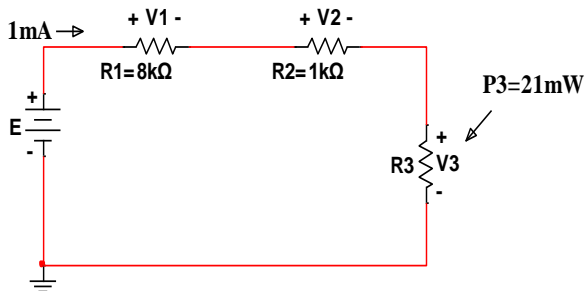


17. For the network below, $R_1=9M\Omega$, the total resistance ($R_T = R_1//R_2$) is $6M\Omega$, and the power dissipated by R_2 is $81kW$. What is the resistance of R_2 ?

A	3 M Ω
B	6 M Ω
C	9 M Ω
D	18 M Ω

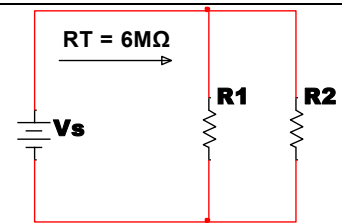


18. $L_1 = 4.0$ mH, $L_2 = 2.0$ mH, $L_3 = 1.0$ mH. What is the total inductance between A and B?

A	7.0 mH
B	1,7 mH
C	3.0 mH
D	4.7 mH

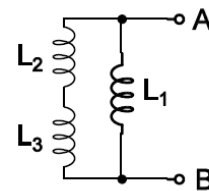

19. Three capacitors, namely $C_1=3\mu F$, $C_2=2\mu F$, and $C_3=20\mu F$, are connected to $E=50$ -volt supply. What is the voltage across $20\mu F$ capacitor C_3 ?

A	50 V
B	40 V
C	10 V
D	6.3 V

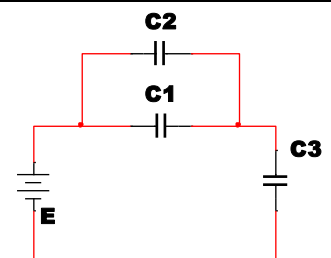


Show your work here.

Student First Name: _____ Last name EMPLID _____ Session Number _____

20. For the sinusoidal signal, the time period of the waveform is 4ms as shown in Figure, what is the frequency of the waveform?

A	0.25 kHz
B	1 kHz
C	4 kHz
D	10 kHz

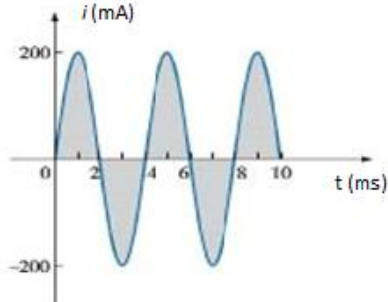


21. Given the AC current source in a circuit $i(t) = 100 \sin(120\pi t)$ (mA), where t is a time in the unit of ms . What is the amplitude of the AC current?

A	200mA
B	100mA
C	70.7mA
D	141.4mA

22. $R_1 = R_2 = 2.0 \text{ k}\Omega$, $R_3 = 1.5 \text{ k}\Omega$, $R_4 = 2.5 \text{ k}\Omega$, and $V_s = 10.0 \text{ V}$. What is the voltage V_{AC} ?


A	2.0V
B	5.0V
C	10V
D	2.5V

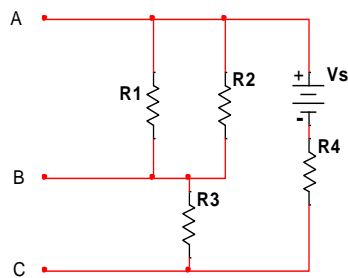

Show your work here. You can use a calculator.

23. $R_1 = R_2 = 2.0 \text{ k}\Omega$, $R_3 = 1.5 \text{ k}\Omega$, $R_4 = 2.5 \text{ k}\Omega$, and $V_s = 10.0 \text{ V}$. What is the current through R_1 ?


A	1.0 mA
B	5mA
C	2.0mA
D	4.0mA

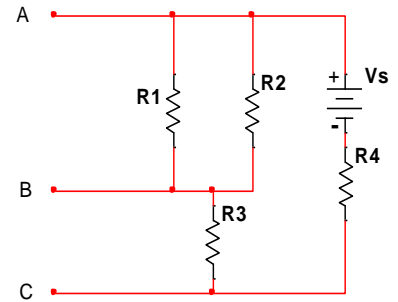

Show your work here. You can use a calculator.

24. $R_1 = R_2 = 2.2 \text{ k}\Omega$, $R_3 = 1.4 \text{ k}\Omega$, $R_4 = 3.5 \text{ k}\Omega$, and $V_s = 6.0 \text{ V}$. How much power is dissipated by resistor R_4 ?

A	1.4mW
B	3.5mW
C	1.1mW
D	2.2mW

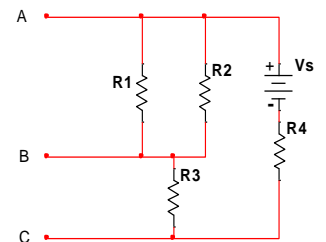


Show your work here. You can use a calculator.

Student First Name: _____ Last name EMPLID _____ Session Number _____.

25. What is the Thevenin voltage V_{th} in the Thevenin equivalent circuit for the network external to the resistor R for the network below?


A.	5 V
B.	20 V
C.	8 V
D.	6.75 V

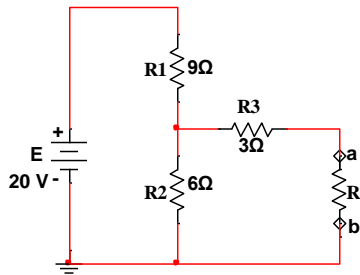

Show your work here including Thevenin equivalent circuit. You can use a calculator.

26. What is the R_{th} in the Thevenin equivalent circuit for the network external to the resistor R for the network below?

A.	3.6 Ω
B.	6.6 Ω
C.	6.0 Ω
D.	9 Ω

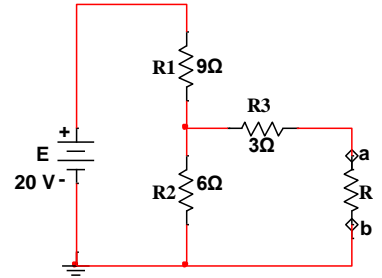

Show your work here including Thevenin equivalent circuit. You can use a calculator.