

TCET 2102 – Lesson 4

Matching networks

Outline

Inductor/Capacitor

Real/ideal

Reactance

Q – factor

Resonant circuits and circuit Q


Maximum power transfer

Matching


L-, T-, π -networks

Inductor

Ideal

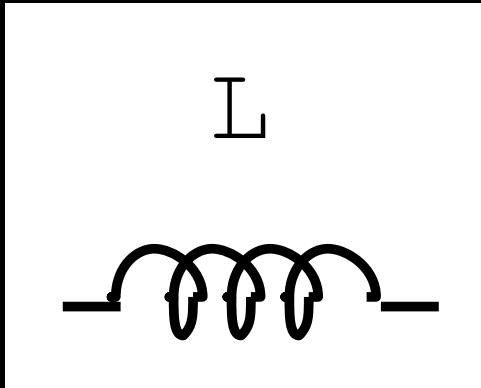


Real

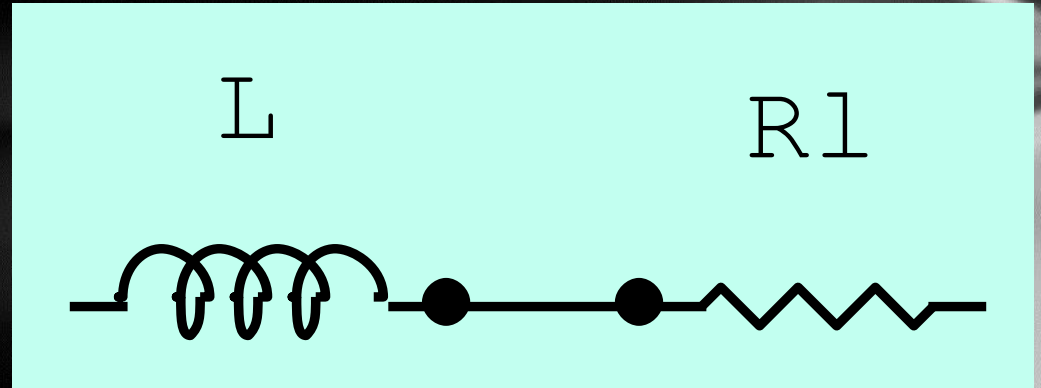

Capacitor


Ideal

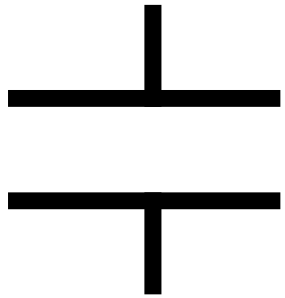

C



Real

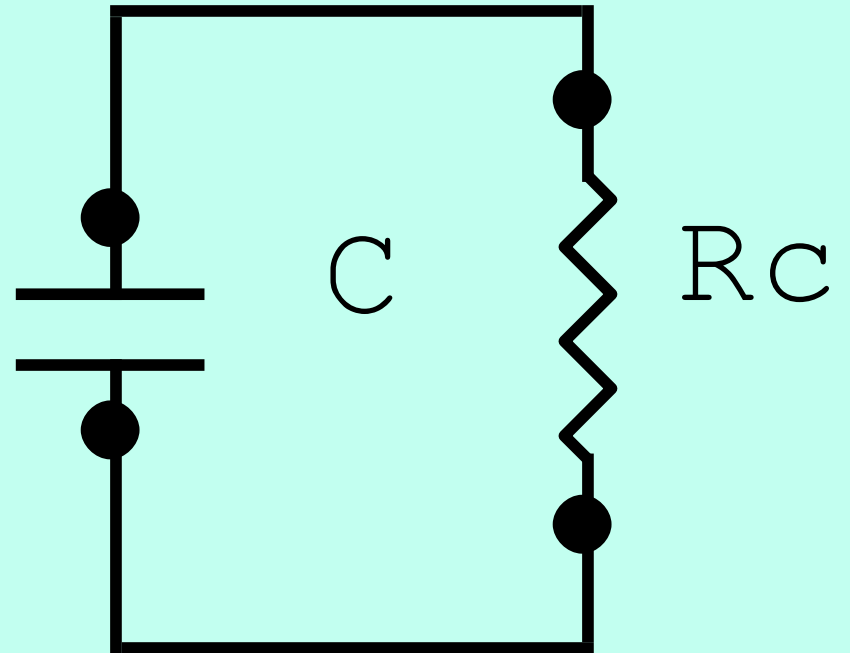

Reactance

$$X_L = j2\pi fL$$

$$X_C = 1/(j2\pi fC)$$

Describes how component reacts to changes in voltage/current.

Quality Factor (Q)

Q-factor: A ratio

$$Q = \frac{\text{reactive power}}{\text{average power}}$$


Can be found from the characteristics of any component.

Depends on how the resistive element is modeled, i.e. in series or in parallel with the ideal.


$$Q = \frac{X}{R_{series}} = \frac{R_{parallel}}{X}$$

Resonant Circuits

RLC tuned circuits

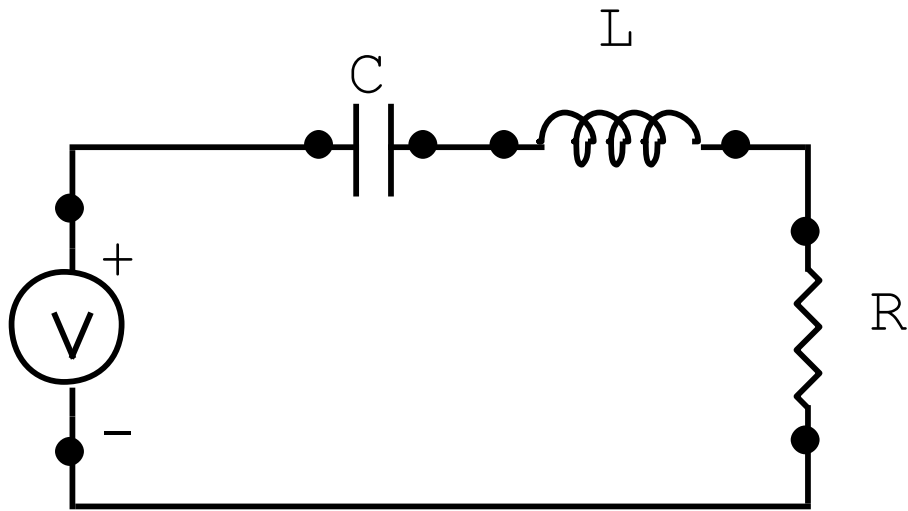

Series Resonant Circuit

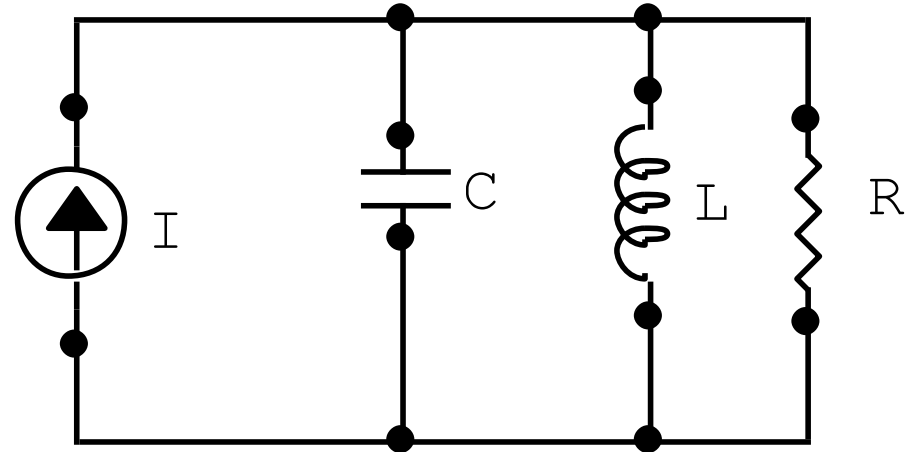

Parallel Resonant Circuit

Resonant circuits

Center resonant frequency: $f_c = \frac{1}{2\pi\sqrt{LC}}$

The quality of a resonant circuit is also a measure of selectivity, i.e. how well the tank circuit can select a specific frequency while filtering out the others.


$$Q = \frac{f_c}{BW_{3dB}}$$

Not all 'Q's are the same!

Component Q is NOT the same as circuit Q!

Component Q DOES AFFECT circuit Q!

Using Q to change the model.

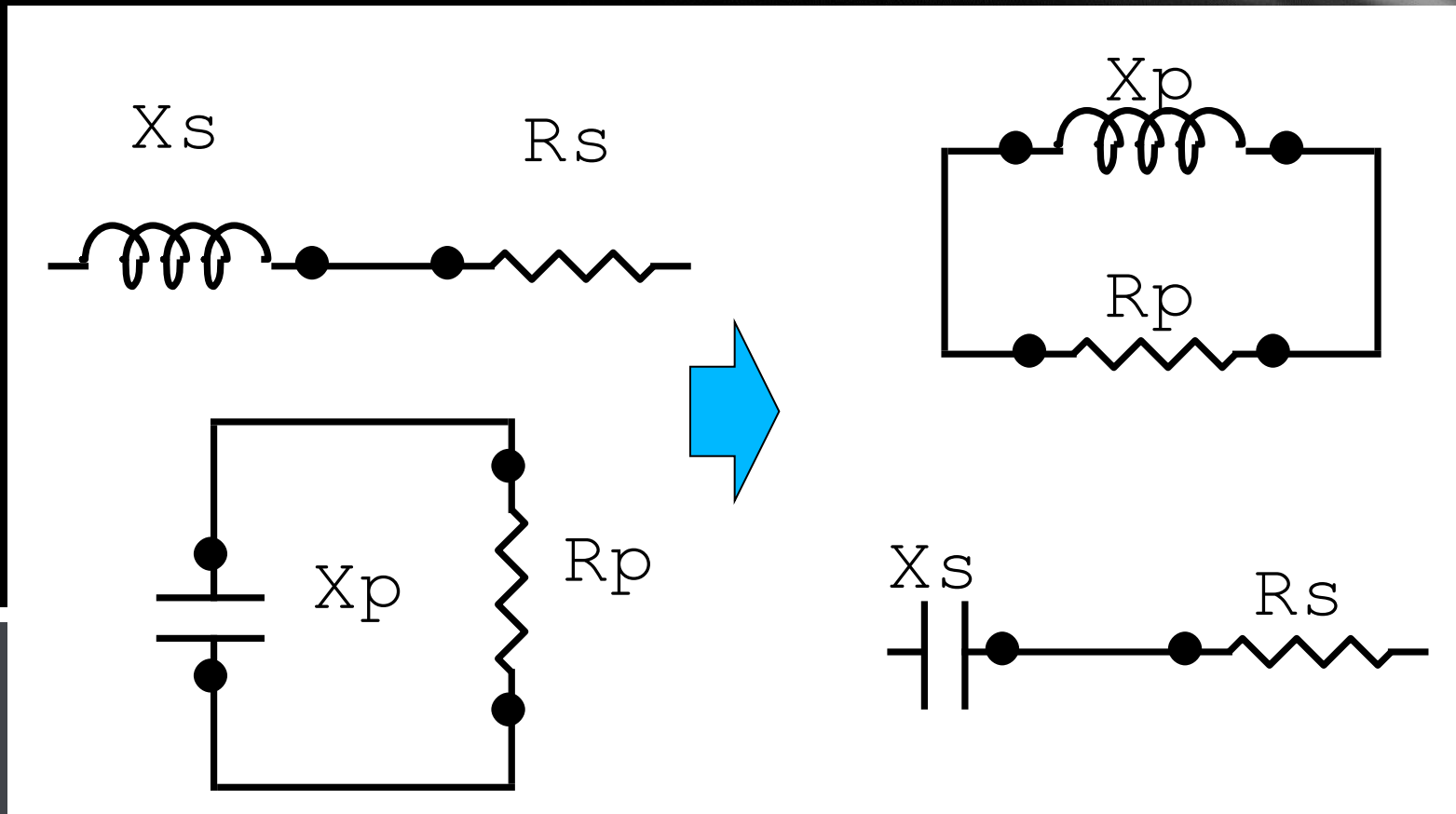

Using Q to change the model

$$R_p = (Q^2 + 1)R_s$$
$$X_p = \frac{R_p}{Q} = X_s \left(\frac{Q^2 + 1}{Q^2} \right)$$


$Q_s = Q_p$ since it's the same component. We're just using a different model.

Insertion Loss


Inductors and capacitors are not ideal!

They're resistance acts as an extra load in the circuit, not only causing changes in circuit Q , but also losses in the transfer of power.

Insertion Loss

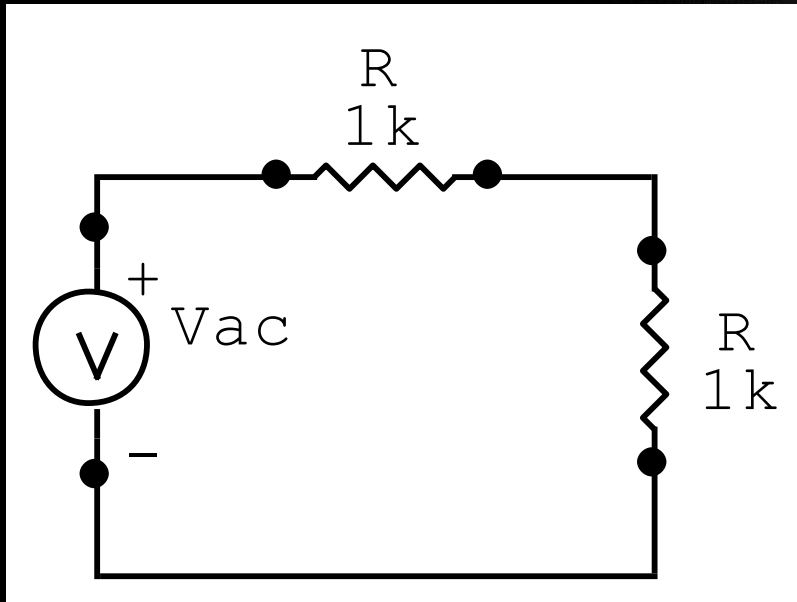

$$V_{out} = \frac{V_{ac}}{2}$$

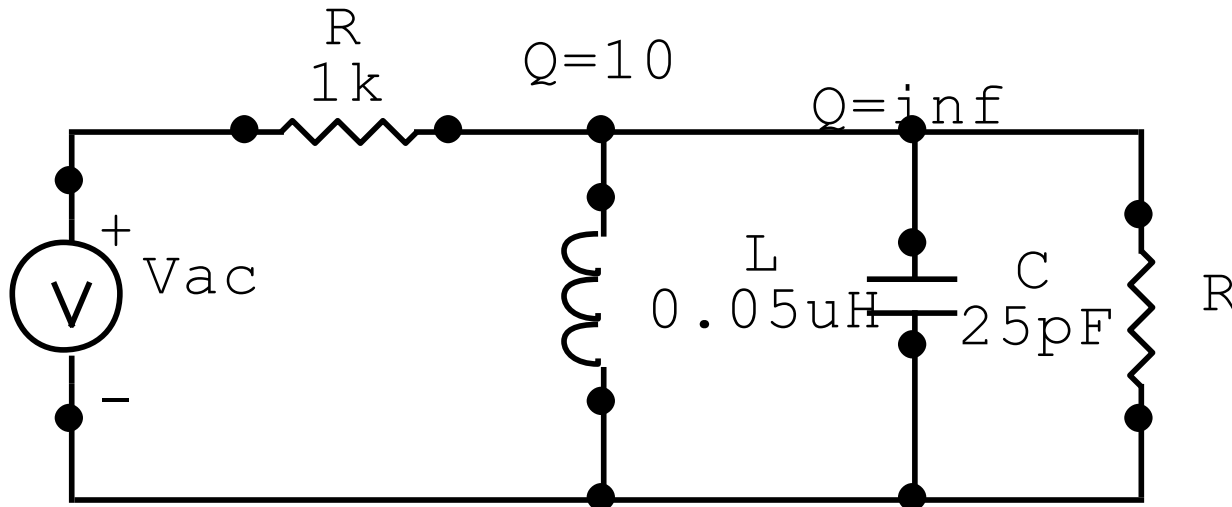

$$V_{out} = 0.45V_{ac}$$

Impedance Matching

What is matching?

Values for load to guarantee maximum transfer of power!


How does it work with complex signals?

Work with complex conjugates!

L-networks

They look like an 'L'.

Matching Networks (Two-Element L-Shape)

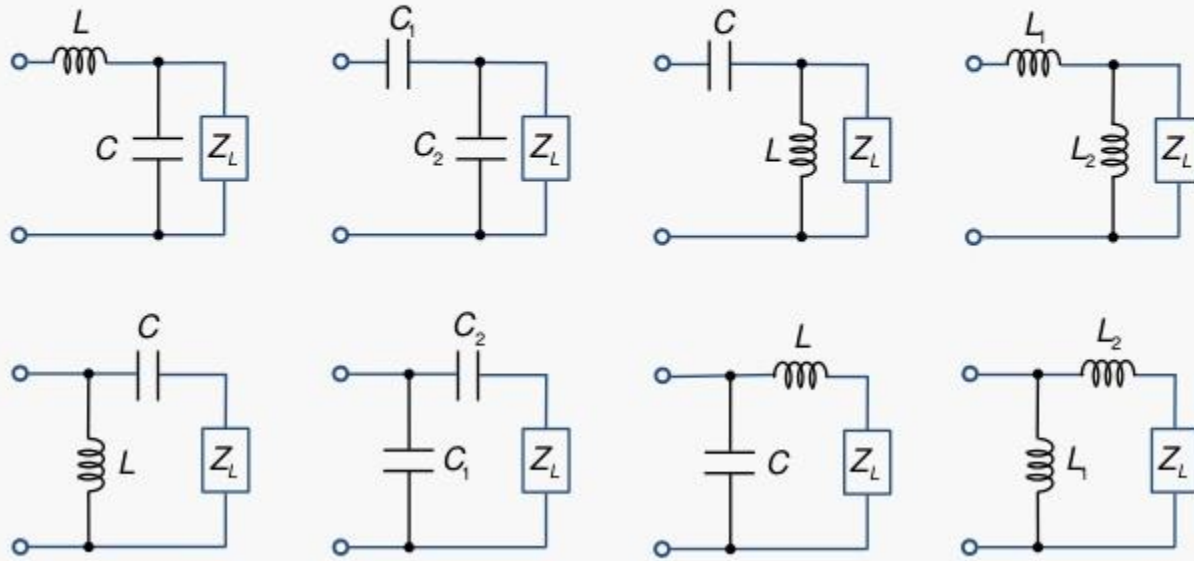

Courtesy of Simen Li, [Attribution 4.0 International](#)

Find the values of L, C .


Can do it analytically, but why?

Simplify!

Work with what we know.. $Q!$

Working with Q
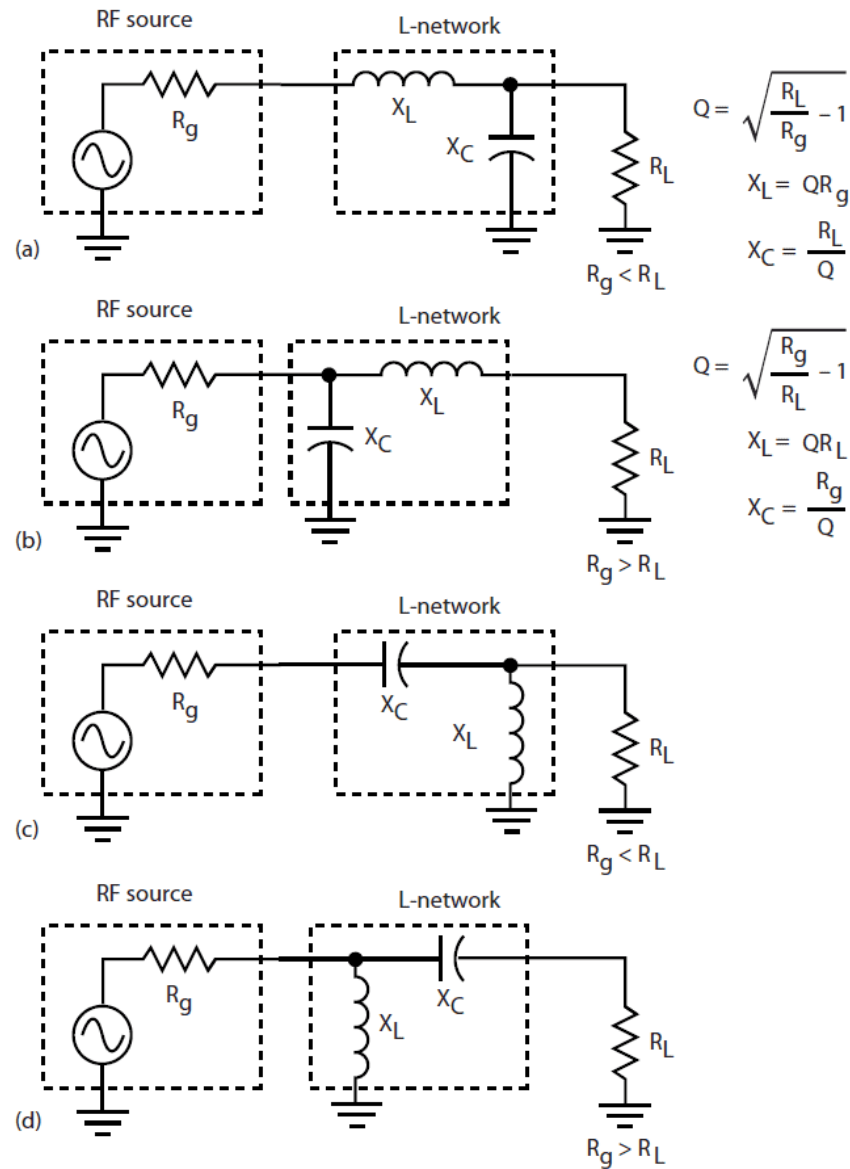
$$Q_s = Q_p = \sqrt{\frac{R_p}{R_s} - 1}$$
$$Q_s = \frac{X_s}{R_s}$$
$$Q_p = \frac{R_p}{X_p}$$



1. There are four basic L-network configurations. The network to be used depends on the relationship of the generator and load impedance values. Those in (a) and (b) are low-pass circuits, and those in (c) and (d) are high-pass versions.

Aren't we limited?

Yes!

Notice that for real Q values, $R_p > R_s$.

Q becomes fixed to a certain value.

What if we want to control Q ?

Why would we even want that?

Three-element matching (T, π)

So what do we choose?

If we can choose our Q , what's the best choice?

It depends.

High selectivity or wide bandwidth?

If wide bandwidth (minimum Q): $R = \sqrt{R_S R_L}$

Can we have several networks?

Of course!

Reference 1

Reference 2