

Laboratory 5 Design a Frequency Divider and Programming a FPGA

For your report:

- The problem written in English
- The flowchart or function table to solve the problem if it is necessary
- The design entry included (VHDL and Schematic)
- The RTL Viewer has to be included
- The simulation result for designed digital component
- The analysis for the simulation
- The pin assignment- the table for assigning the circuit inputs and outputs to specific pins on the FPGA
- The configuration for the FPGA Device (JTAG)
- The test table you designed to record and verify the designed circuit on hardware
- Picture taken for your test if it is necessary
- The conclusion

Background:

A frequency divider can be constructed from T flip-flops, where T-type flip-flop is shown in Figure 1. A T flip-flop is obtained from a JK flip-flop by tying the J and K inputs together to form the T input.

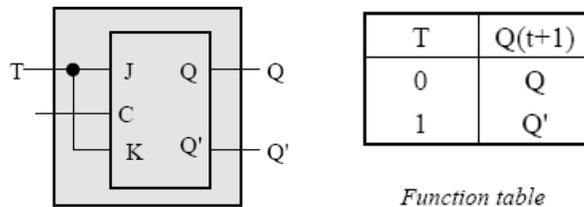


Figure 1

The input of each T flip-flops is set to 1 to produce a toggle at each cycle of the clock input. For each two toggles of the first cell, a toggle is produced in the second cell, so its output is at half the frequency of the first. The output of the third cell is 1/8 the clock frequency. The same device is useful as a counter. Figure 2 shows schematic design for three-bit frequency divider by using three T-type flip-flops.

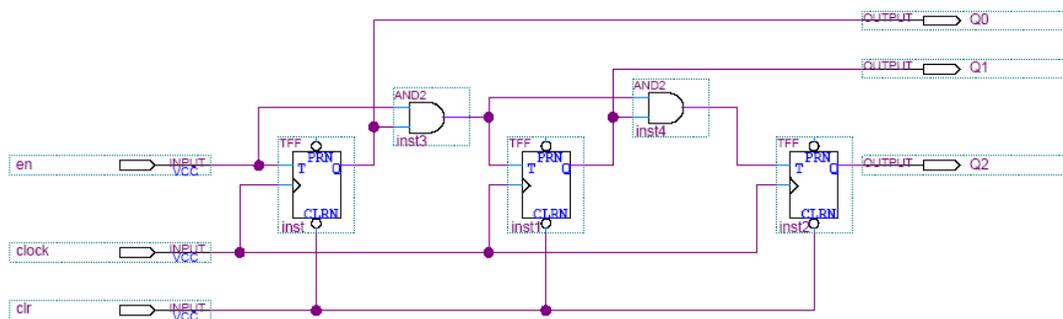


Figure 2

Figure 3 is to use the following library in your VHDL design entry

```

1  library IEEE;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_arith.all;
4  entity FreqDivider is
5      port (
6          clk      : in  std_logic;
7          enable   : in  std_logic;
8          Q0       : out std_logic;
9          Q1       : out std_logic;
10         Q2       : out std_logic
11     );
12     end FreqDivider;
13
14     architecture arc of FreqDivider is
15         signal counter: unsigned (2 downto 0);
16     begin
17         process (clk, enable)
18         begin
19             --positive triggering
20             if (clk' event and clk = '1') then
21                 if (enable = '1') then
22                     counter <= counter + 1;
23                 end if;
24             end if;
25         end process;
26
27         Q0 <= counter(0);
28         Q1 <= counter(1);
29         Q2 <= counter(2);
30     end arc;
31

```

Figure 3

Figure 4 is the simulation result. Check the relation among clock, Q0, Q1, and Q2

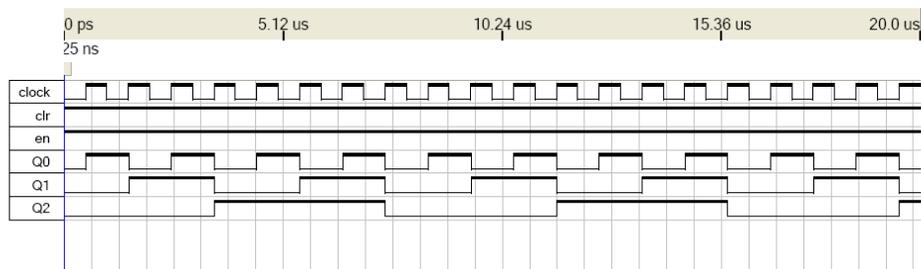


Figure 4

Suppose a clock frequency is clock = 24kHz (you can set different frequency by using function generator)
The frequency of the 2^0 output line (Q0) is 1/2 of the input clock line (12kHz)
The frequency of the 2^1 output line (Q1) is 1/4 of the input clock line (6kHz)
The frequency of the 2^2 output line (Q2) is 1/8 of the input clock line (3kHz)

Project:

Consider the extension of the circuit. Create a 8-bit synchronous counter which uses eight *T-type flip-flops* or VHDL. The counter increments its count on each *positive edge* of the clock if the *Enable* signal is asserted. The counter is reset to 0 by using the *Reset* signal.

8-bit frequency divider

1. Write a *VHDL* file or create a *BDF* file that defines a **8-bit counter (8-bit frequency divider)** by using the structure depicted in Figure 2 (bdf) or extension from Figure 3 (vhdl) or LPM freqdiv (Figure 5), and compile the circuit. What is the frequency relation between the clock and eight outputs from eight *T-type flip-flops*, respectively?
2. Create a waveform vector and simulate your circuit to verify its correctness of the design of 8-bit frequency divider.
3. Augment your VHDL file or BDF file to use the GPIO as the *Clock* input (the input from function generator), switches *SW1* and *SW0* as *Enable* and *Reset* inputs, and 8 pins from GPIO to display the divided frequencies in oscilloscope.
4. All output signals from GPIO must be connected to your breadboard in order to be observed from oscilloscope or displayed by external LEDs
5. Make the necessary pin assignments and compile the circuit.
6. Programming FPGA and test your implementation. All input and output frequencies should be measured from oscilloscope. Develop a table and record the observable frequencies. Take photos from your experiments.

| | Name | Component | Pin Location | | Name | External Component | Pin Location | Component | Pin Location |
|-------|------|--------------------|--------------|--------|------|------------------------------------|--------------|-----------|--------------|
| Input | RST | SW0 | PIN_N25 | Output | Q7 | Frequency observed on oscilloscope | | LEDG7 | |
| Input | .. | .. | | Output | Q6 | Frequency observed on oscilloscope | | LEDG6 | |
| Input | CLK | Function generator | | | : | | | | |
| | | | | Output | Q1 | Frequency observed on oscilloscope | | LEDG1 | |
| | | | | Output | Q0 | Frequency observed on oscilloscope | GPIO | LEDG0 | PIN_AE22 |

7. You may use the following library in your VHDL design entry:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;
...
```

8. Quartus II software provide a library. It is called Library of Parameterized Modules and can be found in the /others. Right-click in a new block design (bdf) workspace and choose insert> symbol **freqdiv**

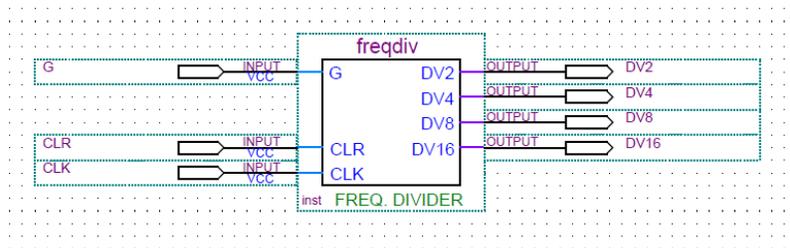


Figure 5

